

# 3- $\phi$ AC circuits

Page No. 93  
Date / /

## \* Introduction:

- Alternating voltages and currents known till now are 1- $\phi$  voltage and current as it has only one armature wdg (for alternator).
- But if the armature wdg are increased then it is known as poly-phase alternator (poly-many, phase wdg or ckt).
- Accordingly, alternator with one wdg is called 1- $\phi$  alternator and with two wdg in armature is called a 2- $\phi$  alternator. Same way for 3- $\phi$ .
- Hence the no. of phases depends on the no. of wdg.
- These wdg are displaced from each other by equal angles which may be obtained from the following relation except for 2- $\phi$  alternator whose two wdg are displaced by 90° elect.  
Phase angles =  $\frac{360^\circ}{\text{no. of phases or arm. wdg}}$
- For 3- $\phi$ ,  
Phase angles =  $\frac{360}{3} = 120^\circ$  (elect)
- 3- $\phi$  are most common although for certain special applications, greater no. of phases found to be economical.
- All modern generators are practically 3- $\phi$ .
- A polyphase sm is said to be symmetrical when the various voltages are equal in magnitude and are displaced from one another by equal angles.

## \* Advantages of 3- $\phi$ system:

→ 3- $\phi$  s/m are in common use for generation, transmission, distribution & utilization.

→ 6- $\phi$ , & 12- $\phi$  s/m are used in poly phase rectifiers.

→ 3- $\phi$  s/m are preferred over 1- $\phi$  s/m for following reasons:

(1) 3- $\phi$  s/m produce uniform torque whereas 1- $\phi$  torque pulsates.

(2) 3- $\phi$  s/m produce a rotating magnetic field, so, 3- $\phi$  motors are simpler in construction, smaller in size, better operating characteristics.

(3) To transmit the same amount of power over a fixed distance at a given voltage 3- $\phi$  s/m requires only  $\frac{3}{4}$ <sup>th</sup> weight of copper compared to required in 1- $\phi$  s/m.

(4) Voltage regulation is better.

(5) The domestic power and industrial or commercial power can be supplied from the same source.


(6) 3- $\phi$  motors are self-starting.

(7) A 3- $\phi$  m/c gives more o/p than a 1- $\phi$  m/c of the same size.


\* comparison b/w 1- $\phi$  & 3- $\phi$  supply s/m:

- Power is pulsating in 1- $\phi$ . This is not objectionable for lighting & for small motors. But for large motors, pulsating power supply causes excessive vibrations.
- 1- $\phi$  motors are not self starting, hence they required auxiliary apparatus for self starting. This is not required in 3- $\phi$ .
- Power factor in 1- $\phi$  motor is less.
- For same size, 3- $\phi$  motor can generate more o/p.
- In 3- $\phi$  transmission, the weight of copper wire is  $3/4^{th}$  of 1- $\phi$ .

\* generation of 3- $\phi$  supply:

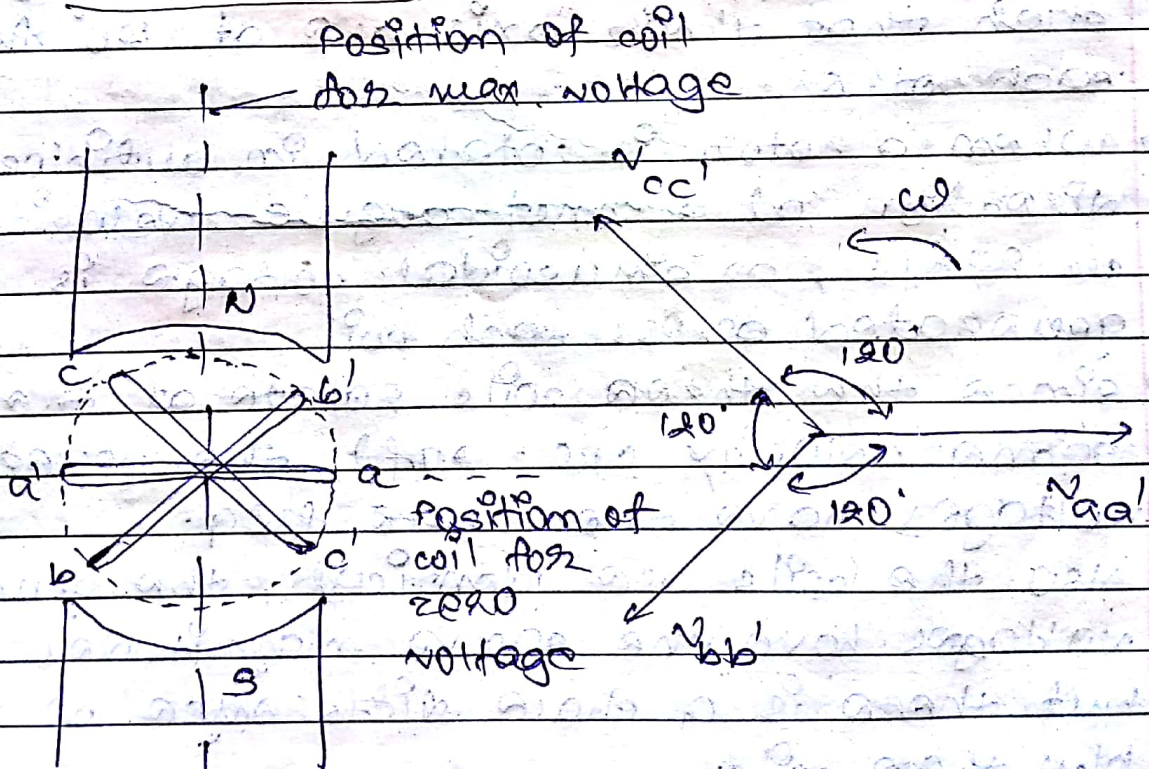

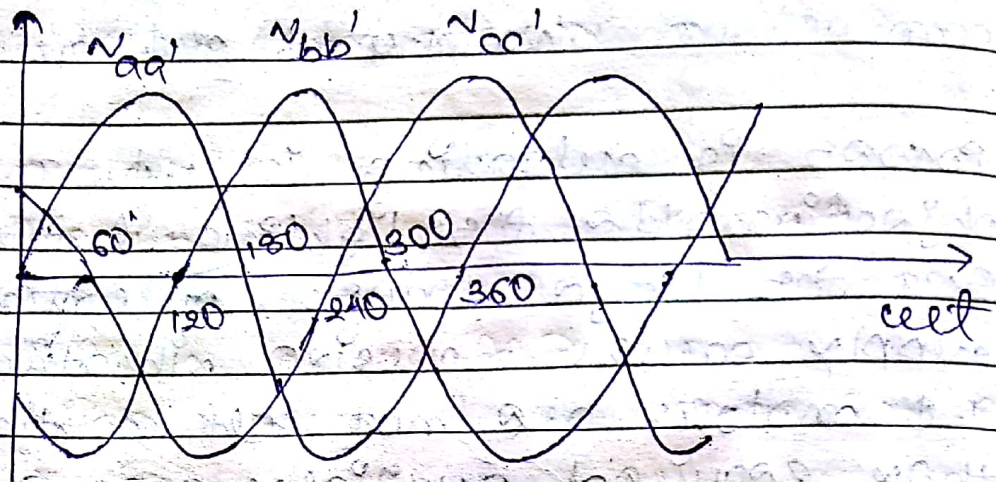[ Fig. 58 generation of 3- $\phi$  supply ]



- when 3 identical coils (or armature windings) are placed with their axis at  $120^\circ$  apart from each other and rotated in a uniform magnetic field a sinusoidal voltage is generated across each coil.
- Fig. 58 shows a 3- $\phi$  2 pole generator.
- It has sets of coil  $aa'$ ,  $bb'$  and  $cc'$  symmetrically mounted on a rotor such that their axis are at  $120^\circ$  from each other.
- when a rotor is rotated in anticlockwise direction at a const. angular velocity  $\omega$  rad/s, a sinusoidal voltage is generated across each coil.
- since the three coils rotate at the same velocity ( $\omega = 2\pi f$ ), the generated voltages have the same freq.
- Also the coils are identical, the generated voltages have the same magnitudes, but there is a phase difference of  $120^\circ$  b/w these coils.

→ The generated voltages in the coils are given by,

$$e_a = E_m \sin \omega t$$

$$e_b = E_m \sin (\omega t - 120^\circ)$$

$$e_c = E_m \sin (\omega t - 240^\circ)$$

\* Phase sequence:

→ The sequence in which the voltages in the 3 phases reach their max. positive value is called the phase sequence or phase order.

→ From a ~~3-φ~~ phase diagram of 3-φ sm, it is clear that the voltage of coil 'a' attains max. value first and then in coil 'b' and 'c'.

→ So, the phase sequence is  $a \rightarrow b \rightarrow c$ .

\* Balanced supply and Balanced load:


→ A 3-φ sm is said to be balanced if

① voltages in the ~~3-φ~~ 3 phases are equal in magnitude & displaced in phase from one another by  $120^\circ$

② currents in the 3 phases are equal in magnitude and differ in phase from one another by  $120^\circ$

③ load connected across the three phases are identical i.e. all the loads per phase have the same magnitude & power factor.

\* Star or Wye connection

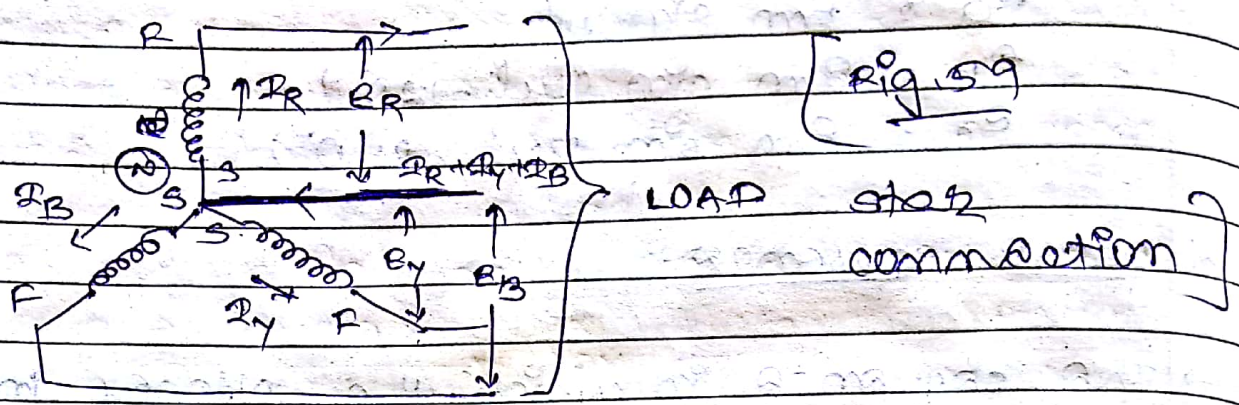


- In this method, the interconnection of the similar ends of three coils (starting or finishing end) are joined together at point  $N$  as shown in Fig. 59.
- The point  $N$  is known as star point or neutral point.
- The 3 conductors meeting at a junction  $N$  are replaced by a single conductor known as neutral conductor.
- Such an interconnection system is known as 3- $\phi$ , 4-wire system.
- If this 3- $\phi$  voltage system is applied to a balanced load system then the neutral wire will be carrying three currents equal in magnitude but are  $120^\circ$  out of phase with each other.
- Hence, the vector sum is zero.  
i.e.  $I_R + I_Y + I_B = 0$  (vectorially)
- The voltage induced in each wire is called the phase voltage ( $V_{ph}$ ) and

current in each wdg is known as phase current ( $I_{ph}$ ).

→ However, the voltage available between any pairs of terminals is called line voltage ( $V_L$ ) and current flowing in each line is called line current ( $I_L$ ).

\* Delta or Mesh connection:

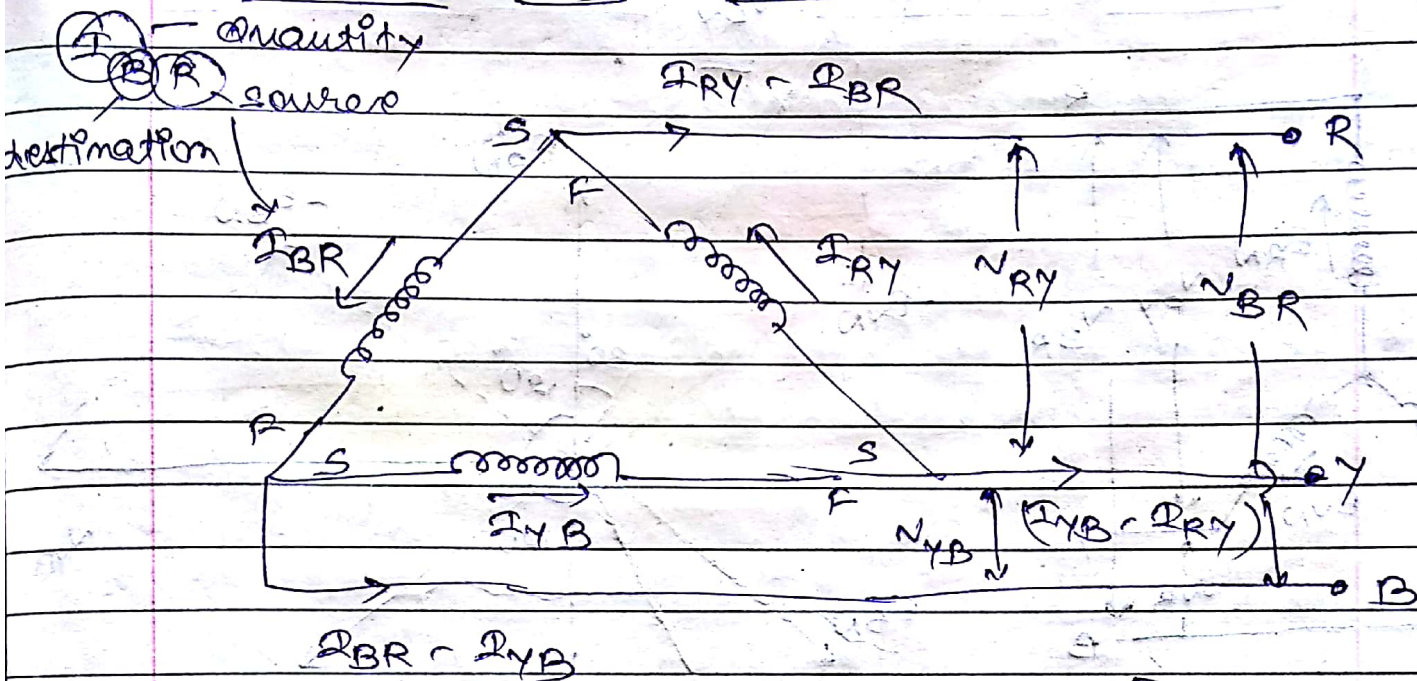


[ Fig. 60 Delta connection ]

→ In this type of interconnection, the dissimilar ends of the 3- $\phi$  wdg are joined together i.e., 'starting' end of one phase is joined to 'finishing' end of the other phase and so on as shown in fig. 60.

→ Three leads are taken out from the junctions & outward ~~junction~~ directions are taken as line.

→ As this is a balanced s/m, the sum of the three voltages around the closed path is zero.  
 → Hence, no current can flow around the mesh when terminals are open.

\* Relationship b/w line voltages and phase voltages in star connection:

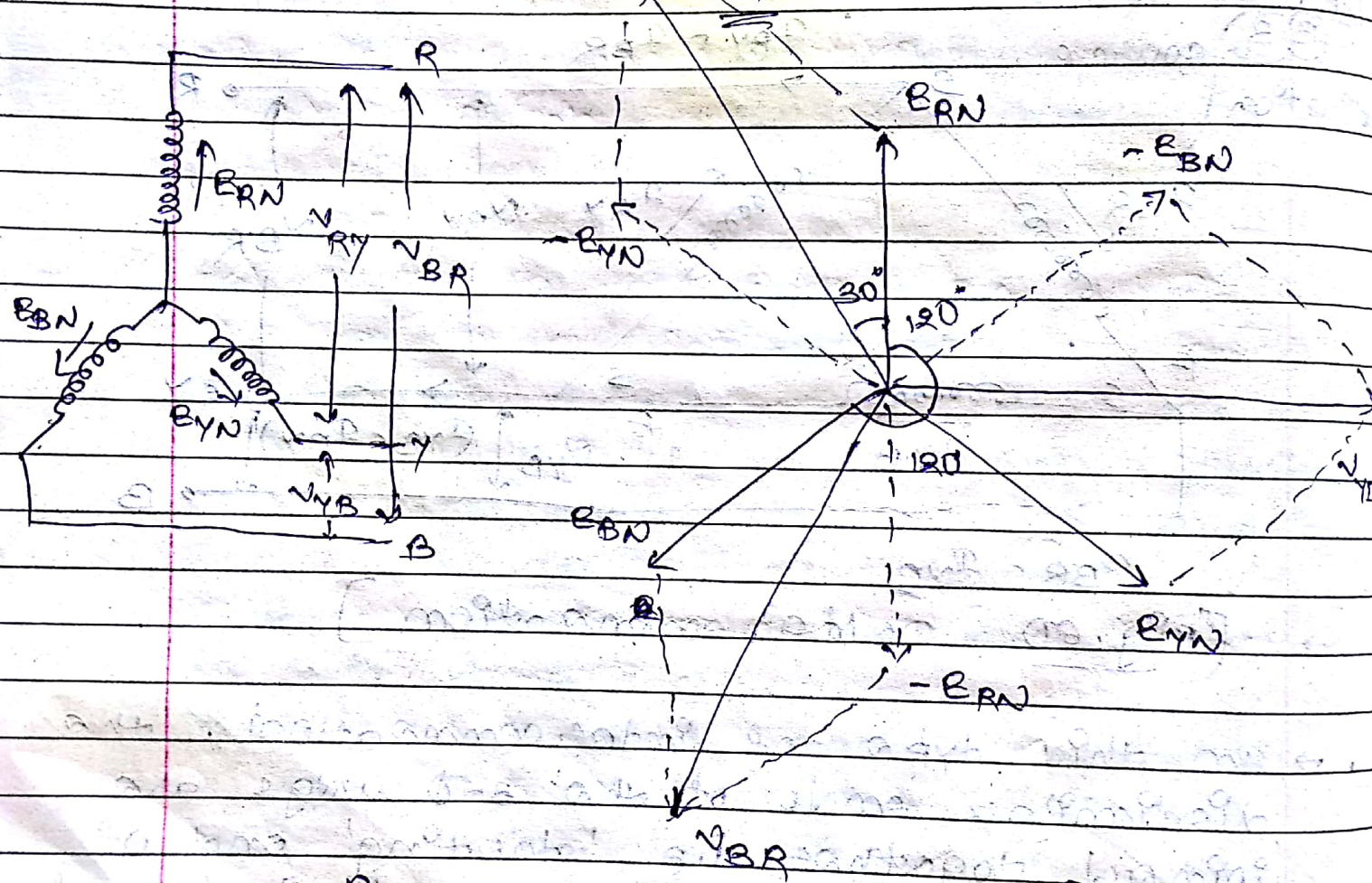

[ Fig. 6 ] star connection

→ Fig. 6] shows a balanced 3-φ star connected s/m.  
 →  $E_{RN}, E_{YN}, E_{BN}$  = rms value of sine (phase voltages) generated in 3-φ



→ As it is balanced system, the magnitude of all emf will be same but differ in phase to one another by  $120^\circ$

→ So,  $E_{RN} = E_{YN} = E_{BN} = E_{ph}$

$$E_{RN} = E_{ph} \angle 0^\circ$$

$$E_{YN} = E_{ph} \angle -120^\circ$$

$$E_{BN} = E_{ph} \angle -240^\circ$$

→ It is clear from the fig. that voltage b/w any two line terminals is the phasor difference b/w voltage of those terminals w.r. to neutral points.

→ Voltage b/w line R and Y,

$$V_{RY} = E_{RN} + E_{YN} \quad (\text{phasor sum}) \\ = E_{RN} - E_{BN}$$

→ Similarly,

$$V_{YB} = E_{YN} + E_{BN}$$

$$= E_{YN} - E_{RN}$$

$$\& V_{BR} = E_{BN} + E_{RN}$$

$$= E_{BN} - E_{YN}$$

→ To find  $V_{RY}$ , take the phasor sum of  $E_{RN}$  &  $E_{YN}$ . Draw reverse of  $E_{BN}$ . So, the difference of angle b/w phasors are  $60^\circ$

→ Thus, two phasors  $E_{RN}$  &  $-E_{BN}$  are equal in magnitude ( $E_{ph}$ ) and are  $60^\circ$  apart.

$$\rightarrow \text{Hence, } V_{RY} = 2 E_{ph} \cos\left(\frac{60^\circ}{2}\right) \quad (\text{Parallelogram law})$$

$$= 2 E_{ph} \cos 30^\circ$$

about  $2 E_{ph} \times \frac{\sqrt{3}}{2}$

$$V_{RY} = \sqrt{3} E_{ph}$$

→ simplify,


$$\begin{aligned} V_{YB} &= \sqrt{3} E_{ph} \\ V_{BR} &= \sqrt{3} E_{ph} \end{aligned}$$

→ Now,  $V_{RY} = V_{YB} = V_{BR} =$  ~~any~~ line voltage (say  $V_L$ )

→ So, in star connection,

$$V_L = \sqrt{3} E_{ph}$$

\* Relationship between line currents and phase currents

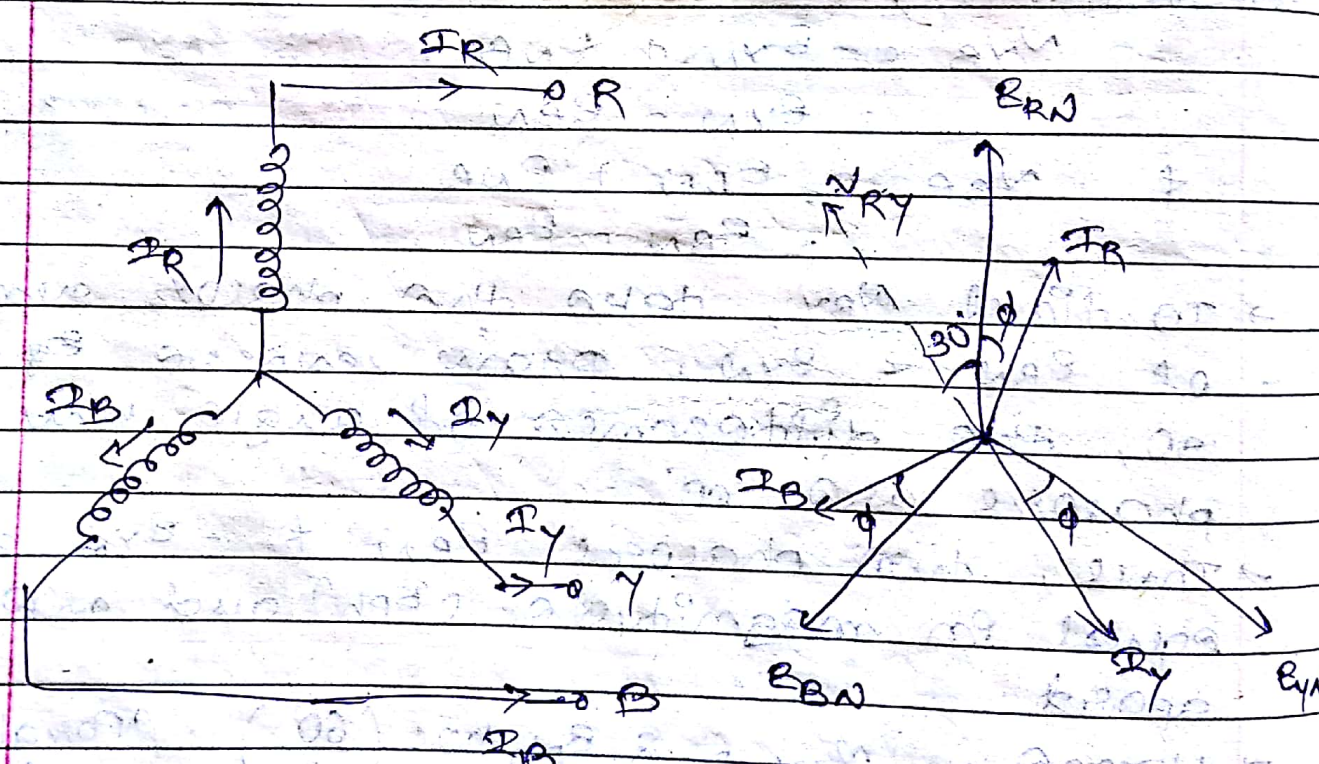

[Fig. 62] Line currents & phase currents in star connection

→ It is seen from fig. 82, that each line is in series with its individual phase winding. Assuming balanced system,

current in line R =  $I_R$   
 current in line Y =  $I_Y$   
 current in line B =  $I_B$   
 $\therefore I_R = I_Y = I_B = \text{line current } I_L$

→ Similarly,

current in phase winding R =  $I_{PR}$   
 current in phase winding Y =  $I_{PY}$   
 current in phase winding B =  $I_{PB}$

→ currents in phase winding,  
 $I_{PR} = I_{PY} = I_{PB} = \text{phase current } I_{Ph}$

→ As phase windings and lines are in series, so same current will flow through them.

→ So,  
 $I_L = I_{Ph}$

→ Hence, in balanced system,

- (1) Line current  $I_L = \text{phase current } I_{Ph}$
- (2) All currents are equal in magnitude and displaced from each other by  $120^\circ$ .
- (3) The angle b/w line current and line voltage is  $30^\circ + \theta$ .  
 + for lagging p.f.  
 - for leading p.f.

\* Expression of Power in star connection

→ Total power  $P = 3 \times$  power in each phase  
 $= 3 \times E_{ph} I_{ph} \cos \phi$   
 $= 3 E_{ph} I_{ph} \cos \phi$

→ Now, for star connection,


$$E_{ph} = \frac{V_L}{\sqrt{3}} \quad \& \quad I_{ph} = I_L$$

So,

$$P = 3 \frac{V_L}{\sqrt{3}} I_L \cos \phi$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

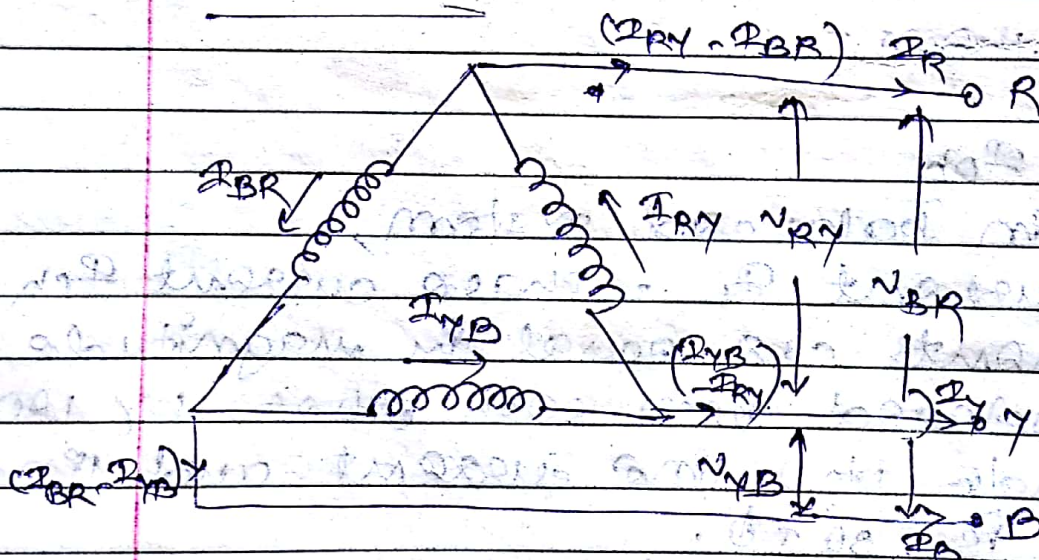\* Relationship between line voltages & phase voltages in balanced delta connection



[Fig. 63 Delta connection]

→ As due to absence of neutral point, phase voltage will be equal to line voltage.

→ And due to balanced system, all line voltages are equal in magnitude and displaced from each other at  $120^\circ$  angle.

→ So,

$V_{RY} = V_{YB} = V_{BR} = V_L$  line voltage  
and  $V_{ph} = V_L$ .

\* Relationship between line current & phase current

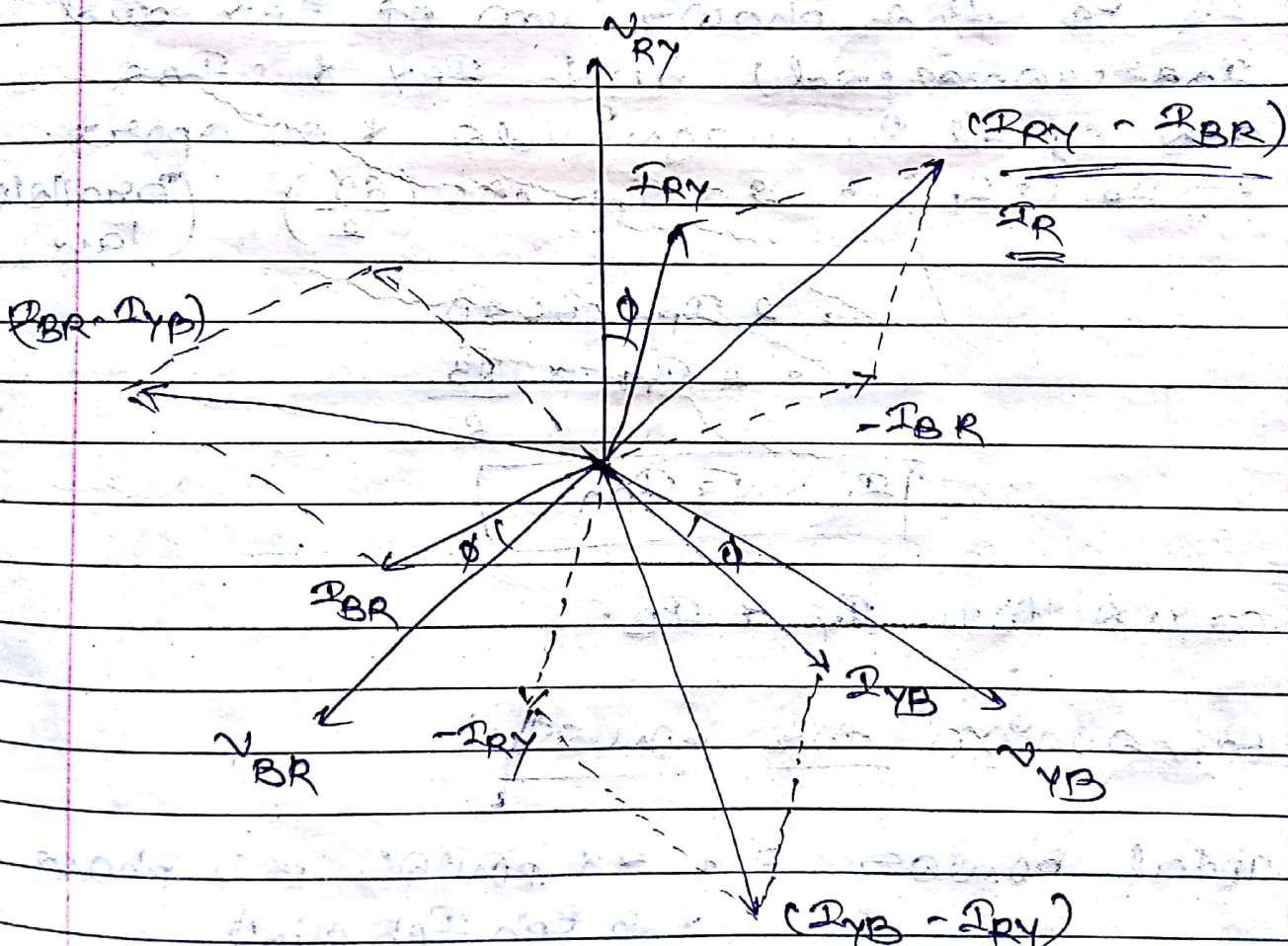


Fig. 6A phasor diagram of delta connection

→ since, the s/m is balanced, all the three phase currents are equal in magnitude and displaced from each other by angle  $120^\circ$

→ so,

$$I_{RY} = I_{YB} = I_{BR} = I_{ph}$$

→ For each line, the current is the phasor sum of two currents.

so,

$$I_R = I_{RY} - I_{BR}$$

$$I_Y = I_{YB} - I_{RY}$$

$$I_B = I_{BR} - I_{YB}$$

→  $I_R$  is the phasor sum of  $I_{RY}$  and  $I_{BR}$  (reversed) and  $I_{RY}$  &  $-I_{BR}$  are equal in magnitude &  $60^\circ$  apart.

$$\therefore I_R (= I_L) = 2 \times I_{ph} \cos\left(\frac{60^\circ}{2}\right) \quad (\text{Parallelogram law})$$

$$= 2 I_{ph} \cos 30^\circ$$

$$= 2 I_{ph} \times \frac{\sqrt{3}}{2}$$

$$\boxed{I_L = \sqrt{3} I_{ph}}$$

→ same for  $I_Y$  &  $I_B$ .

\* Expression for power:

→ Total power  $P = 3 \times$  power per phase  
 $= 3 E_{ph} I_{ph} \cos \phi$

→ For delta connection,

$$V_L = E_{ph}$$


$$I_{ph} = \frac{P_L}{\sqrt{3}}$$

$$\rightarrow \text{So, } P = 3 \times V_L \times \frac{P_L}{\sqrt{3}} \times \cos \phi$$

$$= \sqrt{3} \cdot V_L \cdot P_L \cdot \cos \phi$$

\* Measurement of power in 3- $\phi$  circuit

(1) One wattmeter method:

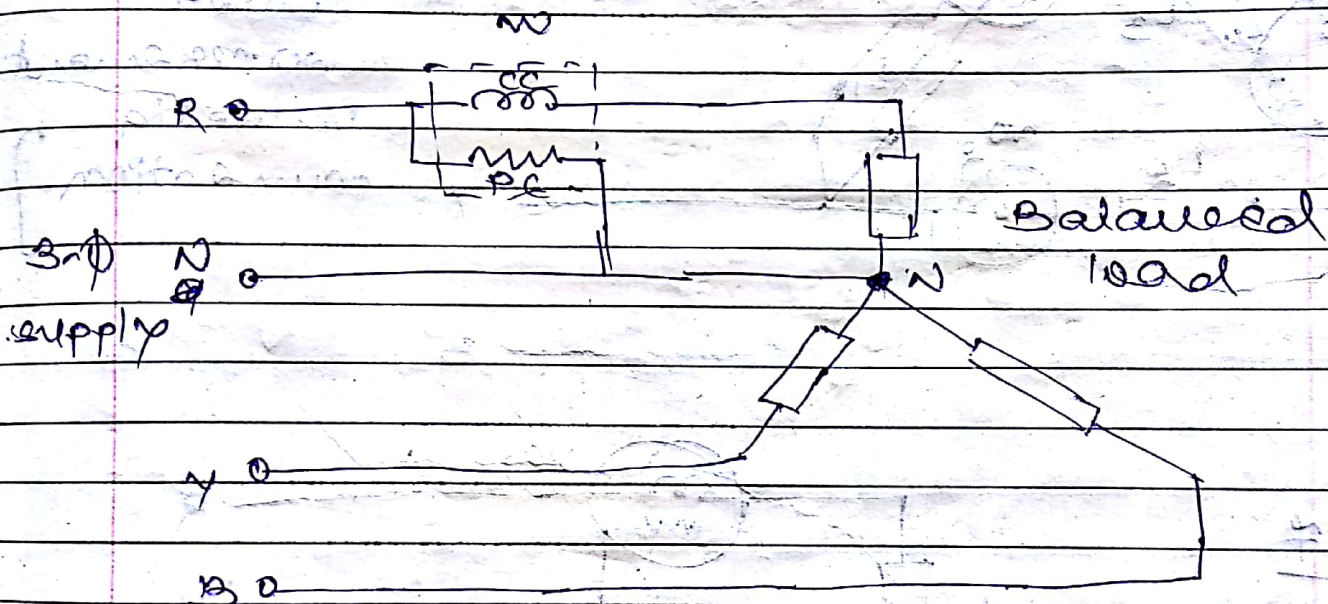

[Fig. 85 Power measurement using a single wattmeter.]

→ condition: Balanced load should be there,



→ The wattmeter is connected in any one phase and the reading is taken,  
 → Then this reading is multiplied with

no. of phases to find total power in the circuit.

→ so,

total power  $P = 3 \times$  power per phase  
 $= 3 \times$  wattmeter reading

(2) Three wattmeter method:

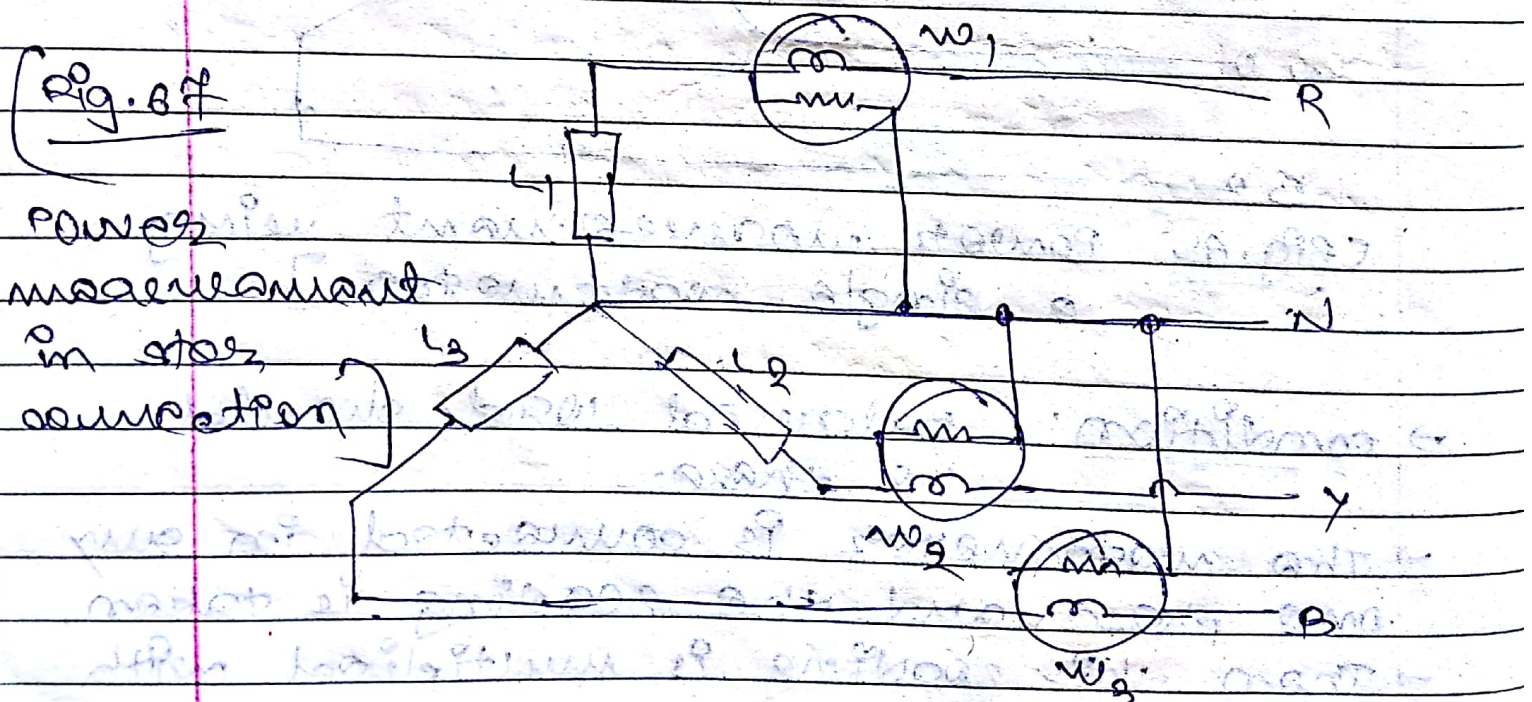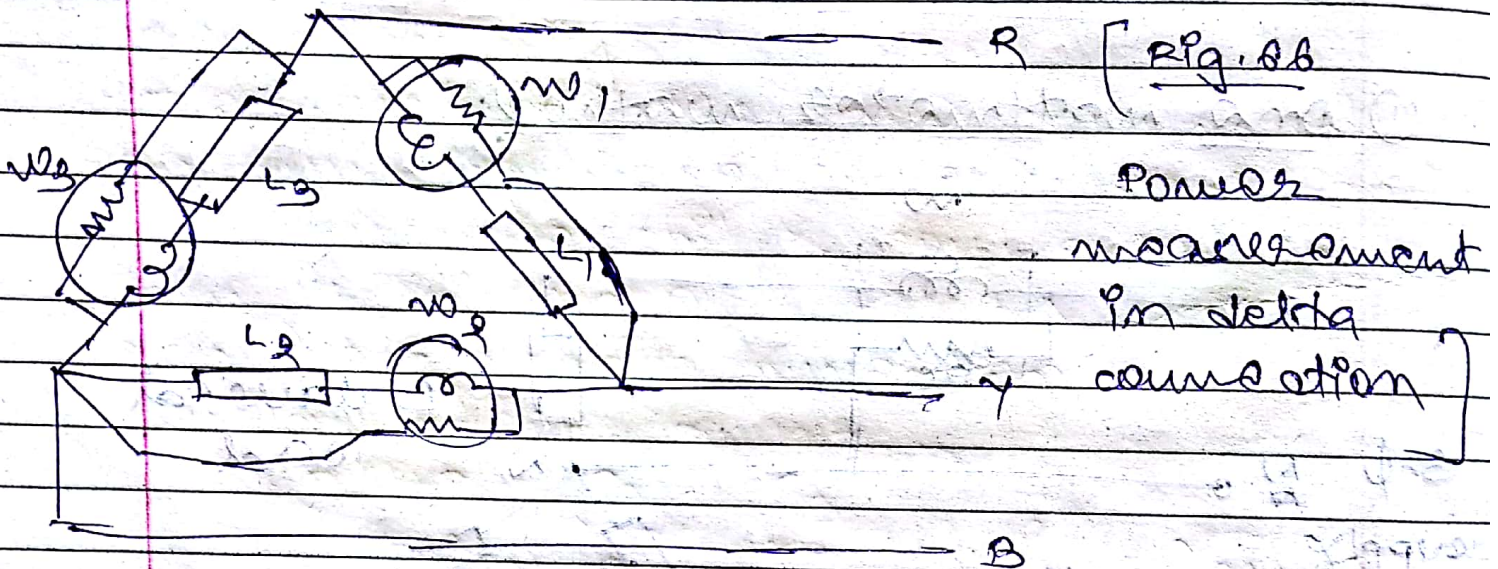




→ This method can be applicable to balanced and unbalanced  $\Delta$  in both


→ The total power,  $P = W_1 + W_2 + W_3$  (algebraic sum)

→ If neutral is not provided in star then the potential (pressure) coil is been grounded.

(3) Two wattmeter method

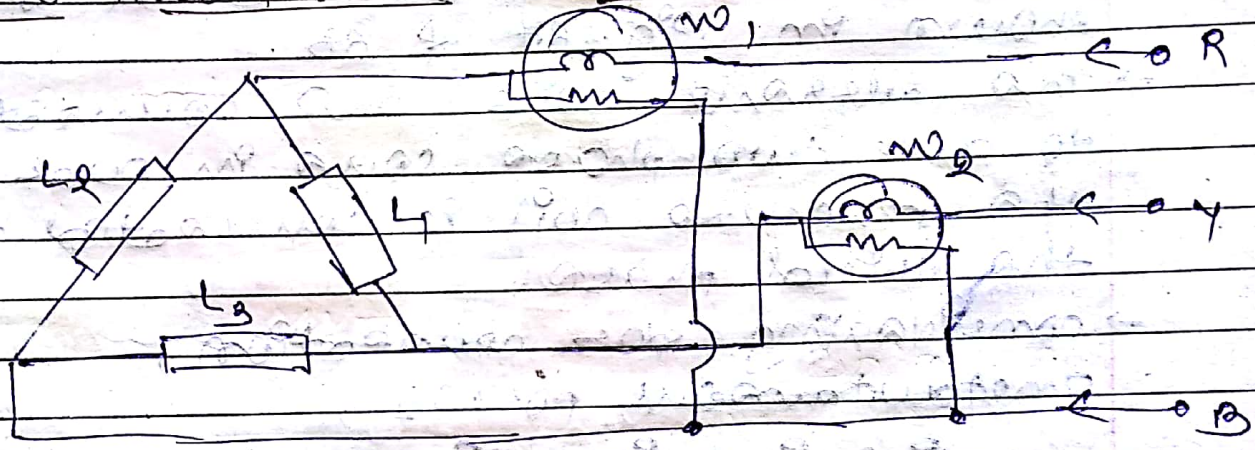

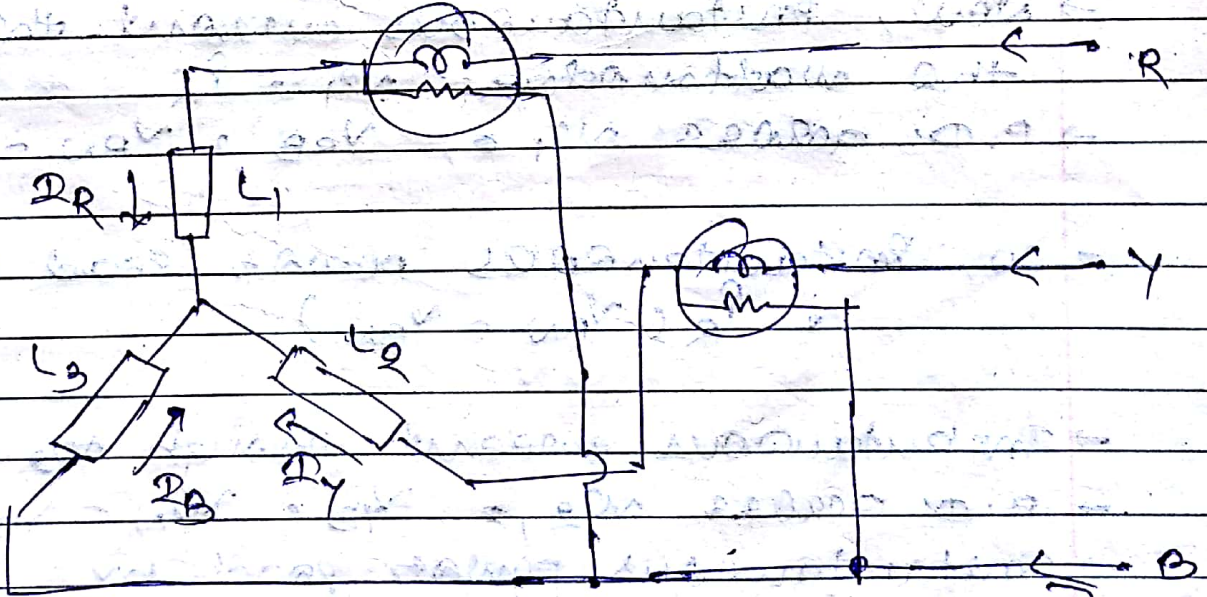[Fig. 67 2-wattmeter method for delta connected load]



[Fig. 68 2-wattmeter method for star connected load]

→ This method of power measurement can be applied to 3-phase, 3-wire s/m (balanced/unbalanced, star/delta) and 3-phase, 4-wire s/m (balanced/unbalanced) (not in unbalanced as  $I_1 + I_2 + I_3 \neq 0$ ) in unbalanced load, so power differs

→ The connections of two wattmeters for star & delta connected load is shown in Fig. 67 & 68.

→ The current coils are connected to any two phase (one in each) and the pressure coil is connected to the third phase.

→ Considering star connection, instantaneous power,

$$P = P_1 + P_2 + P_3$$

$$= V_{RN} I_R + V_{YN} I_Y + V_{BN} I_B$$

→ Now, instantaneous current through the wattmeter  $w_1 = I_R$

→ P.D. across  $w_1$  is  $V_{RB} = V_{RN} - V_{BN}$

→ So, instantaneous power read by  $w_1$  is  $I_R (V_{RN} - V_{BN})$

→ Instantaneous current through  $w_2 = I_Y$

→ P.D. across  $w_2$  is  $V_{YB} = V_{YN} - V_{BN}$

→ Instantaneous power read by

$$w_2 = I_Y (V_{YN} - V_{BN})$$

## Factorial Rate

Page No. 111

Date / /

$$\rightarrow \text{SO, } W_1 + W_2 = i_R (V_{RN} - V_{BN}) + i_Y (V_{YN} - V_{BN})$$
$$= i_R V_{RN} - i_R V_{BN} + i_Y V_{YN} - i_Y V_{BN}$$

$$= i_R V_{RN} + i_Y V_{YN} - (i_R V_{BN} + i_Y V_{BN})$$
$$= i_R V_{RN} + i_Y V_{YN} - (i_R + i_Y) V_{BN}$$

$$\rightarrow \text{NOW, } P_R + P_Y + P_B = 0 \quad (\text{KCL})$$
$$\therefore i_R + i_Y = -i_B$$

$$\rightarrow \text{SO, } W_1 + W_2 = i_R V_{RN} + i_Y V_{YN} + i_B V_{BN}$$
$$= \underline{\underline{P_1 + P_2 + P_3}}$$