

Electrostatics & capacitors

* Electrostatics:

Electrostatics is the branch of science which deals with the static charge.

* Electric charge:

The total deficiency or excess of electrons in a body is called its charge.

→ The unit of charge is coulomb

$$1 \text{ coulomb} = 6.24 \times 10^{+18} \text{ electrons}$$

→ Electric charge is denoted by Q .

* Permittivity, Absolute permittivity and Relative permittivity:

→ Permittivity is the property of a medium that affects the magnitude of the force between two point charges.

→ While, Absolute or Actual permittivity is nothing but the actual permittivity of a medium.

→ It is denoted by ϵ .

→ The Absolute permittivity of air or vacuum is denoted by ϵ_0 , and its value is $8.854 \times 10^{-12} \text{ F/m}$

→ Relative permittivity is the ratio of absolute permittivity of some material (ϵ) to the absolute permittivity of air or vacuum (ϵ_0).

→ It is denoted by Eq.

$$\epsilon_r = \frac{\epsilon}{\epsilon_0}$$

→ Here, it should be remembered that, the relative permittivity ϵ_r of air or ϵ_r vacuum is 1.

Ques. Explain the coulomb's laws of electrostatics.

OR

Explain the fundamental law of electrostatics.

Ans. coulomb, a french scientist had given two laws about the electrostatics and which are given below:

★ coulomb's first law:

"Like charges of electricity repel each other while unlike charges of electricity attract each other."

★ coulomb's second law:

"The force between two charged bodies...

- is directly proportional to the product of the magnitude of charges
- is inversely proportional to the square of the distances between them."

Mathematically,

$$\left[F \propto \frac{Q_1 Q_2}{d^2} \right] \Rightarrow \left[F \propto \frac{k Q_1 Q_2}{d^2} \right] \rightarrow \textcircled{1}$$

where,

Q_1, Q_2 = charges at point 1 & 2 respectively
 d = distance b/w two point charges
 k = constant of proportionality

→ The constant k depends upon the nature of the medium in which charges are placed

→ The value of k is determined by,

$$k = \frac{1}{4\pi \epsilon_0 q_2}$$

→ Now, put the value of k into eqⁿ $\textcircled{1}$, it becomes,

$$\left[F = \frac{q_1 q_2}{4\pi \epsilon_0 r^2} \right] \rightarrow \textcircled{2}$$

Eqⁿ $\textcircled{2}$ indicates the equation of force b/w two charges.

* Electric Field:

A region of space around a charge body in which an electric charge experiences a force of attraction or repulsion is called an electric field.

* Electric flux:

The total number of lines of force emanating from a certain charge is called electric flux.

→ It is denoted by Ψ .

→ The unit of it is a coulomb.

* Electric flux density:

It is defined as the electric flux passing through unit area at right angle to the direction of electric field.

→ It is denoted by Φ .

mathematically,

$$\Phi = \frac{\Psi}{A}$$

Ψ ? electric flux in coulomb

A ? Area in m^2

→ The unit of it is coulombs/ sq. meter (C/m^2)

Ques. What is Electric field intensity? Define the expression for electric field intensity.

Ans. Electric field intensity:

It is defined as the force experienced by a unit positive charge placed at the point.

→ It is denoted by E .

mathematically,

$$E = \frac{F}{Q} + \frac{V}{q}$$

Capacitance:

* Some important definitions:

(1) Capacitance:

Capacitance is the property of a material which stores the elec. charge.

- It is denoted by C .
- The unit is Farad (F).
- It can be found with the help of,

$$C = \frac{Q}{V}$$

(2) Dielectric:

Dielectric is nothing but the insulating material by which plates of capacitors are separated.


- Air, paper, mica etc. can be used as a dielectric.

Ques. Define the equation of a capacitance for parallel plate capacitor.

Ans. → For deriving the eqⁿ, let's consider a capacitor which have two parallel plates of area $A \cdot m^2$ as shown in fig 4(A).

→ Both the plates are separated by a dielectric of thickness 'd' meters having relative permittivity ϵ_r .

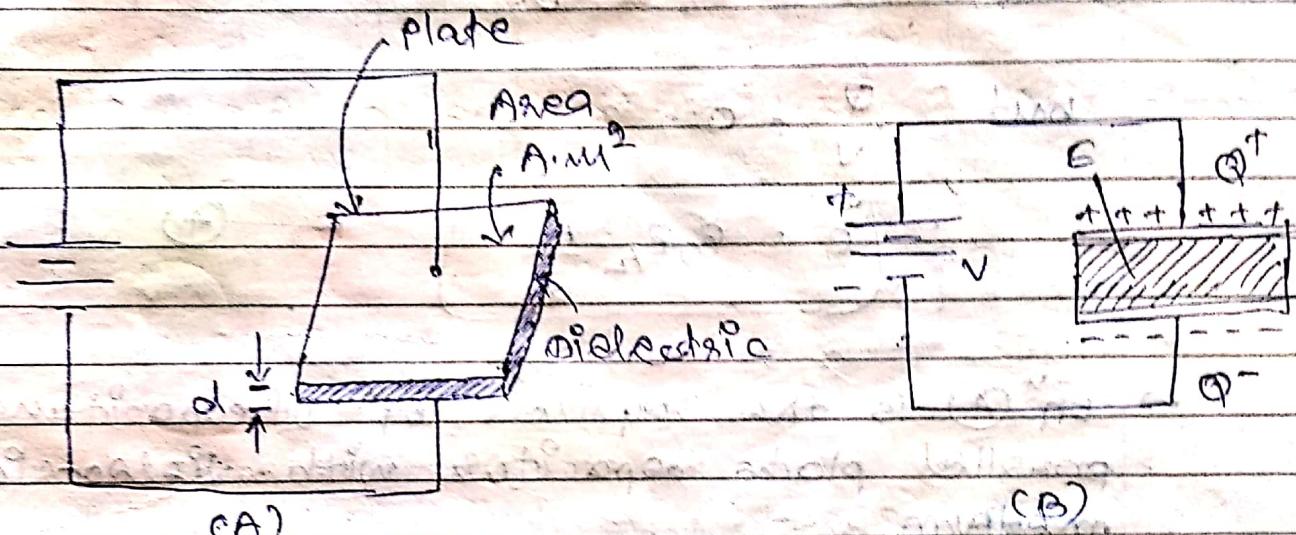→ Now, when the voltage is applied across the capacitor then $+Q$ and $-Q$ charges are established on plate A and plate B respectively shown in Fig. Q1(B).



[Fig. 1 Parallel-plate capacitors]

→ Now, as we know that, electric flux density in the dielectric is given by,

$$\Phi = \frac{\Psi}{A}$$

$$\frac{\Psi}{A} \quad (Q \propto \Psi)$$

and electric field strength in the dielectric is given by,

$$E = \frac{V}{d} \quad (2)$$

→ We also know that,

$$\Phi = \epsilon_0 \Psi E$$

$$\text{From eq } (2), \quad \Phi = \epsilon_0 \epsilon_r \frac{V}{d} \quad (3)$$

→ Now, compare eqⁿ ① + ③, we get

$$\frac{Q}{A} = \epsilon_0 \epsilon_r \frac{V}{d}$$

$$\therefore \frac{Q}{V} = \epsilon_0 \epsilon_r \frac{A}{d}$$

but

$$Q = C V$$

$$\therefore C = \epsilon_0 \epsilon_r \frac{A}{d}$$

→ Eqⁿ ④ is the required eqⁿ of capacitance for parallel plate capacitors with dielectric medium.

→ Now, if the air is the dielectric medium then the eqⁿ ④ becomes,

$$C = \epsilon_0 \frac{A}{d}$$


(as air $\epsilon_r = 1$)

Ques. Define the equation of capacitance for a parallel plate capacitor with composite dielectric.

OR

Prove that : $C = \frac{\epsilon_0 A}{\sum \frac{d}{\epsilon_r}}$

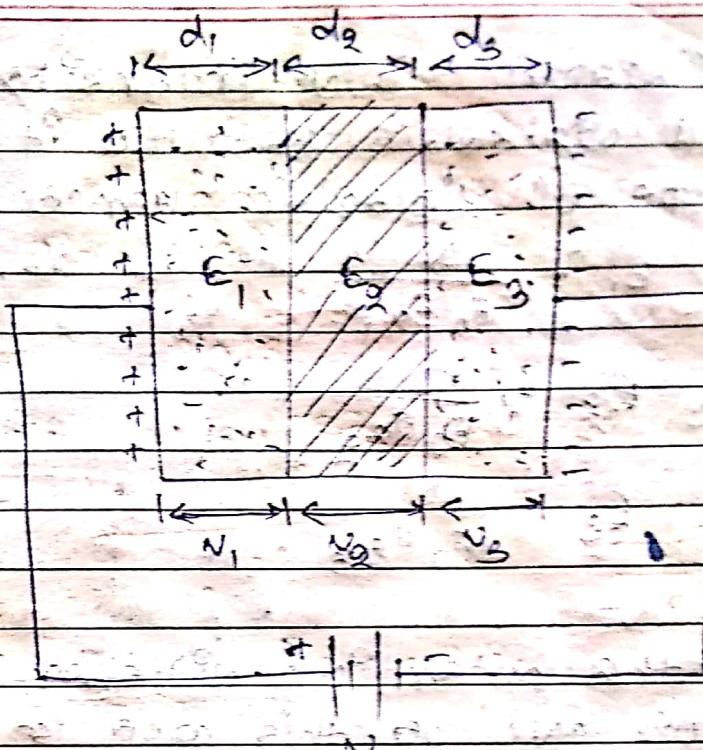Ans. For the derivation of the eqⁿ, it's consider a capacitor having three dielectric materials shown in below fig. 5



[Fig.5 parallel plate capacitors with composite dielectrics]

→ Let's hear,

d_1, d_2, d_3 = thicknesses of dielectrics & $\epsilon_1, \epsilon_2, \epsilon_3$ = relative permittivities of dielectrics

E_1, E_2, E_3 = field intensities in dielectrics

V_1, V_2, V_3 = potential difference across the dielectrics

→ The electric flux density Φ is same for all dielectric charge because it depends upon the charge and some charge would flow through all dielectrics. Hence,

$$\Phi = \frac{Q}{A}$$

while electric field intensity E is different for all dielectric because it depends upon the type of dielectric. Hence it is given by,

$$\epsilon_1 = \frac{Q}{\epsilon_0 \epsilon_{r1}}$$

$$\epsilon_2 = \frac{Q}{\epsilon_0 \epsilon_{r2}}$$

$$\epsilon_3 = \frac{Q}{\epsilon_0 \epsilon_{r3}}$$

Now, the potential difference across the capacitors (V) for this case is becomes the sum of the potential differences across three dielectrics:

$$V = V_1 + V_2 + V_3$$

$$\text{but as we know that, } \epsilon = \frac{Q}{A}$$

$$\therefore V = E \cdot d$$

$$V = E_1 d_1 + E_2 d_2 + E_3 d_3$$

$$= \frac{Q}{\epsilon_0 \epsilon_{r1}} d_1 + \frac{Q}{\epsilon_0 \epsilon_{r2}} d_2 + \frac{Q}{\epsilon_0 \epsilon_{r3}} d_3$$


$$= \frac{Q}{\epsilon_0} \left[\frac{d_1}{\epsilon_{r1}} + \frac{d_2}{\epsilon_{r2}} + \frac{d_3}{\epsilon_{r3}} \right]$$

$$\text{but } Q = \frac{Q}{A}$$

$$\text{Ans: } V = \frac{Q}{\epsilon_0 A} \left[\frac{d_1}{\epsilon_{r1}} + \frac{d_2}{\epsilon_{r2}} + \frac{d_3}{\epsilon_{r3}} \right]$$

$$V = \frac{Q}{\epsilon_0 A} \left[\frac{d_1}{\epsilon_{r1}} + \frac{d_2}{\epsilon_{r2}} + \frac{d_3}{\epsilon_{r3}} \right]$$

$$\text{but } \frac{Q}{A} = C$$

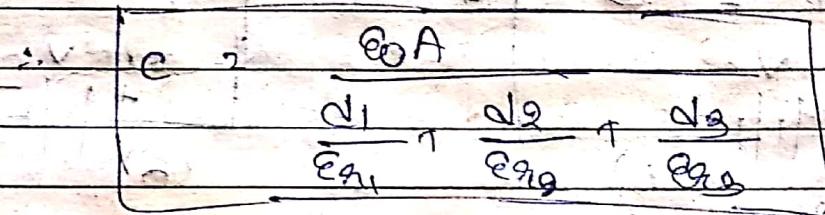

→ By ① is the required eq^u of capacitance for parallel plate capacitors with three dielectrics.


→ But, if the no. of dielectrics are given, then ϵ_r^u becomes

$$C = \frac{\epsilon_0 A}{\epsilon_r \frac{d}{d}}$$

Ques. Derive the equation of a equivalent capacitance when capacitors are connected in series.

PROVE THAT: $\frac{1}{C_{eq.}} = \sum_{n=1}^m \frac{1}{C_n}$

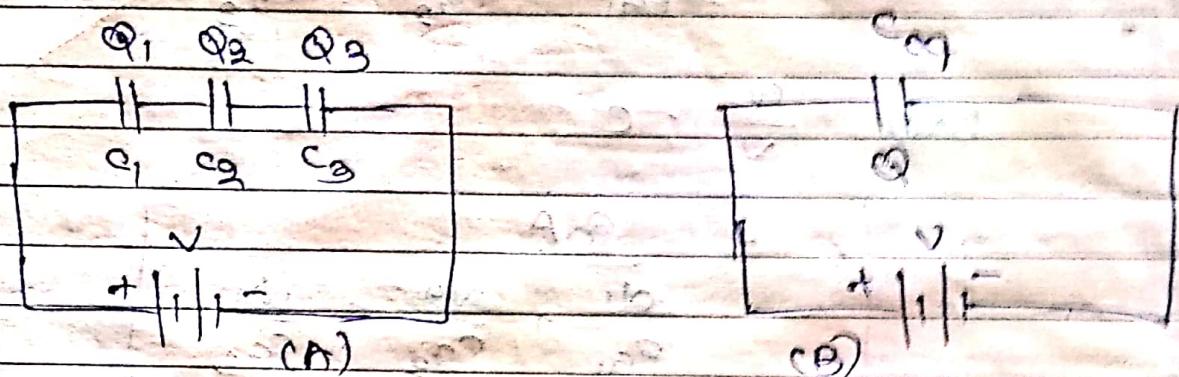Ans. For deriving the eqⁿ of a equivalent capacitance, let's consider that three capacitors having its capacitance C_1, C_2, C_3 are connected in series as shown in fig below:-



[Fig 6 series connection of capacitors]

- Here, all these capacitors are connected in series, therefore the current flows through the each capacitor is same at any point.
- Therefore, let's consider that for time t seconds, the charging current I flows through each capacitor.
- Hence, due to flow of currents (actions), the charges are developed on each capacitor. Hence,

$$Q_1 = Q_2 = Q_3 = Q = I \cdot t \quad \text{①}$$

- As we know that, when the voltage is applied across the connection then it must

be equal to the sum of voltages across each capacitors. It means -

$$V_2 = V_1 + V_2 + V_3 \quad \text{--- (2)}$$

→ But, we know that, $C = \frac{Q}{V}$

$$\text{i.e., } V = \frac{Q}{C}$$

therefore, from eqⁿ (2),

$$\text{Hence, } V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

→ Here, we have to derive the eqⁿ for a equivalent capacitance. Therefore, let's replace the series connection shown in Fig. 6 (A) by a equivalent capacitance C_{eq} shown in Fig. 6 (B). therefore,

$$\begin{aligned} & V = \frac{Q}{C_{eq}} \\ \therefore \frac{Q}{C_{eq}} &= \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3} \\ \therefore \frac{1}{C_{eq}} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad \text{--- (3)} \end{aligned}$$

→ Eqⁿ (3), indicates the eqⁿ of a equivalent capacitance when three capacitors are connected in series.

→ But if n numbers of capacitors are connected in series, then Q^4 becomes,


$$\begin{aligned} C_{eq} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n} \\ &= \frac{1}{C_{eq}} = \frac{m}{\sum \frac{1}{C_m}} \end{aligned}$$

Ques. Define the Q^4 of a equivalent capacitor when capacitors are connected in parallel.

OR

prove that: $C_{eq} = \frac{1}{\sum \frac{1}{C_m}}$

Ans.

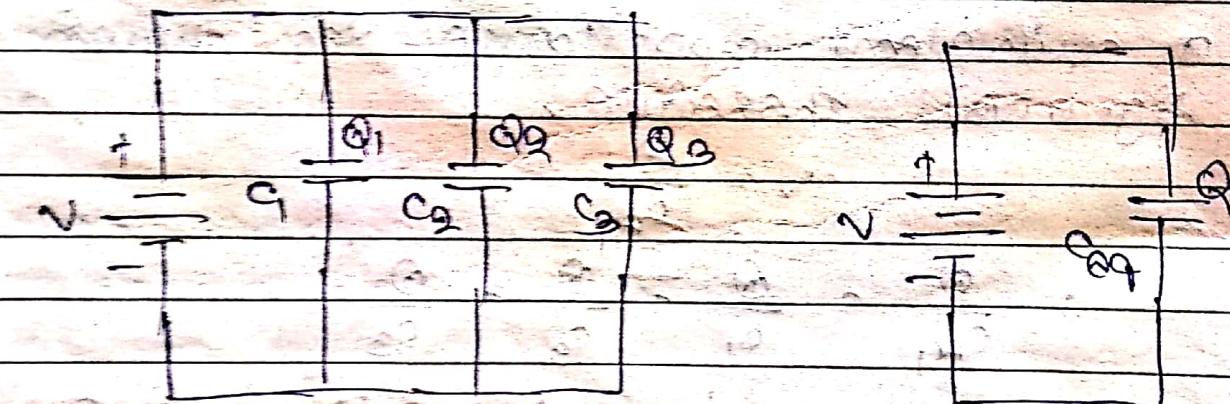

[Fig. 2(a): parallel connection] [Fig. 2(b) Equ. ckt]

→ For deriving the Q^4 , of a equivalent capacitor, let's consider three capacitors are connected in parallel as shown in Fig. 2(a).

→ When a voltage is applied across the parallel connection of capacitors, then due to closed switch, current will flow through each capacitor.

→ Here, due to parallel connection, the current flows through the each capacitor is different.

→ Hence, due to different flow of current, the charge produced by each capacitor becomes different, i.e., Q_1, Q_2, Q_3, \dots etc.

→ For deriving the eqⁿ for equivalent capacitance let's consider that the total charge produced by parallel connection must be the sum of charges produced by each capacitor, i.e.

$$Q = Q_1 + Q_2 + Q_3$$

$$\text{but } Q = C_2 \cdot V$$

$$\therefore Q = C_2 V$$

(1)

→ From eqⁿ (1),

$$Q = C_1 V + C_2 V + C_3 V$$

→ Here, we need to find out the equivalent capacitance C_{eq} , therefore let's replace the parallel connection shown in fig. 2(a), by eqⁿ. capacitance shown in fig. 2(b).

→ Eq^u (1) indicates the equivalent capacitance when these capacitors are connected in parallel.

→ But $C_{eq} = C_1 + C_2 + C_3$

→ Eq^u (2) shows the eq. capacitance when these capacitors are connected in parallel.

→ But, if n number of capacitors connected in parallel, eq^u (2) becomes

$$C_{eq} = \sum_{n=1}^m C_n$$

Ques. What is capacitor? Explain the capacitor action in detail.


Ans. Capacitor is a device which stores the electric charge.

- It consists of two conducting surfaces (plates) separated by an insulating material of dielectric in between.
- It uses Air, paper, mica, ceramic etc. as a dielectric b/w plates.

→ A capacitor may be in the form of parallel plates, concentric cylinders, concentric spheres etc. according to the shape of the plates.

* Capacitor Action:

→ As we have discussed that the capacitor is used to stored the energy, but how? so, let's understand this concept by considering & below fig. 8

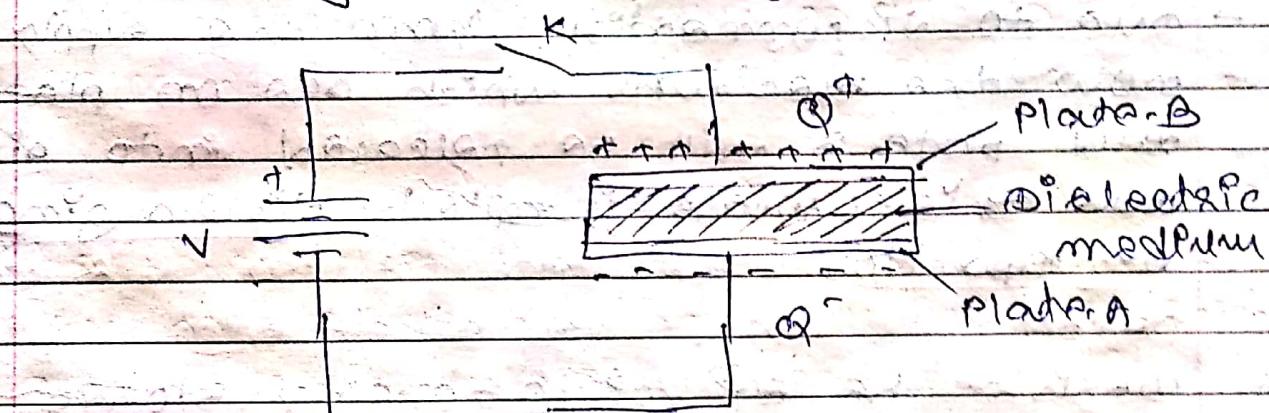

[Fig. 8]

- When the DC supply is connected across the capacitor then-
 - Due to closed circuit & potential difference, electrons starts flowing from negative terminal and positive terminal of the battery.
 - Electrons from negative terminal flows towards the bottom plate A.
 - Due to the presence of dielectric b/w two plates, electrons from plate A does not go further. Therefore, they will remain (collect) at plate A.

- Likewise, electrons from positive terminal collects at plate B.
- Due to collection of charges, plate A & plate B starts to storage of electrons charging and this process is called charging of a capacitor.
- Now, when the switch (shown in fig. 8) is open, then capacitor disconnects from the supply.
- Due to its connection from the supply, now the electrons which are on plate A and plate B will be released into air and this process is called discharging of capacitor.

Ques. Define the eqn of energy stored in a charged capacitor.

Ans.

From that: $E = \frac{1}{2} C V^2$

Ans. → As we know that, when the potential difference is applied across the capacitor, then it starts to charging.
 It means, electrons start to flow from voltage terminals to the plates of capacitor and this flowing of electrons is called workdone.

→ suppose let's take any instant of charging. At this instant, potential difference across the plates will be $\sim V$ volts.

→ After sometimes, suppose dq amount of charges is transferred then total work done is given by,

$$dW = V \cdot dq$$

①

$$\therefore \text{but } C = \frac{Q}{V} \\ \therefore Q = CV$$

take the differentiation on both sides, we get

$$\therefore dQ = C \cdot dV \quad \text{②}$$

→ put the value of dQ ② into eq ①, we get

$$dW = V \cdot dq$$

$$= V \cdot C dV$$

→ For finding total work done, take the integration on both sides, we get

$$\therefore \int dW = \int V \cdot C dV$$

→ As we have seen that, capacitor starts charging when it gets voltage across it and it still charging upto max. volt. V . Hence limit of voltage becomes $0 \rightarrow V$

$$\int \text{d}W = \int v \cdot c \cdot dv$$

$$W = c \int v \cdot dv$$

$$= c \left[\frac{v^2}{2} \right]_0^V$$

$$= c \left[\frac{V^2 - 0}{2} \right]$$

$$\boxed{W = \frac{1}{2} c V^2}$$

→ Due to this workdone, energy will be stored into the capacitor. So, we can take,

$$\text{workdone} = \text{Energy} (B) = \frac{1}{2} c V^2$$

$$B = \frac{1}{2} c V^2 N$$

$$\therefore \frac{1}{2} Q \cdot V \quad (Q = CV)$$

$$\therefore \frac{1}{2} Q \cdot \frac{Q}{C} \quad (\because V = Q/C)$$

$$\boxed{E = \frac{1}{2} \frac{Q^2}{C} \text{ joules}}$$

→ $BQ^2/2$ indicates the amount of energy stored into capacitor.

Ques. Explain the charging of a capacitor through resistor.

[OR]

Derive the eqⁿ, $V_c = V_{ci} e^{-t/RC}$)

Ans. For understanding the concept of a charging capacitor through resistor, let's consider Fig. 10.

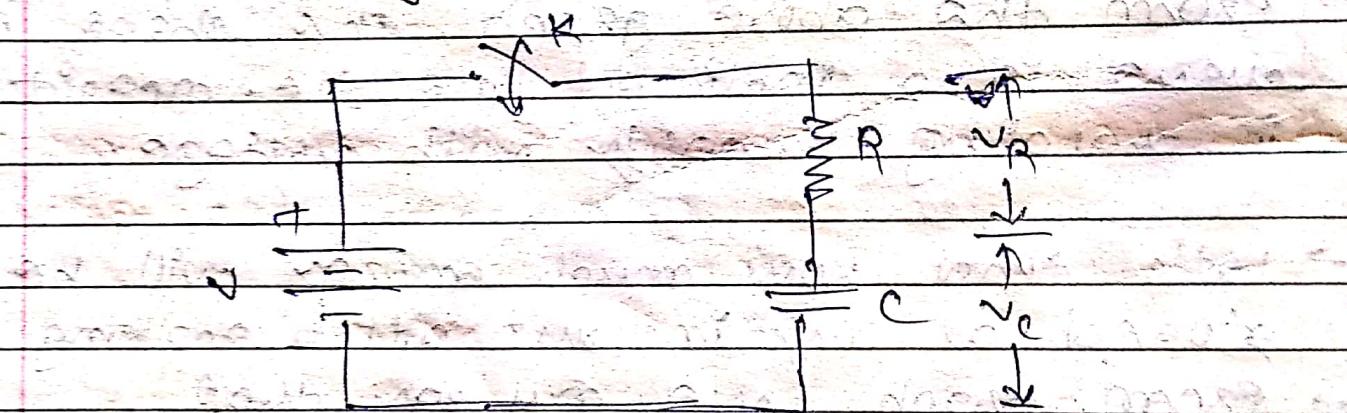


Fig. 10 charging of a capacitor through resistor

→ Fig. 10 shows that one resistor R is connected in series with capacitor.

- When the supply is connected across capacitor then it starts charging through resistor i.e. charging of capacitor can be controlled by the resistor.
- Due to potential difference, some current would flow through capacitor as well as resistor.

$$i_o = i_R \quad \text{--- (1)}$$

$$\rightarrow \text{As we know that, } C = \frac{Q}{V}$$

$$\therefore Q = CV$$

$$Q = C V_c$$

Q = charge on capacitor

C = capacitance of a capacitor

V_c = voltage across the capacitor

- Take differentiation w.r.t time on both sides, we get

$$\therefore \frac{dQ}{dt} = C \cdot \frac{dV_c}{dt}$$

$$\text{but } Q = i_R t \Rightarrow i_R = \frac{Q}{t} = \frac{\frac{dQ}{dt}}{t}$$

$$\rightarrow \text{so, } i_R = C \cdot \frac{dV_c}{dt} \quad \text{--- (2)}$$

→ While the current through resistors is given by,

$$\frac{i_R}{R} = \frac{V_R}{R}$$

but from Fig. 10, $V_R = V - V_C$

$$\therefore \frac{i_R}{R} = \frac{V - V_C}{R}$$

(3)

→ Put eqn (3) & (2) in eqn (1), we get

$$C \frac{dV_C}{dt} = \frac{V_r V_C}{R}$$

$$\therefore R.C \cdot \frac{dV_C}{dt} = V_r V_C$$

$$\therefore \frac{dV_C}{V_r V_C} = \frac{1}{RC} dt$$

→ Now, take the integration on both sides, we get,

$$\int \frac{dV_C}{V_r V_C} = \int \frac{dt}{RC}$$

$$\therefore -\ln(V_r V_C) + K = t/RC$$

whose K is constant of integration.

The value of K is obtained by considering initial conditions i.e. $V_C = 0$, $t = 0$.

$$\frac{dV}{dt} = \frac{1}{RC} (V - V_c) + K$$

$$\therefore 0 = -\ln V + K$$

$$\therefore K = \ln V$$

→ put the value of K into eq^{n. ④}, we get

$$\frac{dV}{dt} = -\ln(V - V_c) + \ln V$$

$$\therefore \frac{dV}{dt} = \frac{\ln \left(\frac{V}{V - V_c} \right)}{RC}$$

$$\therefore \frac{V}{V - V_c} = e^{\frac{t}{RC}}$$

$$\therefore \frac{V}{V - V_c} = e^{-\frac{t}{RC}}$$

$$\therefore \frac{V}{e^{-\frac{t}{RC}}} = V - V_c$$

$$\therefore V = V_c e^{-\frac{t}{RC}}$$

$$-\frac{t}{RC}$$

$$\therefore V = V_c e^{-\frac{t}{RC}}$$

$$\boxed{V_c = V_c(1 - e^{-\frac{t}{RC}})}$$

where $RC = \lambda = \text{time constant}$

$$\boxed{V_c = V_c(1 - e^{-\frac{t}{\lambda}})}$$

Ques: Explain the discharging of a capacitor through resistors.

[Ans] Describe the ac⁻ wave $v = v_0 e^{-t/R_C}$

Ans: For understanding this concept, let's consider the fig. II which is given below.

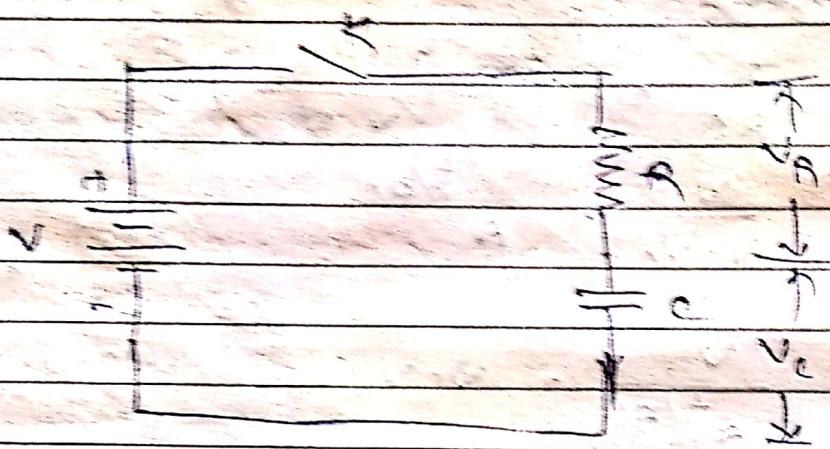


Fig. II Discharging of a capacitor through resistors]

- From fig. II, it's clear that, here switch K is open i.e. supply is disconnected from the ckt.
- Hence, capacitor starts discharging through the resistors.
- Hence, discharging current flows through R and C will be equal but opposite.
- As we know that, $C = Q/V$
 $\therefore Q = CV$
 $Q = CVC$

Q = charge on capacitors

C = capacitance of a capacitor

V_C = volt. across capacitor

→ Take differentiation w.r.t time on both sides, we get,

$$\frac{dQ}{dt} = C \cdot \frac{dV_C}{dt}$$

$$\text{but } Q = Pt \Rightarrow i_C = \frac{Q}{t} = \frac{Pt}{t} = P \quad \text{--- (1)}$$

$$\therefore i_C = C \cdot \frac{dV_C}{dt} \quad \text{--- (2)}$$

→ While current through resistor i_R is given by,

$$i_R = \frac{V_R}{R}$$

→ But from fig., $V_P = V_C$

$$\therefore i_R = \frac{V_C}{R} \quad \text{--- (3)}$$

→ Put eqn (2) & (3) in eqn (1), we get,

$$C \cdot \frac{dV_C}{dt} = -\frac{V_C}{R}$$

$$RC \cdot \frac{dV_C}{dt} = -V_C$$

$$-\frac{dV_C}{V_C} = \frac{dt}{RC}$$

→ Now, take integration on both sides, we get

$$\int \frac{dt}{RC} = \int \frac{dV_C}{-V_C}$$

$$\therefore \frac{t}{RC} = -\ln V_C + k \quad (2)$$

where k is constant of integration.

The value of k can be obtain by considering initial conditions, i.e.,

$$t=0, V_C = V$$

$$\therefore \frac{0}{RC} = -\ln V + k$$

$$k = \ln V$$

→ put the value of k into eq(2), we get

$$\frac{t}{RC} = -\ln V_C + \ln V$$

$$\therefore \frac{t}{RC} = \ln(V/V_C)$$

$$\therefore V/V_C = e^{t/RC}$$

$$\therefore \frac{V_0 - V_C}{V_0} = e^{-t/RC}$$

$$\therefore V_C = V_0 e^{-t/RC}$$

where $RC = \lambda$ = time constant

$$\therefore V_C = V_0 e^{-t/\lambda}$$

35

Ex. Examples based on capacitors:

- Ex. 1 A capacitor consists of two parallel square plates each 120mm side separated by 1 mm in air. When a voltage of 1000 V is applied b/w the plates, an average current of 12 mA flows for 5 sec. calculate,
- (a) the charge on the capacitor
 - (b) the electric flux
 - (c) the electric flux density
 - (d) the ele. field strength in the dielectric

Ans. given,

$$V = 1000 \text{ V}$$

$$I = 12 \text{ mA} = 12 \times 10^{-3} \text{ A}$$

$$t = 5 \text{ sec.}$$

$$d = 1 \text{ mm} = 1 \times 10^{-3} \text{ m}$$

$$A = 120 \text{ mm} \times 120 \text{ mm}$$

$$= 144 \times 10^2 \times 10^{-6} = 144 \times 10^{-4} \text{ m}^2$$


Find,

$$\text{(Q)} = (?)$$

$$\text{(Φ)} = (?)$$

$$\text{(D)} = (?)$$

$$\text{(E)} = (?)$$

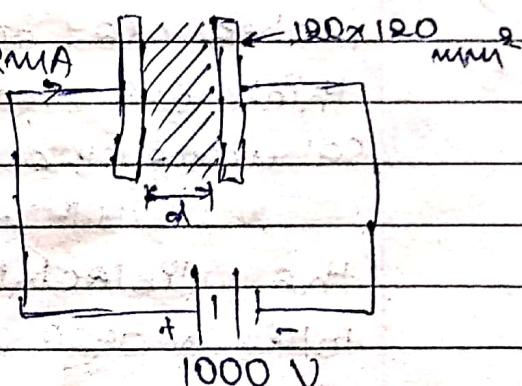

(A) charge $\text{Q} = It$

$$= 12 \times 10^{-3} \times 5$$

$$= 60 \times 10^{-3} \text{ C}$$

$$\boxed{\text{Q} = 60 \text{ mC}}$$

— Ans. (A)

(b) As we know, $Q = \psi$

$$\therefore \boxed{\psi = 60 \text{ mC}} \quad \text{Ans. (2)}$$

(c) the ele. flux density,

$$\sigma = \frac{Q}{A}$$

$$= \frac{60 \times 10^{-3}}{1.1 \times 10^{-2}}$$

$$\boxed{\sigma = 5.45 \times 10^4 \text{ C/m}^2} \quad \text{Ans. (3)}$$

(d) the ele. field strength,

$$E = \frac{\psi}{d}$$

$$= \frac{1000}{1 \times 10^{-2}}$$

$$\boxed{E = 1 \times 10^6 \text{ V/m}} \quad \text{Ans. (4)}$$

Ex. 2 A capacitor is constructed from two square metal plates each of side 120 mm. The plates are separated by a dielectric of thickness 2 mm and relative permittivity 5. Calculate the capacitance.

If the electric field strength in the dielectric is 12.5 kV/mm , calculate the total charge on each plate.

Ans: given,

$$A = 120 \text{ mm}^2$$

$$\Rightarrow 120 \times 120 \text{ mm}^2 \text{ (replaced)}$$

$$\Rightarrow 144 \times 10^{-4} \text{ m}^2$$

$$d = 9 \text{ mm}$$

$$\Rightarrow 2.2 \times 10^{-3} \text{ m}$$


$$E_0 = 5$$

$$B = 12.5 \text{ } \cancel{\text{N/mm}}$$

$$\Rightarrow 12.5 \times 10^3 \text{ N/mm} = 12.5 \times 10^8 \text{ N/m}$$

$$\therefore \text{Final, } C = ?$$

$$Q = ?$$

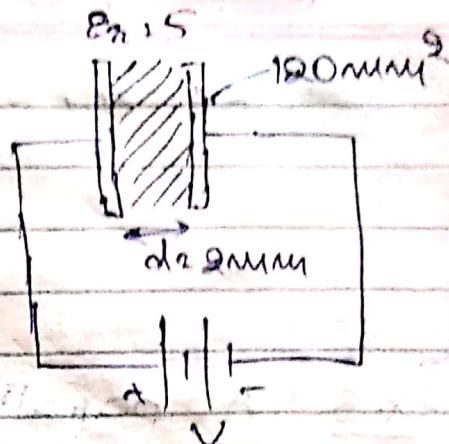

(A) As we know that, the eq for parallel plate capacitor is given by,

$$C = \frac{\epsilon_0 E_0 A}{d}$$

$$= 8.854 \times 10^{-12} \times 5 \times 144 \times 10^{-4}$$

$$\times 2 \times 10^{-3}$$

$$= 318.4 \times 10^{-12} \text{ F}$$

$$\boxed{C = 318.4 \text{ pF}}$$

Aus. (1)

(B) charge, $Q = CV$

Here, voltage is not given but electric field strength is given. Hence we know that,

$$E = \frac{V}{d}$$

$$\therefore V = Ed$$

$$= 12.5 \times 10^8 \times 9 \quad \leftarrow \text{in mm}$$

$$\boxed{V = 25 \times 10^8 \text{ V}} \quad (\text{as } E \text{ is in mm})$$

$$\text{Hence, } Q = CV$$

$$= 313.2 \times 10^{-12} \times 25 \times 10^3$$

$$= 7.833 \times 10^{-6} \text{ C}$$

$$\boxed{Q = 7.833 \mu\text{C}}$$

Ans (a)

Ex. 3 A parallel plate capacitor has plates of area 1.5 m^2 . It has three dielectrics 1 mm, 1.6 mm and 2 mm thick. The relative permittivities of these dielectrics are 2, 4 and 5 respectively; calculate the capacitance of the capacitor and the electric field strengths in the dielectrics. If a voltage of 2.5 kV is applied b/w the plates.

Ans. Given,

$$A = 1.5 \text{ m}^2$$

$$d_1 = 1 \text{ mm} = 1 \times 10^{-3} \text{ m}$$

$$d_2 = 1.6 \text{ mm} = 1.6 \times 10^{-3} \text{ m}$$

$$d_3 = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}$$

$$\epsilon_{r1} = 2$$

$$\epsilon_{r2} = 4$$


$$\epsilon_{r3} = 5$$

$$V = 2.5 \text{ kV} = 2.5 \times 10^3 \text{ V}$$

$$= 2500 \text{ V}$$


Find,

$$d_1, d_2, d_3$$

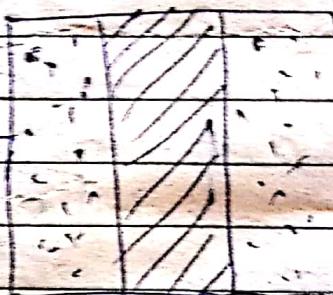

$$\epsilon_{r1}, \epsilon_{r2}, \epsilon_{r3}$$

$$2, 4, 5$$

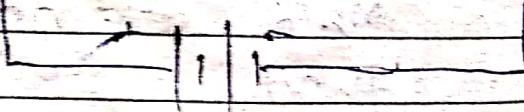

$$V_1, V_2, V_3$$

$$C = (?)$$

$$E_1 = (?)$$

$$E_2 = (?)$$

$$E_3 = (?)$$

Ans. (1) As we know the eq^m of a capacitor of a parallel plate with composite dielectrics and it is given by,

$$C = \frac{\epsilon_0 A}{\frac{d_1}{\epsilon_{r1}} + \frac{d_2}{\epsilon_{r2}} + \frac{d_3}{\epsilon_{r3}}}$$

$$\begin{aligned} & 8.854 \times 10^{-12} \rightarrow 1.5 \\ & \left(\frac{1}{2} + \frac{1.6}{4} + \frac{2}{5} \right) \times 10^{-3} \\ & = 10.216 \times 10^{-9} F \end{aligned}$$

$$C = 10.216 \text{ mF}$$

Ans (1)

(2) As we know that, electric field strength for dielectric ϵ_r is given by,

$$E = \frac{\phi}{\epsilon_0 \epsilon_r}$$

$$\text{where, } \phi = \frac{Q}{A}$$

but $\phi = CV$

$$\begin{aligned} & 10.216 \times 10^{-9} \times 9500 \\ Q & = 95.54 \times 10^{-6} C \end{aligned}$$

$$\phi = \frac{95.54 \times 10^{-6}}{1.5}$$

$$\phi = 17.027 \times 10^{-6} \text{ C/m}^2$$

Hence, $E_1 = ?$

$$E_0 E_{n_1}$$

$$12.097 \times 10^6$$

$$3.854 \times 10^{12} \times 2$$

$$E_1 = 0.98154 \times 10^8 \text{ N/C}$$

Ans (1)

$B_2 = ?$

$$E_0 E_{n_2}$$

$$12.097 \times 10^6$$

$$3.854 \times 10^{12} \times 4$$

$$E_2 = 0.481 \times 10^8 \text{ N/C}$$

Ans (2)

$B_3 = ?$

$$E_0 E_{n_3}$$

$$12.097 \times 10^6$$

$$3.854 \times 10^{12} \times 5$$

$$E_3 = 0.381 \times 10^8 \text{ N/C}$$

Ans (3)

Ex:
Ques. 4


Two capacitors having capacitances of 6 μF and 10 μF respectively are connected in parallel. A 18 μF capacitor is connected in series with the parallel combination and the complete circuit is connected across a 400 V DC supply. Calculate,

(a) total capacitance of the circuit

(b) the voltage across each capacitor

(c) total charge in the circuit

(d) charge on capacitors.

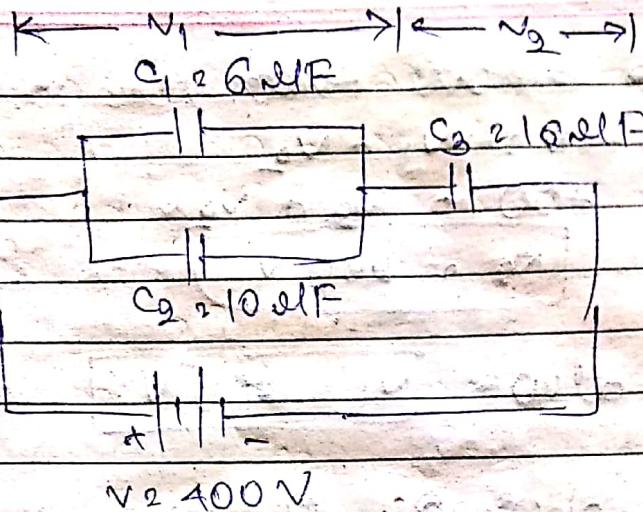Ans.

(1) Here, c_1 and c_3 are connected in parallel.

$$\text{Hence, } C_{12} = 6 + 16$$

$$C_{12} = 16 \mu F$$

and $C_2 = 16 \mu F$ capacitor is connected in series with parallel combination.

Hence,

$$\text{total capacitance, } \frac{16 \times 16}{16 + 16}$$

$$C_T = 8 \mu F$$

Ans ①

(2) As we know that, $Q = CV$

$$Q = C_p V_1 = C_s V_2$$

$$\frac{V_1}{V_2} = \frac{C_s}{C_p}$$

$$\frac{16}{16}$$

$$\frac{V_1}{V_2} = 1$$

$$\therefore V_1 = V_2$$

As we know that;

$$N = N_1 + N_2$$

$$400 = N_2 + N_1$$

$$N_2 = 200 \text{ V}$$

Ans. ②

and also $N_1 = 200 \text{ V}$ ($CN_1 = V_2$) Ans. ③

(3) Total charge $Q = CN$

$$= 8 \text{ MF} \times 400$$

$$= 8 \times 10^{-6} \times 400$$

$$= 3.2 \times 10^{-3} \text{ C}$$

$$Q = 3.2 \text{ mC}$$

Ans. ③

(4) charge on capacitor (C_1)

$$Q_1 = C_1 V_1$$

$$= 6 \times 10^{-6} \times 200$$

$$Q_1 = 1.2 \text{ mC}$$

Ans. ④

charge on capacitor (C_2)

$$Q_2 = C_2 N_2$$

$$= 10 \times 10^{-6} \times 200$$

$$Q_2 = 2 \text{ mC}$$

Ans. ④

charge on capacitor (C_3)

$$Q_3 = C_3 N_3$$

$$= 16 \times 10^{-6} \times 200$$

$$Q_3 = 3.2 \text{ mC}$$

Ans. ④