

Chapter 2 AC - DC Converter

Contents of Chapter

- Single phase and three phase rectifier (type of AC input)
- Uncontrolled and controlled rectifier (use of diode or SCR)
- Analysis with R, R-L and R-L-E load
- Effect of source impedance
- PF improvement for uncontrolled rectifier
- Filters

Diode Circuits or Uncontrolled Rectifier

Rectification: The process of converting the alternating voltages and currents to direct currents

Performance Parameters

$$\eta = P_{dc} / P_{ac} \quad \text{rectification efficiency}$$

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$FF = V_{rms} / V_{dc} \quad \text{form factor}$$

ripple factor

$$RF = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \sqrt{\frac{V_{rms}^2}{V_{dc}^2} - 1} = \sqrt{FF^2 - 1}$$


$$THD_i = \sqrt{\frac{I_S^2 - I_{S1}^2}{I_{S1}^2}} = \sqrt{\frac{I_S^2}{I_{S1}^2} - 1}$$

$$THD_v = \sqrt{\frac{V_S^2 - V_{S1}^2}{V_{S1}^2}} = \sqrt{\frac{V_S^2}{V_{S1}^2} - 1}$$

$$PF = \frac{P}{V_S I_S} = \frac{V_S I_{S1} \cos \phi_1}{V_S I_S} = \frac{I_{S1}}{I_S} \cos \phi_1$$

*= DistortionFactor * Displacement Faactor*

Instantaneous Values

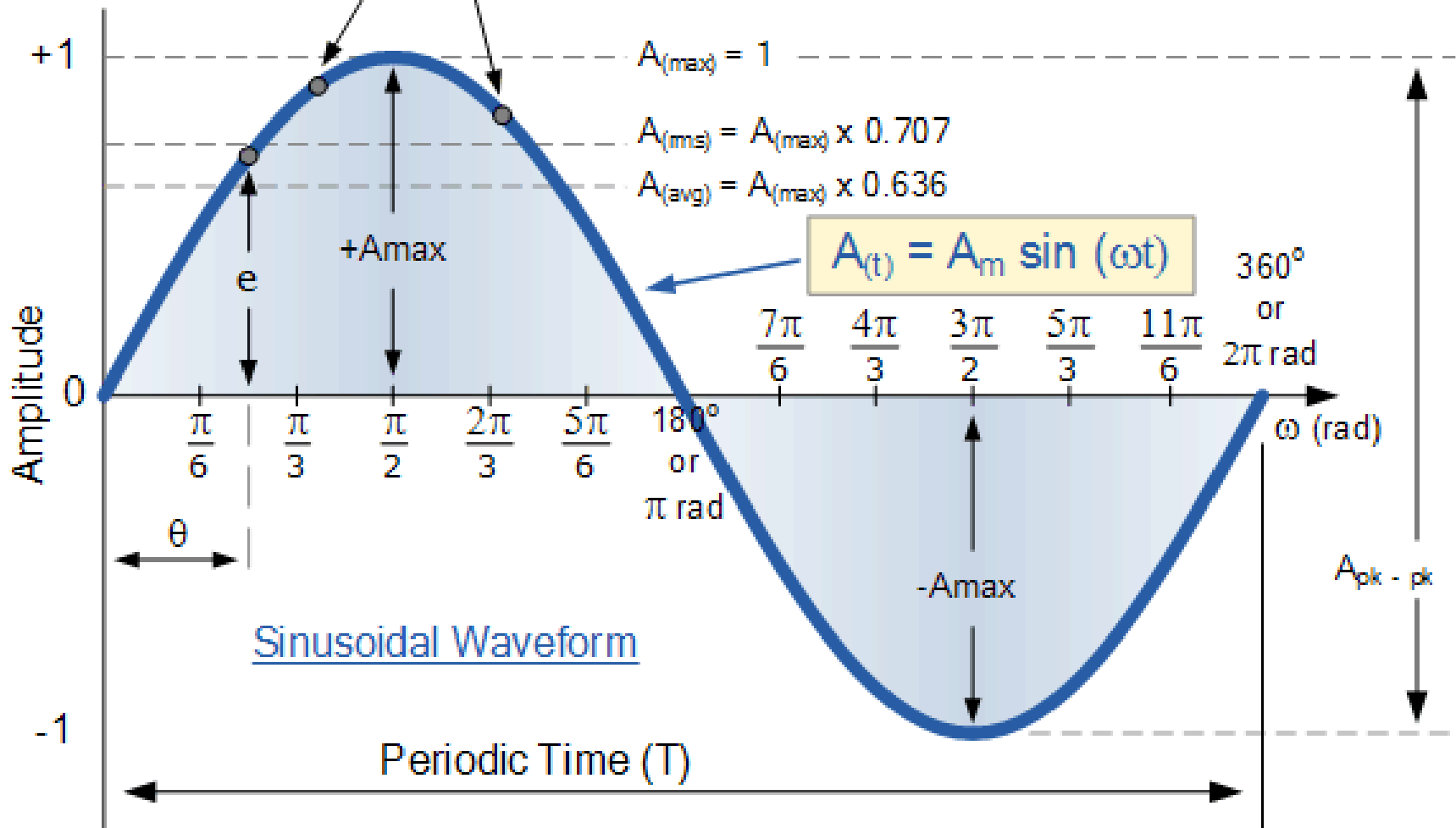



Important Equations to Remember


$$V_p \times .707 = V_{rms}$$

$$V_{rms} = 1.11 \times V_{avg}$$

$$1.414 \times V_{rms} = V_p$$

$$V_{avg} = .637 \times V_p$$

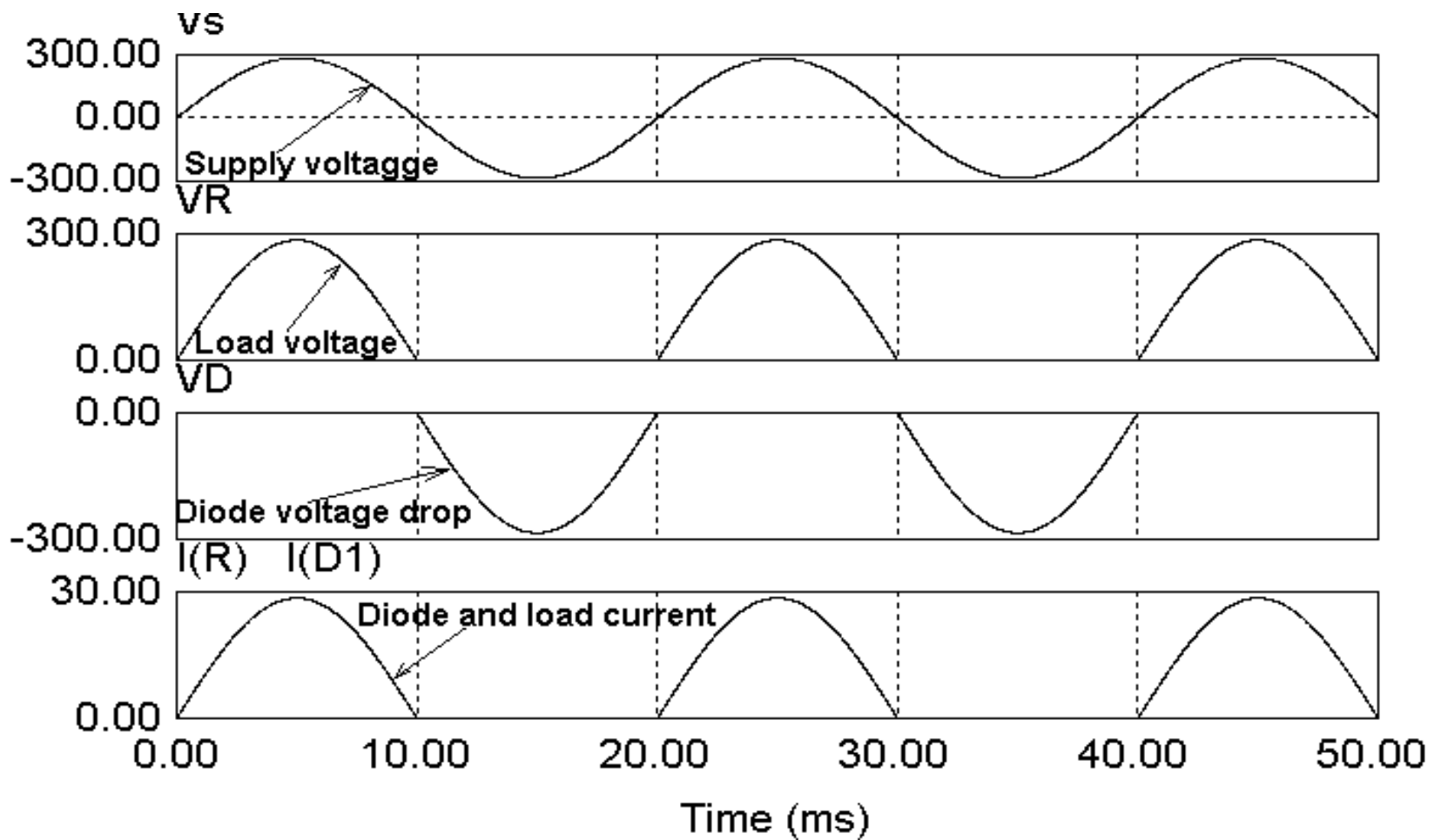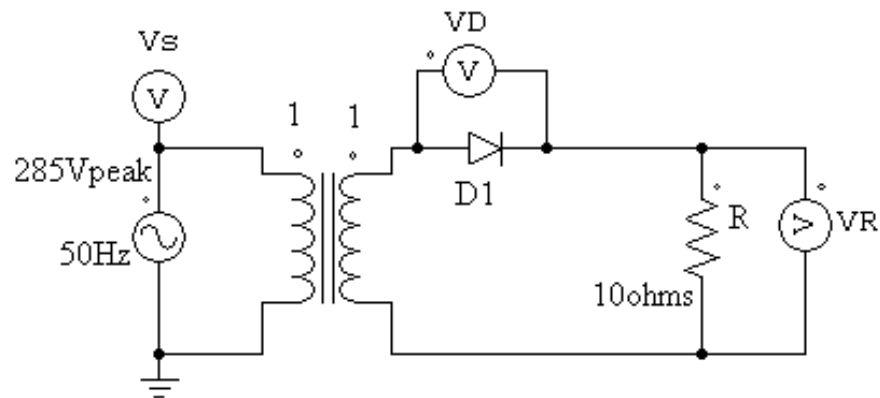

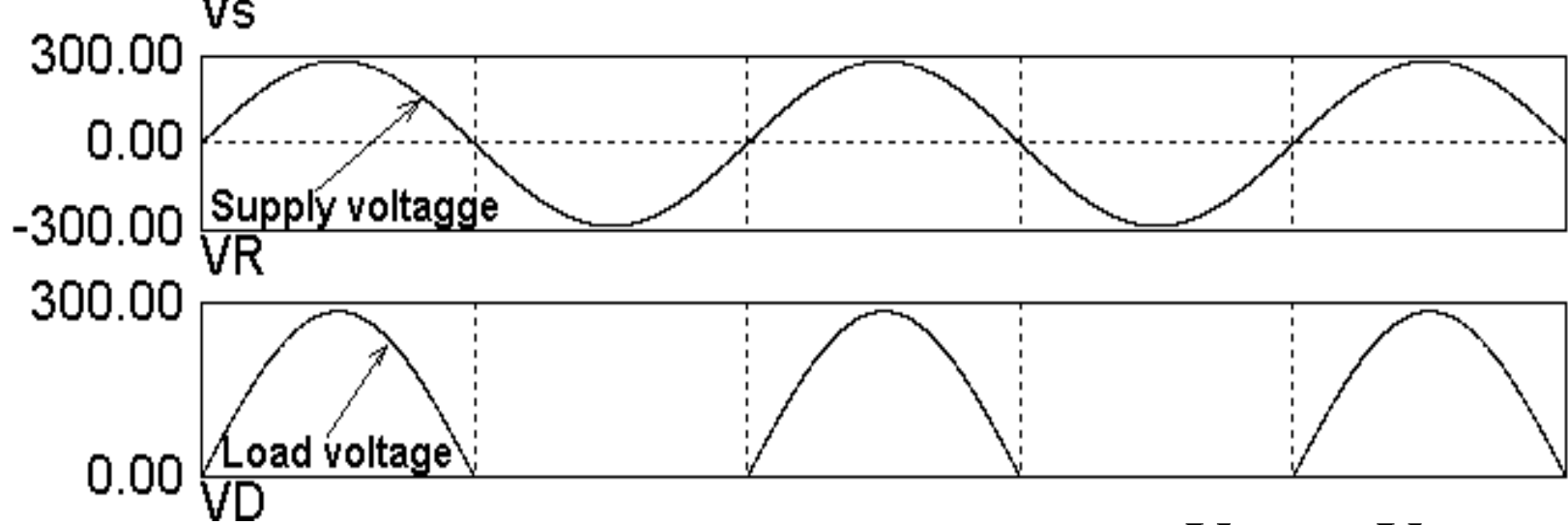

$$V_{dc} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi}$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t \, d\omega t} = \frac{V_m}{2}$$


$$I_{rms} = \frac{V_{rms}}{R} = \frac{V_m}{2R}$$

the load and diode currents

$$I_S = I_D = \frac{V_m}{2R}$$

Half-wave Rectifier Simulation

PartSim Simulation Client

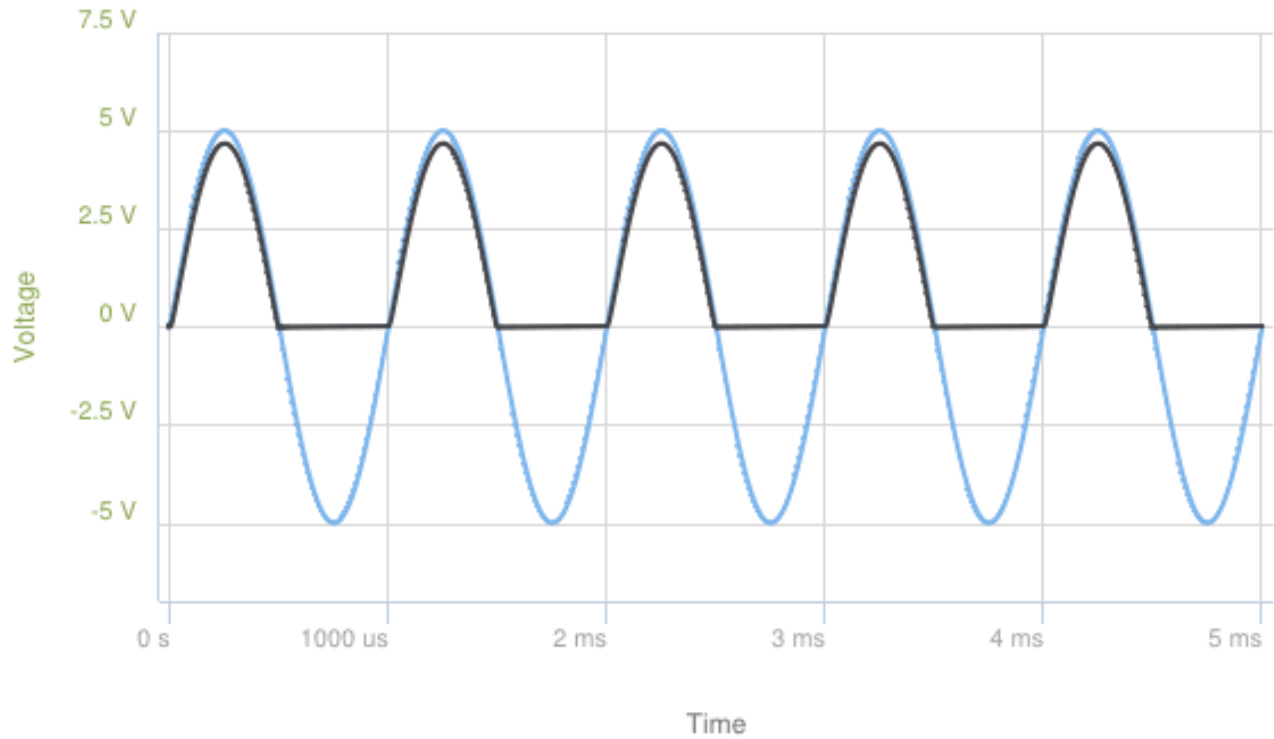

The main disadvantages of half wave rectifier are:

- High ripple factor,**
- Low rectification efficiency,**
- Low transformer utilization factor,**
and,
- DC saturation of transformer secondary winding.**

Example 1: The rectifier shown in Fig. has a pure resistive load of R . Determine (a) The efficiency, (b) Form factor (c) Ripple factor (d) Peak inverse voltage (PIV) of diode D1.

$$V_{dc} = \frac{1}{2\pi} \int_0^{\pi} V_m \sin(\omega t) d\omega t = \frac{V_m}{2\pi} (-\cos \pi - \cos(0)) = \frac{V_m}{\pi} \quad I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2} = \frac{V_m}{2} \quad I_{rms} = \frac{V_m}{2R}$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} * I_{dc}}{V_{rms} * I_{rms}} = \frac{\frac{V_m}{\pi} * \frac{V_m}{\pi R}}{\frac{V_m}{2} * \frac{V_m}{2R}} = 40.53\%$$

$$FF = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_m}{2}}{\frac{V_m}{\pi}} = \frac{\pi}{2} = 1.57$$

$$RF = \frac{V_{ac}}{V_{dc}} = \sqrt{FF^2 - 1} = \sqrt{1.57^2 - 1} = 1.211$$



(d) It is clear from Fig. that the PIV is V_m

Consider the half-wave rectifier circuit of with a resistive load of 25Ω and a 60 Hz ac source of 110 V rms.

- (a) Calculate the average values of v_o and i_o .
- (b) Calculate the rms values of v_o and i_o .
- (c) Calculate the average power delivered to the load.

$$\begin{aligned} V_o &= \frac{V_s}{\pi} & I_o &= \frac{V_o}{R} & P_o &= \frac{V_{o,\text{rms}}^2}{R} \\ &= 49.52 \text{ V} & &= 1.98 \text{ A} & &= 242 \text{ W} \end{aligned}$$

Half Wave Diode Rectifier With R-L Load

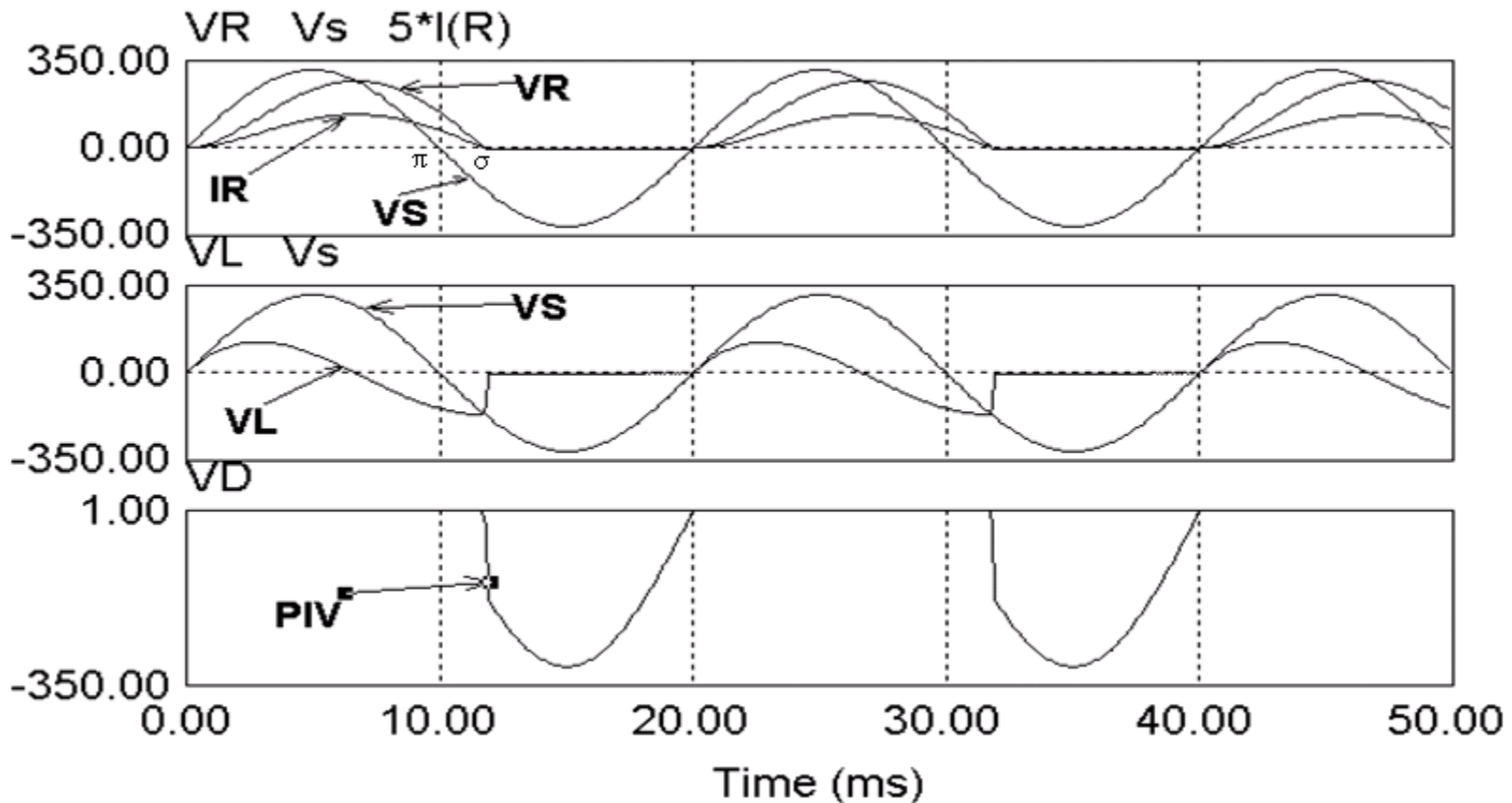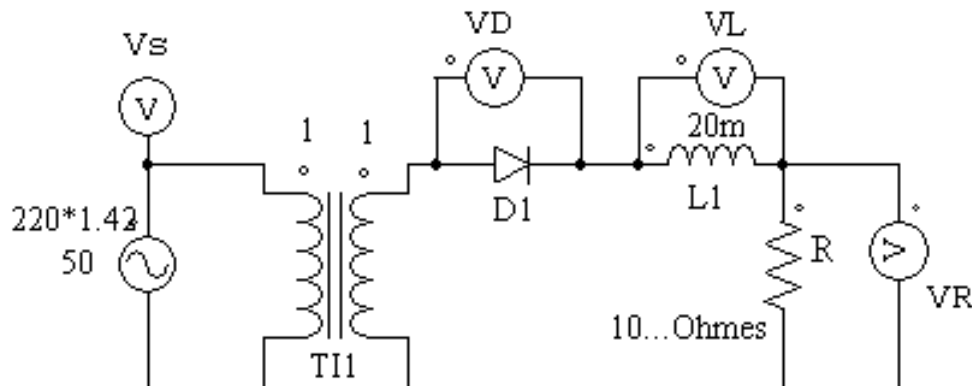

- The operation of the circuit is as follows:
- As in the case of a resistive load, the diode turns on when its anode is positive w.r.t its cathode, and the forward voltage is greater than the threshold voltage.
- Assuming a turn-on voltage of zero volts, the voltage across the load is the same as the positive half cycle of the ac source.

During the interval 0 to $\Pi/2$

- The source voltage v_s increases from zero to its positive maximum, while the voltage across the inductor v_L opposes the change of current through the load.
- It must be noted that the current through an inductor cannot change instantaneously, hence the current gradually increases until it reaches its maximum value.
- The current does not reach its peak when the voltage is at its maximum, which is consistent with the fact that the current through an inductor lags the voltage across it.
- During this time, energy is transferred from the ac source and is stored in the magnetic field of the inductor.

For the interval $\Pi/2$ and Π

- The source voltage decreases from its positive maximum to zero. The induced voltage in the inductor reverses polarity and opposes the associated decrease in current, thereby aiding the diode forward current.
- Therefore, the current starts decreasing gradually at a delayed time, becoming zero when all the energy stored by the inductor is released to the circuit. Again this is consistent with the fact that current lags voltage in an inductive circuit. Hence, even after the source voltage has dropped past zero volts, there is still load current, which exists a little more than half a cycle.

For the interval greater than Π

- At θ , the source voltage reverses and starts to increase to its negative maximum. However, the voltage induced across the inductor is still positive and will sustain forward conduction of the diode until this induced voltage decreases to zero. When this induced voltage falls to zero, the diode will now be reversed biased, but would have conducted forward current for an angle θ , where $\theta = \Pi + \sigma$. σ is the extended angle of current conduction due to the energy stored in the magnetic field being returned to the source.


$$V_{dc} = \frac{V_m}{2\pi} * \int_0^{\beta} \sin \omega t \, d\omega t = \frac{V_m}{2\pi} * (1 - \cos \beta)$$

Where, $\beta = (\pi + \sigma)$

$$V_{rms} = \sqrt{\frac{1}{2\pi} * \int_0^{\beta} (V_m \sin \omega t)^2 \, d\omega t} = \frac{V_m}{2\sqrt{\pi}} * \sqrt{\beta + 0.5(1 - \sin(2\beta))}$$

Single-Phase Full-Wave Diode Rectifier

Center-Tap Diode Rectifier

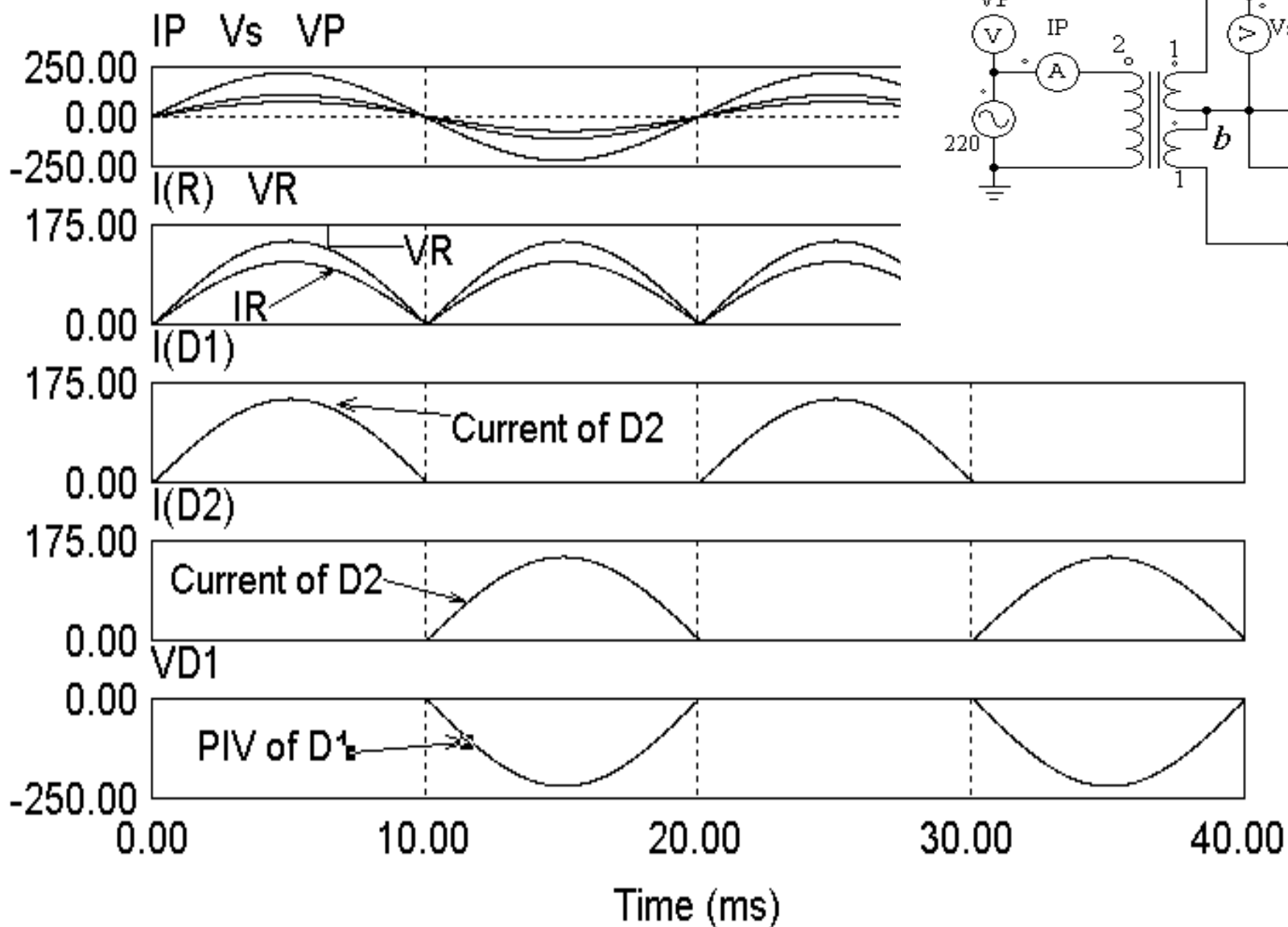

$$V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi}$$

$$I_{dc} = \frac{2V_m}{\pi R}$$

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (V_m \sin \omega t)^2 \, d\omega t} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{V_m}{\sqrt{2} R}$$

$$\text{PIV of each diode} = 2V_m$$

$$I_S = I_D = \frac{V_m}{2R}$$


Example 3. The rectifier in Fig.2.8 has a purely resistive load of R . Determine (a) The efficiency, (b) Form factor (c) Ripple factor (d) TUF (e) Peak inverse voltage (PIV) of diode D1

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} * I_{dc}}{V_{rms} * I_{rms}} = \frac{\frac{2 V_m}{\pi} * \frac{2 V_m}{\pi R}}{\frac{V_m}{\sqrt{2}} * \frac{V_m}{\sqrt{2} R}} = 81.05\%$$


$$FF = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_m}{\sqrt{2}}}{\frac{2 V_m}{\pi}} = \frac{\pi}{2 \sqrt{2}} = 1.11$$

$$RF = \frac{V_{ac}}{V_{dc}} = \sqrt{FF^2 - 1} = \sqrt{1.11^2 - 1} = 0.483$$


The PIV is $2V_m$

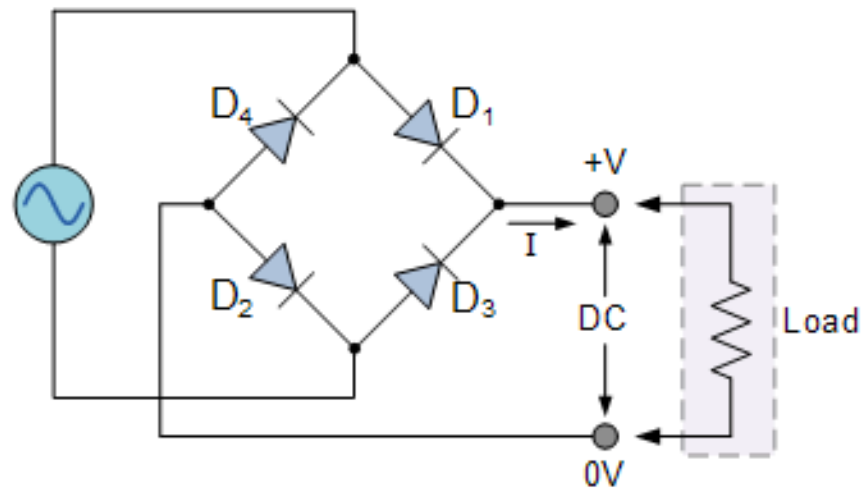



Positive Half-cycle

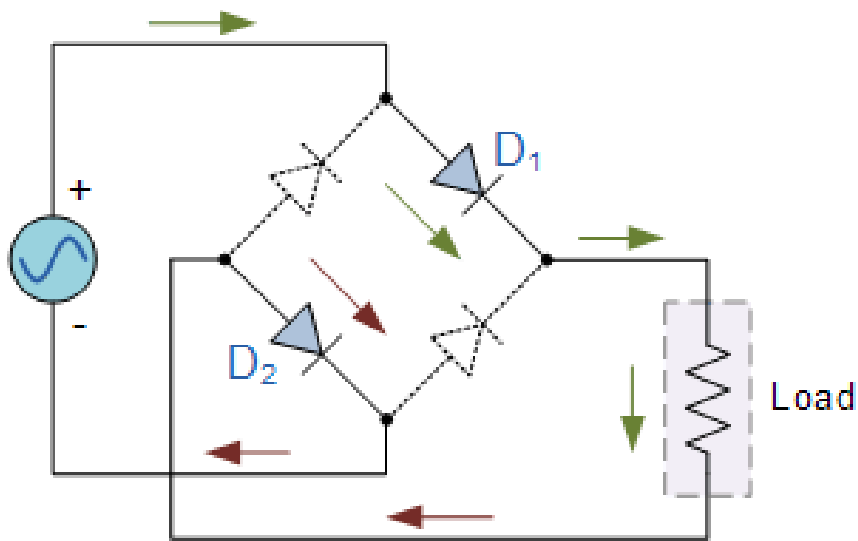



Negative Half-cycle

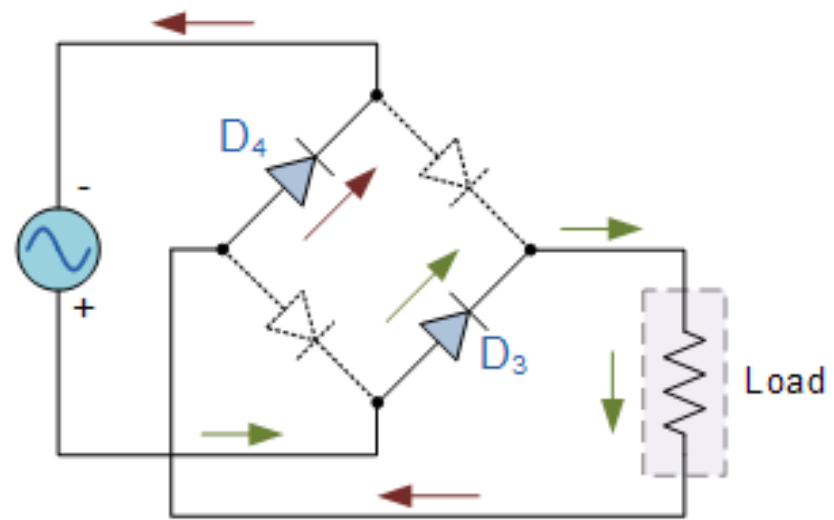

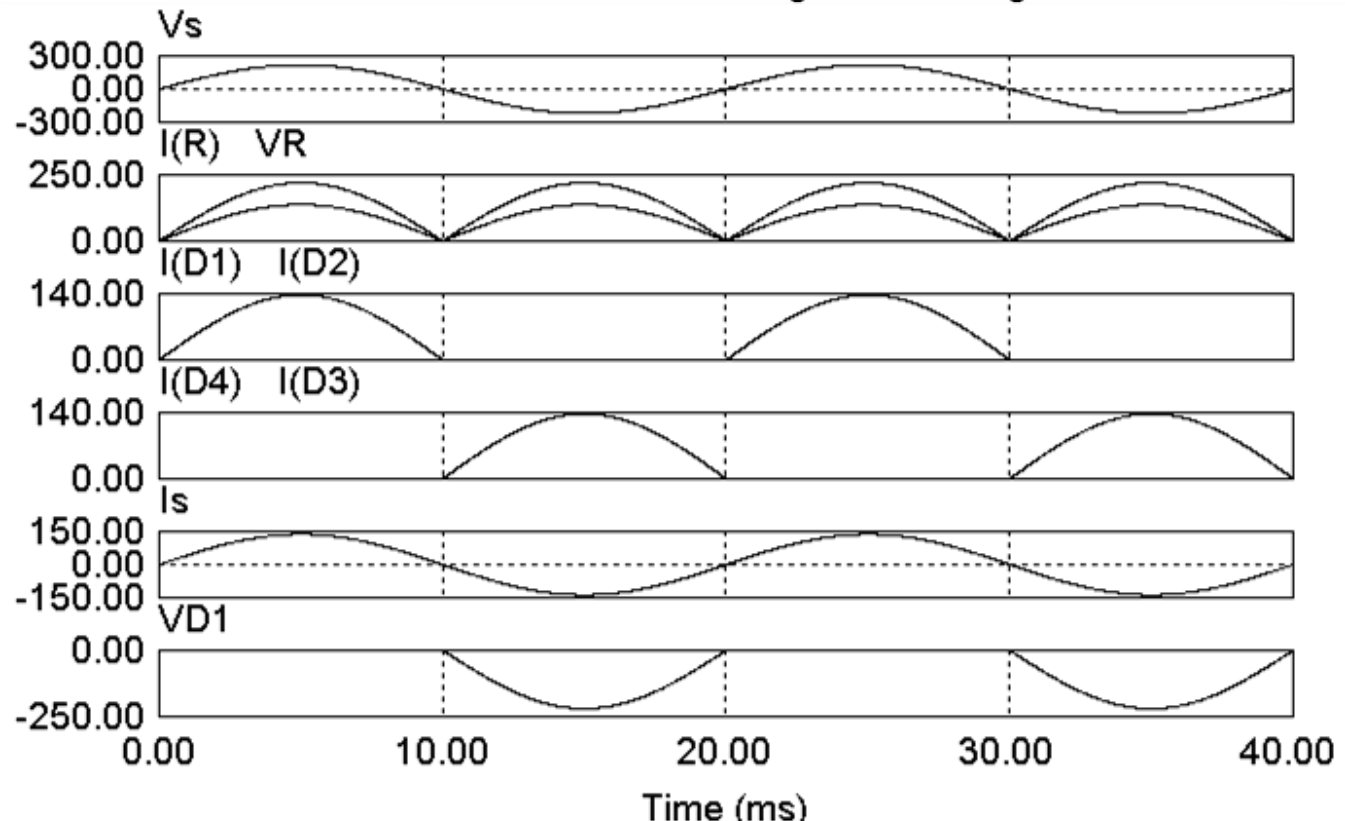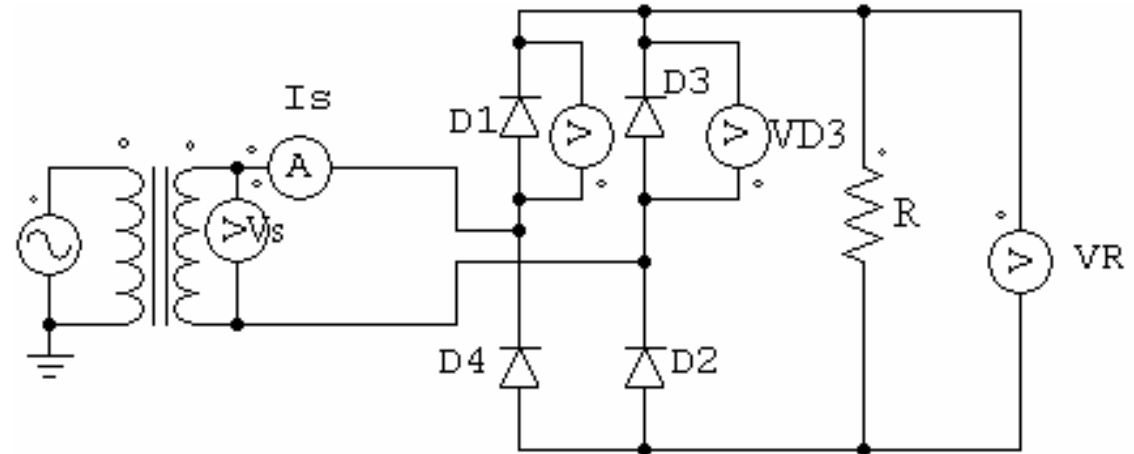Single-Phase Full Bridge Diode Rectifier With Resistive Load



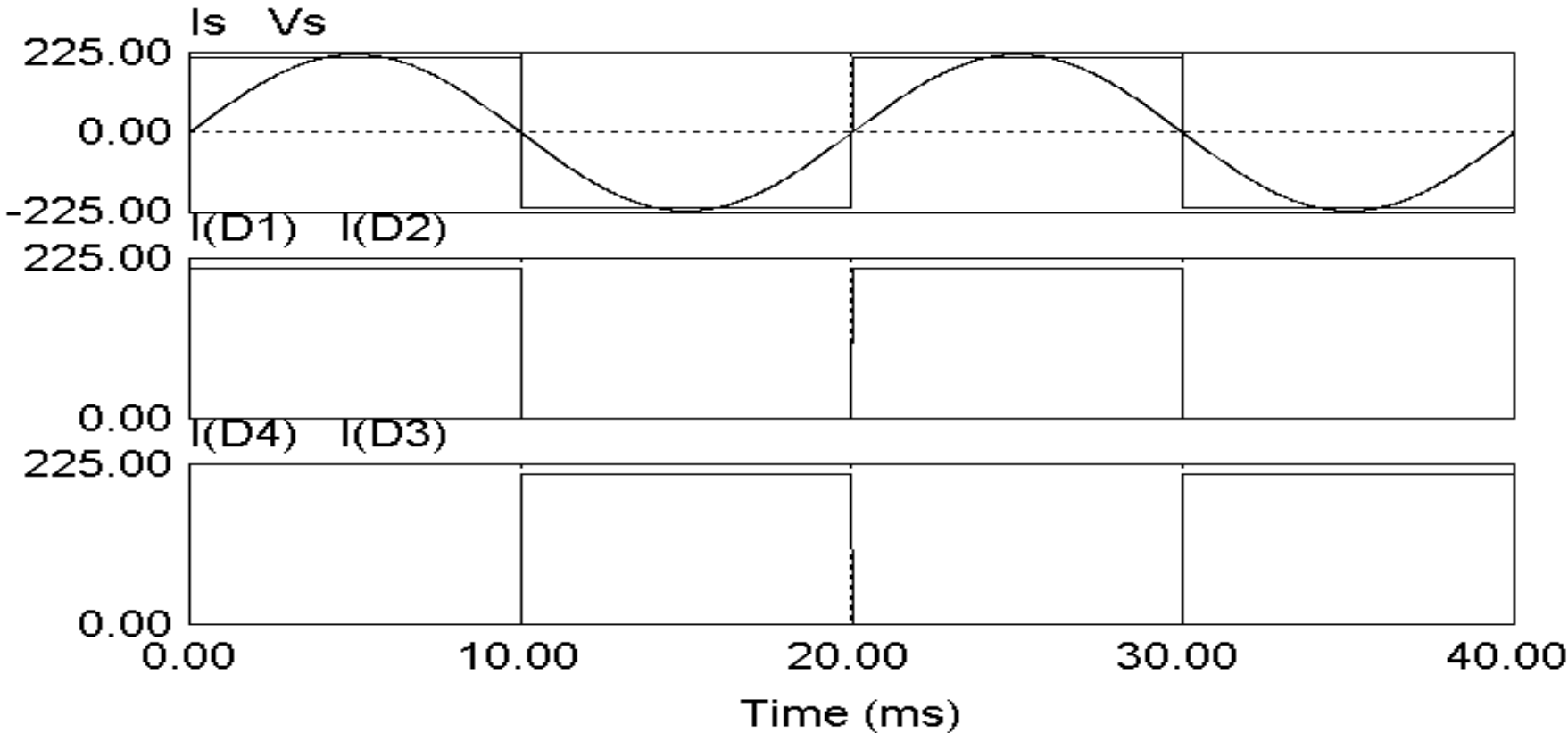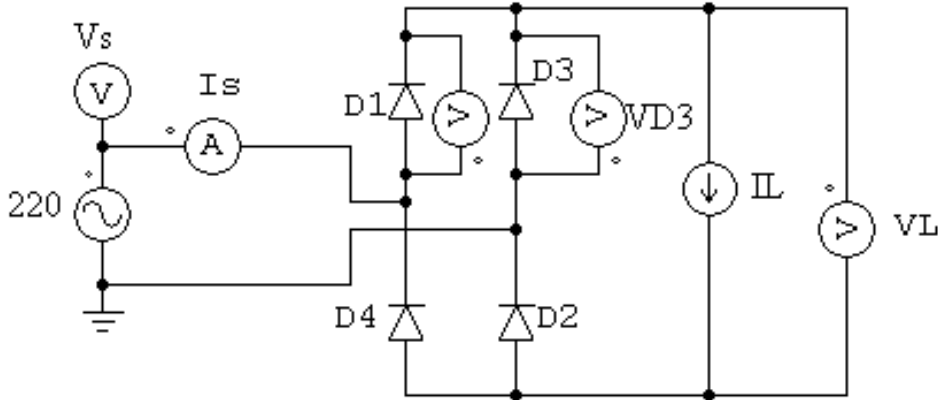Full Bridge Single-phase Diode Rectifier with DC Load Current




The Full Wave Bridge Rectifier

This type of single phase rectifier uses four individual rectifying diodes connected in a closed loop “bridge” configuration to produce the desired output.



The main advantage of this bridge circuit is that it does not require a special centre tapped transformer, thereby reducing its size and cost. The single secondary winding is connected to one side of the diode bridge network and the load to the other side as shown below.


COMPARISON OF SINGLE PHASE RECTIFIER



Sr. No.	Parameters	Half-wave	Full-wave	
			Centre-tap	Bridge
1	DC output Voltage, V_o	V_m/π	$2V_m/\pi$	$2V_m/\pi$
2	Rms value of output Voltage, V_{or}	$V_m/2$	$V_m/1.41$	$V_m/1.41$
3	Ripple Voltage, V_r	$0.3856 V_m$	$0.3077 V_m$	$0.3077 V_m$
4	Voltage ripple Factor, VRF	1.211	0.482	0.482
5	Efficiency	40.53%	81.06%	81.06%
6	TUF	0.2865	0.672	0.8106
7	PIV	V_m	$2V_m$	V_m
8	Number of Diode	1	2	4
9	Ripple frequency	f	2f	2f




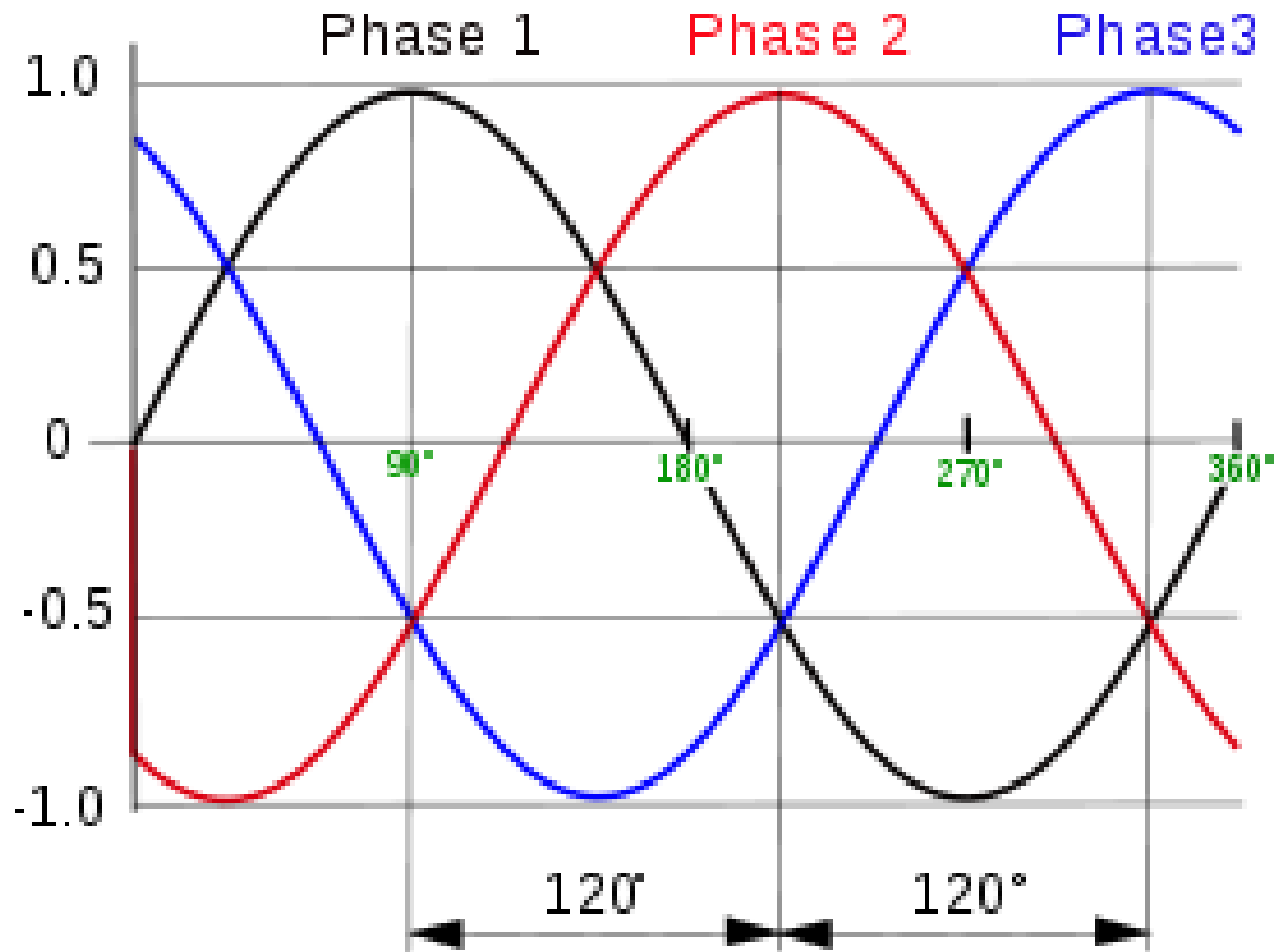




Three-Phase Half Wave Rectifier

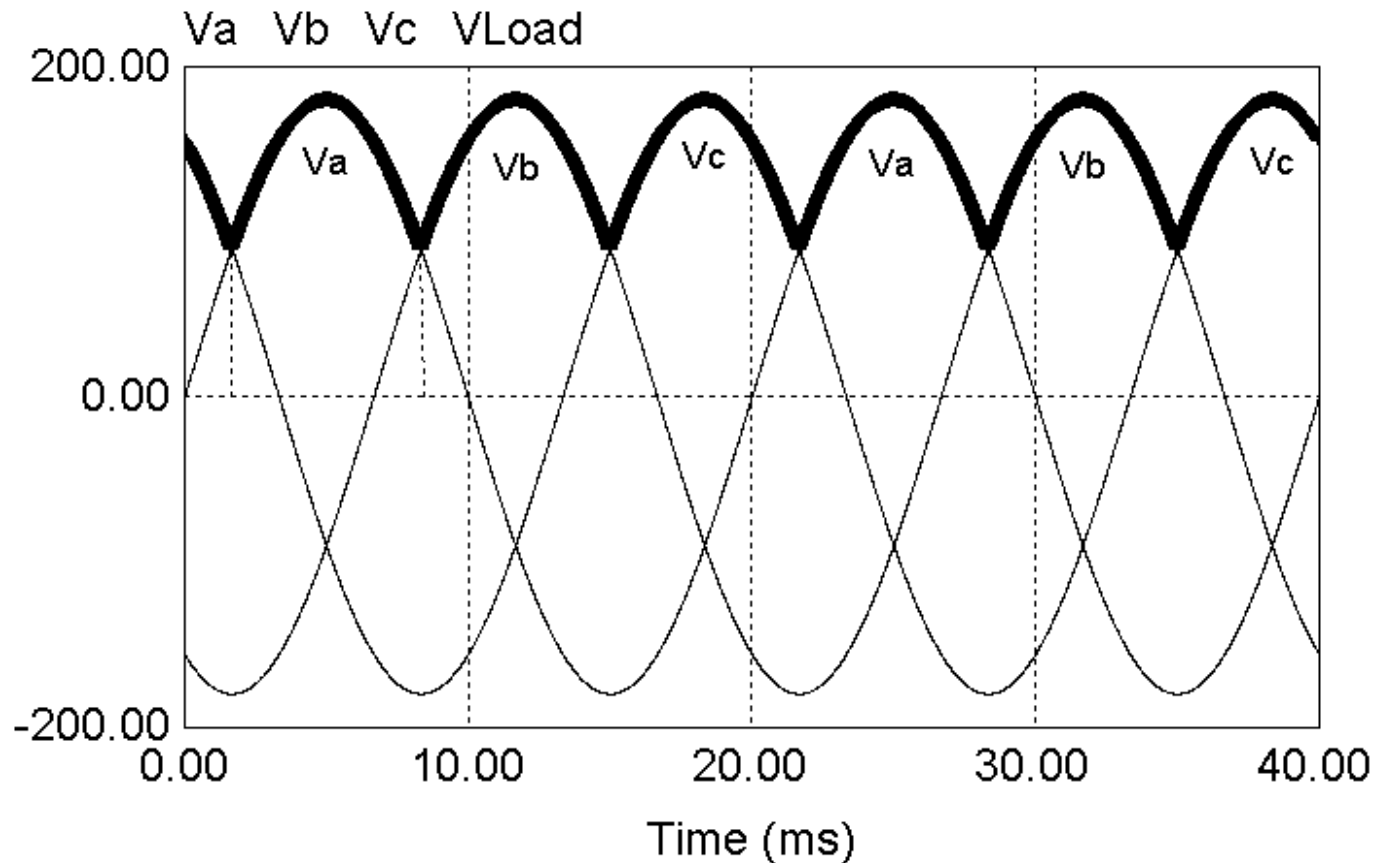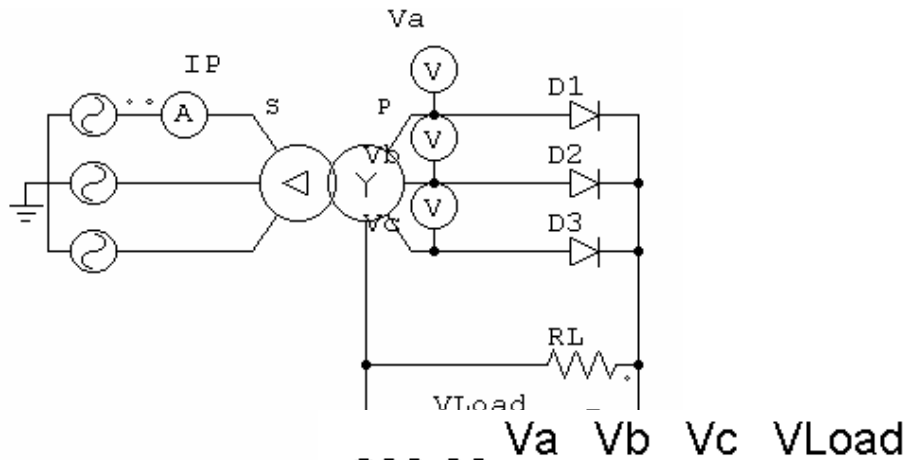

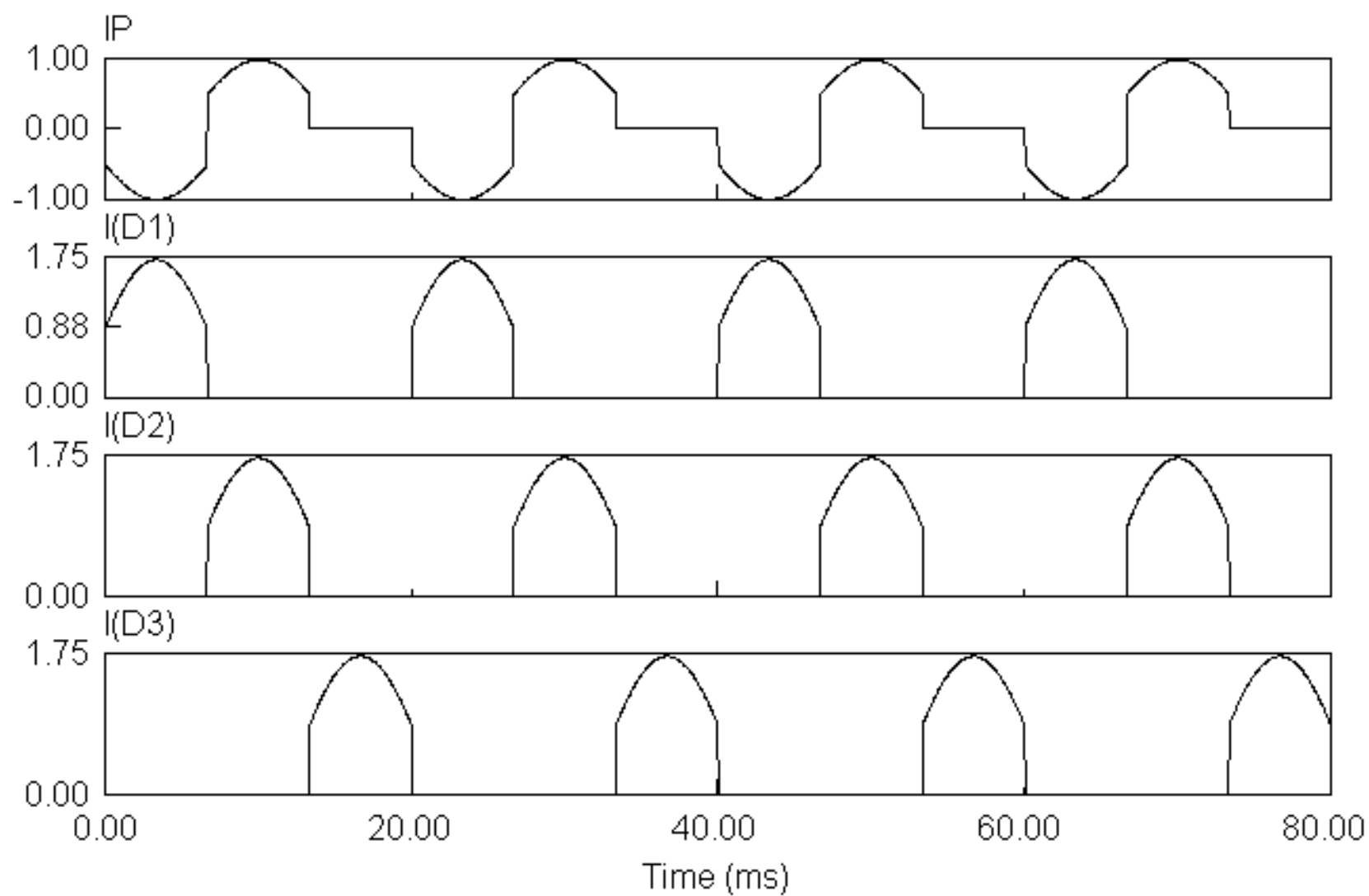


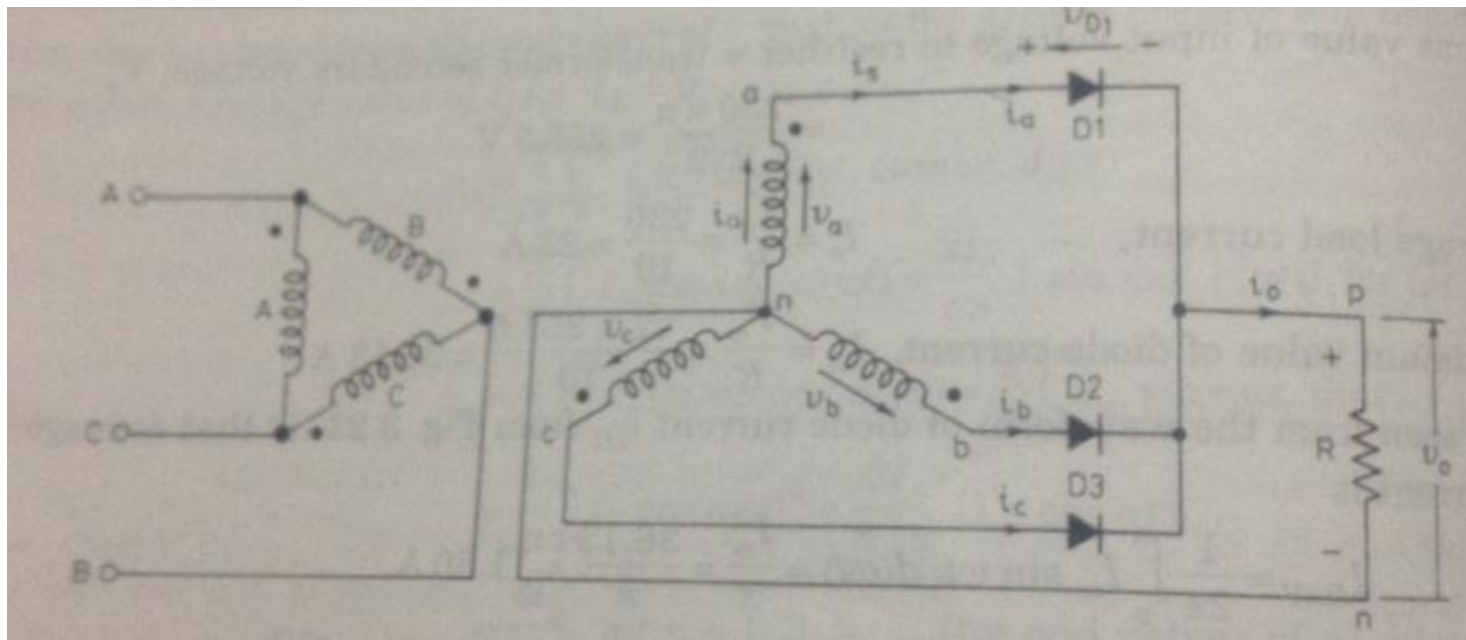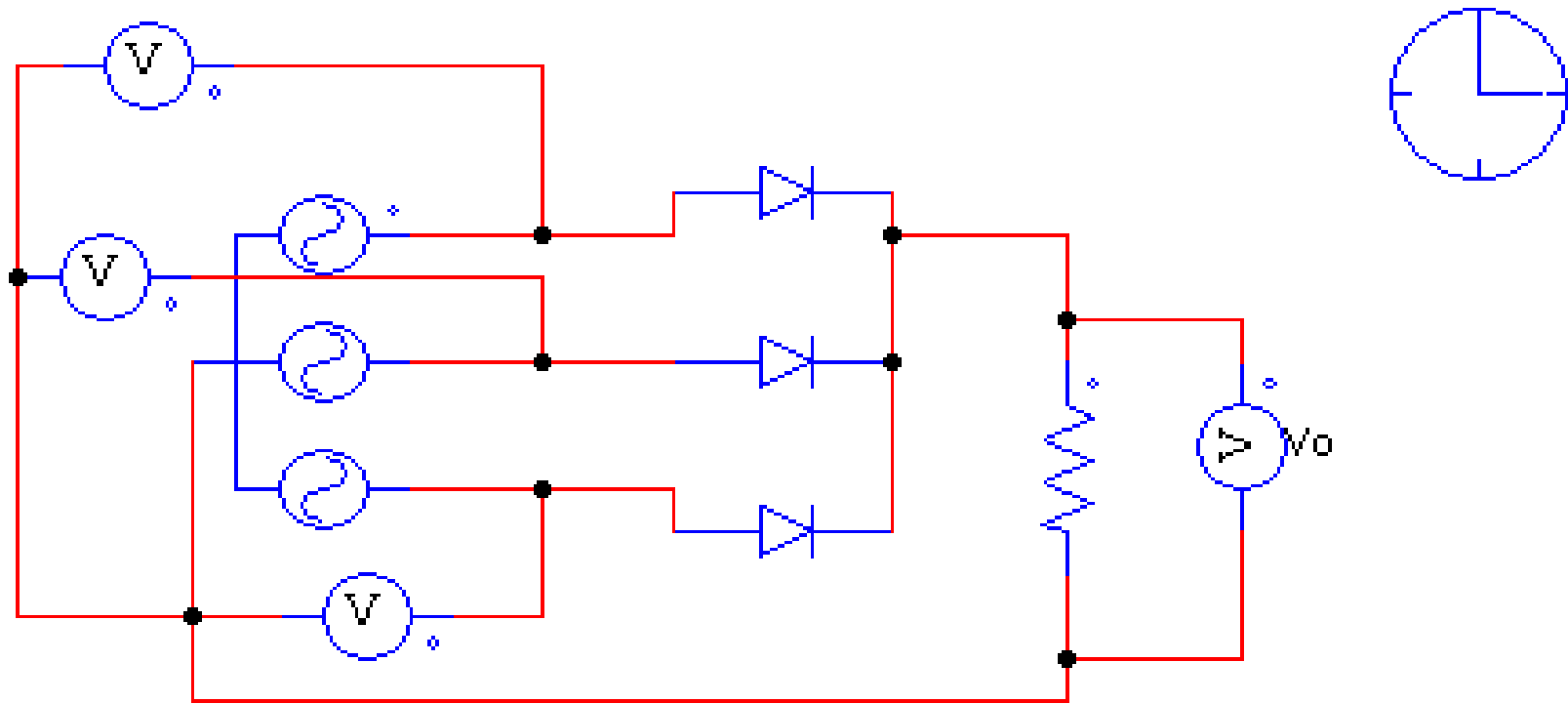

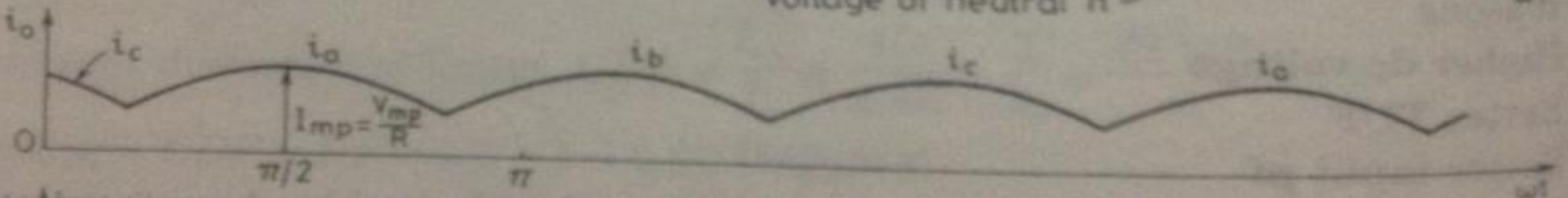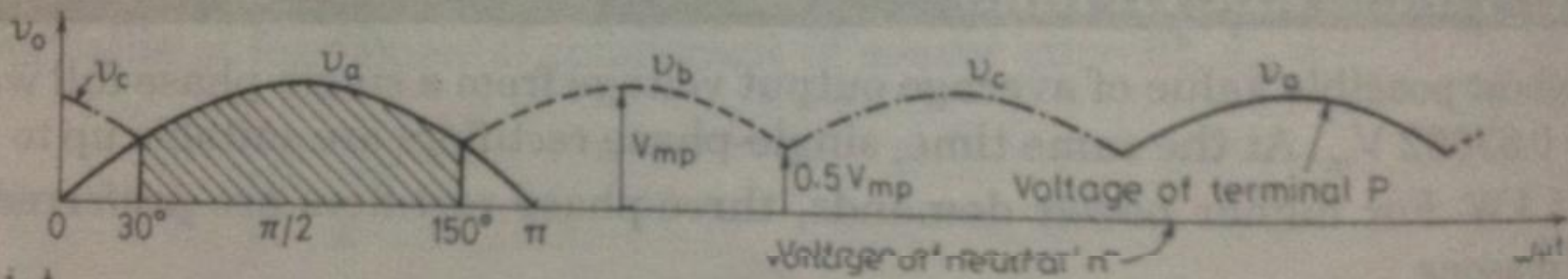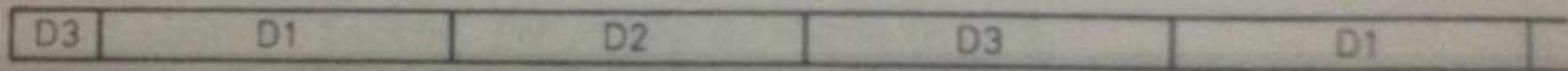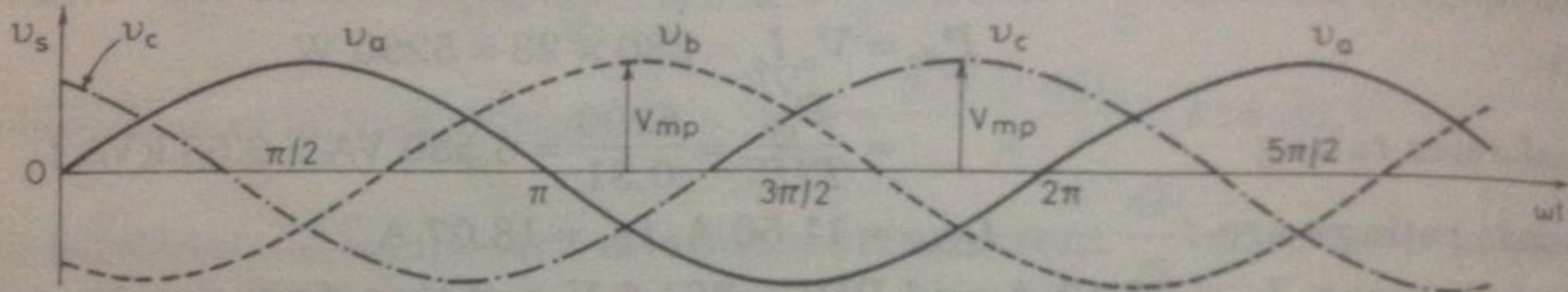


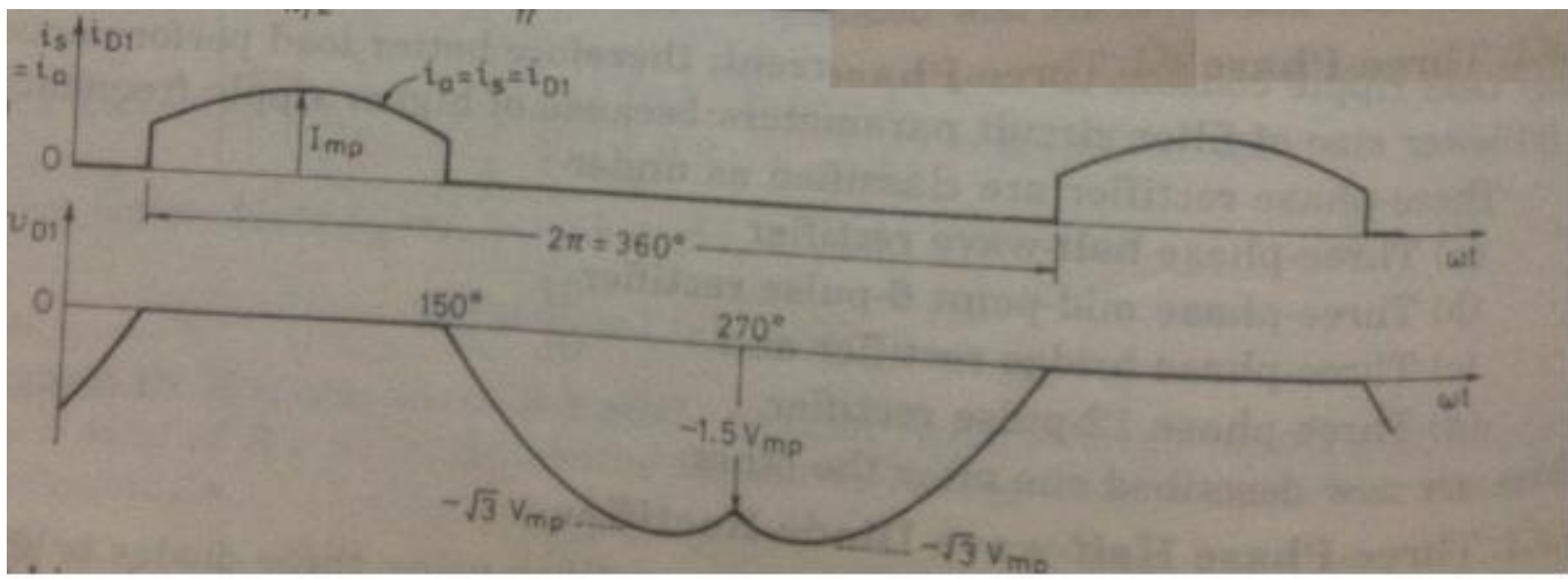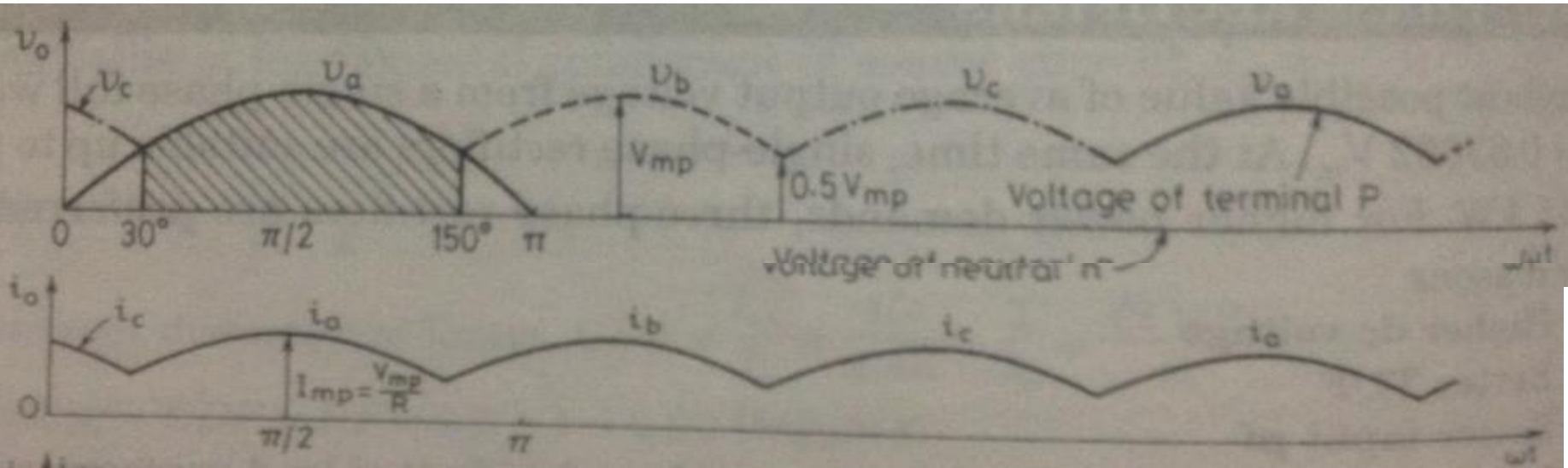

VR VY VB Vo

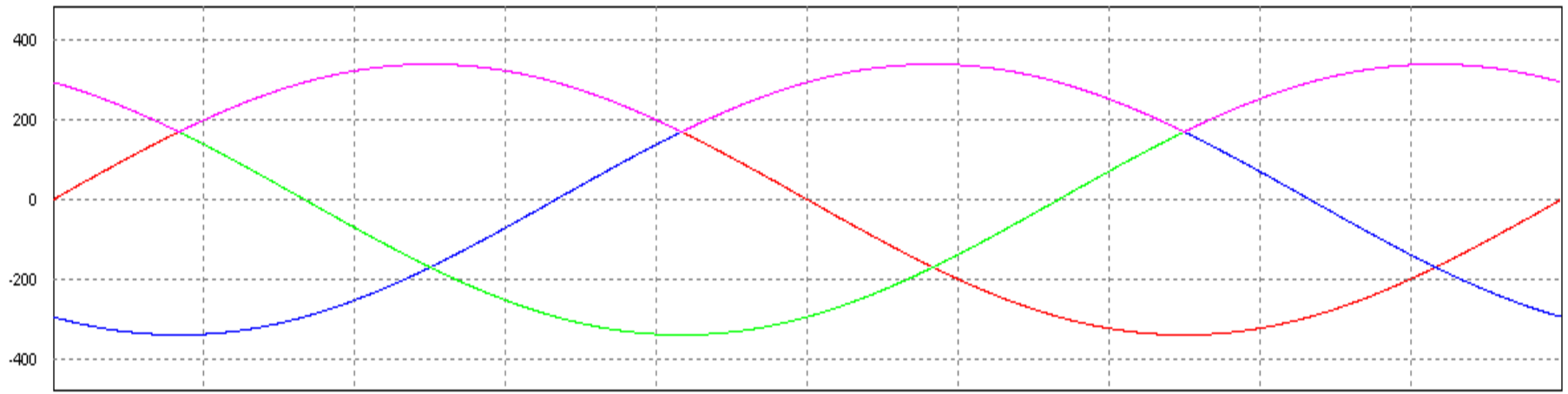

Vo

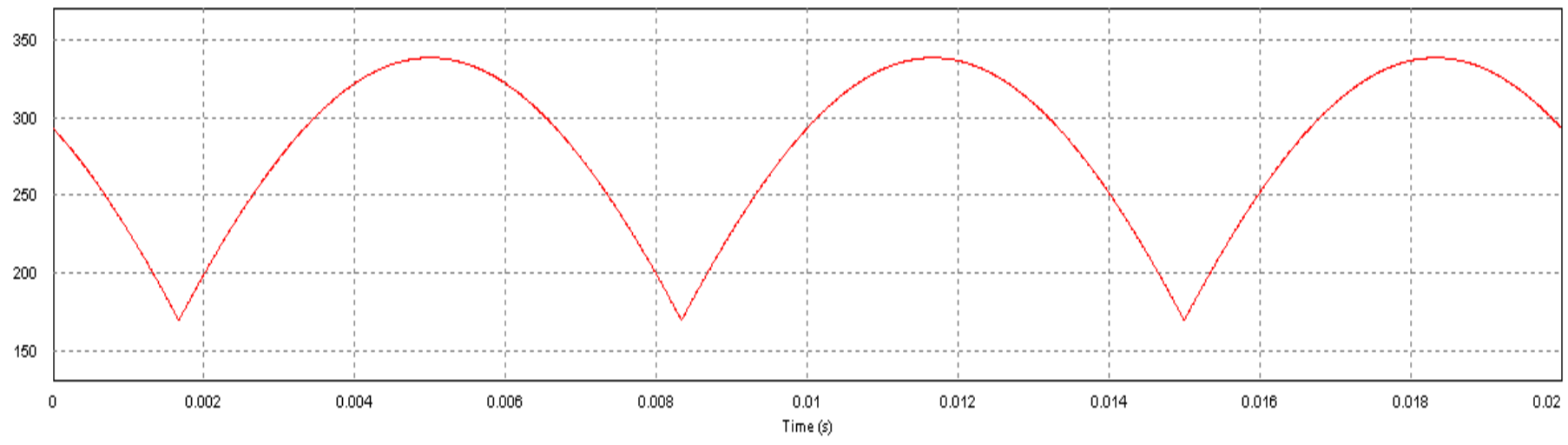


$$V_{dc} = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_m \sin \omega t \, d\omega t = \frac{3\sqrt{3} V_m}{2\pi} = 0.827V_m \quad I_{dc} = \frac{3\sqrt{3} V_m}{2 * \pi * R} = \frac{0.827 * V_m}{R}$$

$$V_{rms} = \sqrt{\frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} (V_m \sin \omega t)^2 \, d\omega t} = \sqrt{\frac{1}{2} + \frac{3 * \sqrt{3}}{8 \pi}} V_m = 0.8407 V_m$$

$$I_{rms} = \frac{0.8407 V_m}{R} \quad I_r = I_S = \frac{0.8407 V_m}{R \sqrt{3}} = 0.4854 \frac{V_m}{R}$$

The PIV of the diodes is $= \sqrt{3} V_m$

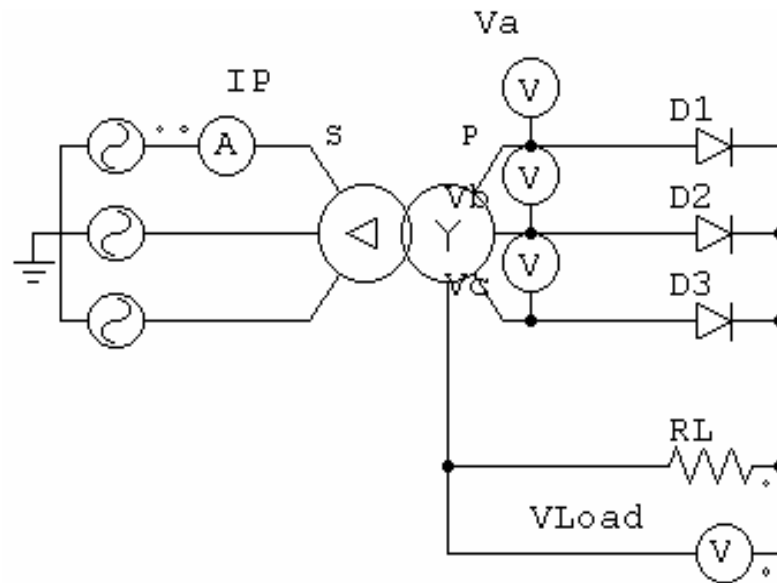Example 7 The rectifier in below is operated from 460 V 50 Hz supply at secondary side and the load Ω resistance is $R=20$. If the source inductance is negligible, determine (a) Rectification efficiency, (b) Form factor (c) Ripple factor (d) Peak inverse voltage (PIV) of each diode.



$$V_S = \frac{460}{\sqrt{3}} = 265.58 \text{ V}, \quad V_m = 265.58 * \sqrt{2} = 375.59 \text{ V}$$

$$V_{dc} = \frac{3\sqrt{3} V_m}{2\pi} = 0.827 V_m \quad I_{dc} = \frac{3\sqrt{3} V_m}{2\pi R} = \frac{0.827 V_m}{R}$$

$$V_{rms} = 0.8407 V_m \quad I_{rms} = \frac{0.8407 V_m}{R}$$


$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{V_{dc} I_{dc}}{V_{rms} I_{rms}} = 96.767 \%$$



$$FF = \frac{V_{rms}}{V_{dc}} = 101.657 \%$$


$$RF = \frac{V_{ac}}{V_{dc}} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \sqrt{\frac{V_{rms}^2}{V_{dc}^2} - 1} = \sqrt{FF^2 - 1} = 18.28 \%$$

$$\text{The PIV} = \sqrt{3} V_m = 650.54 \text{ V}$$


Three-Phase Bridge Rectifier

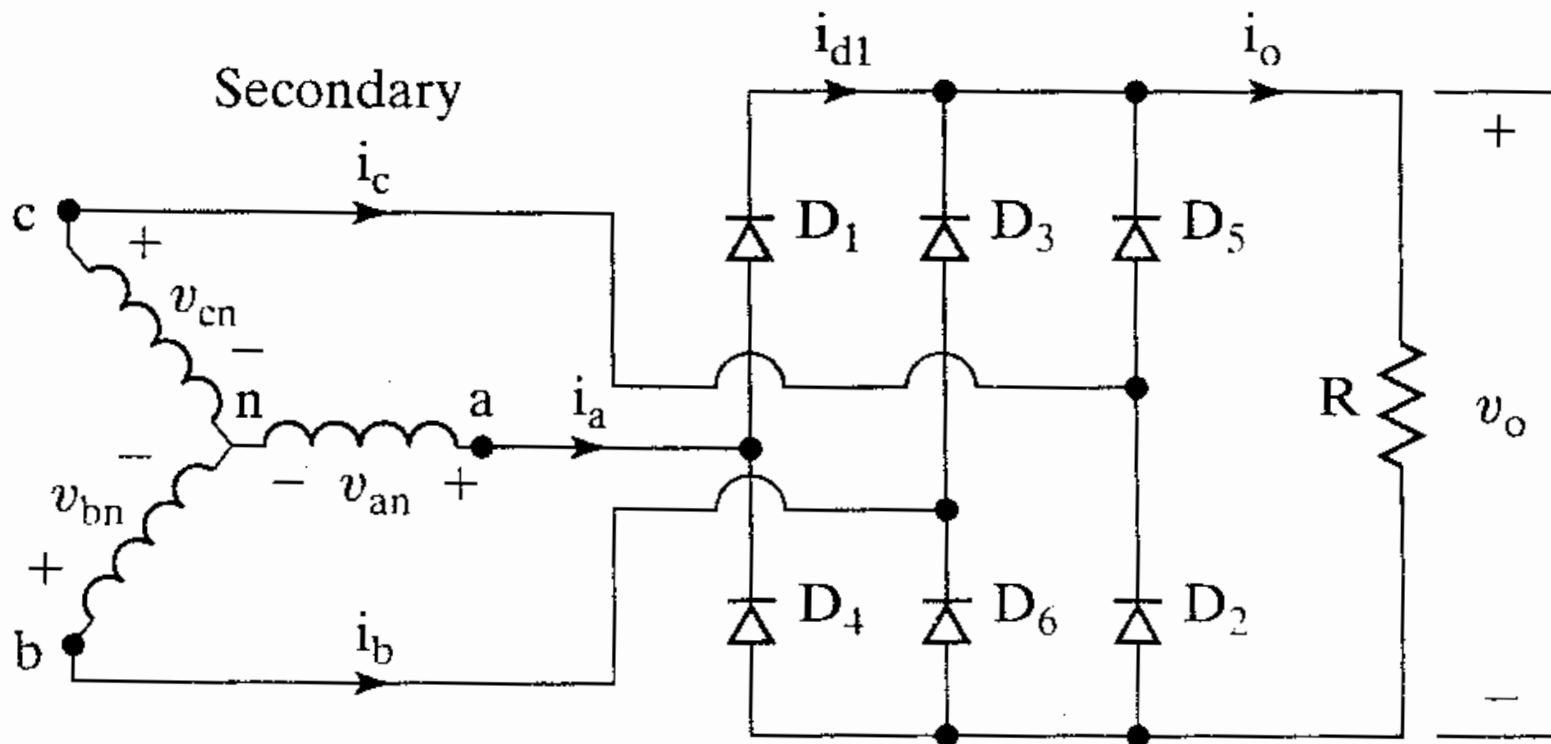

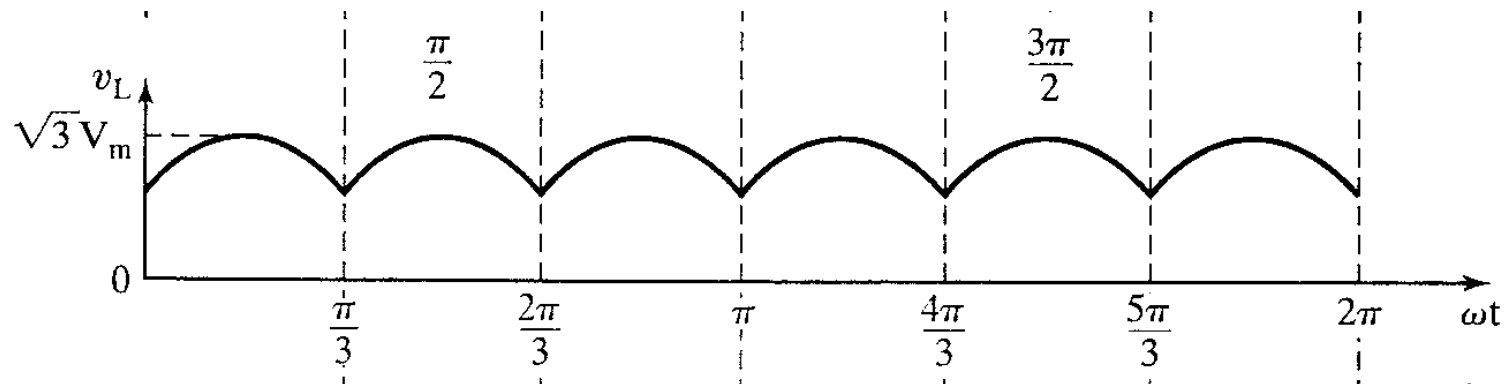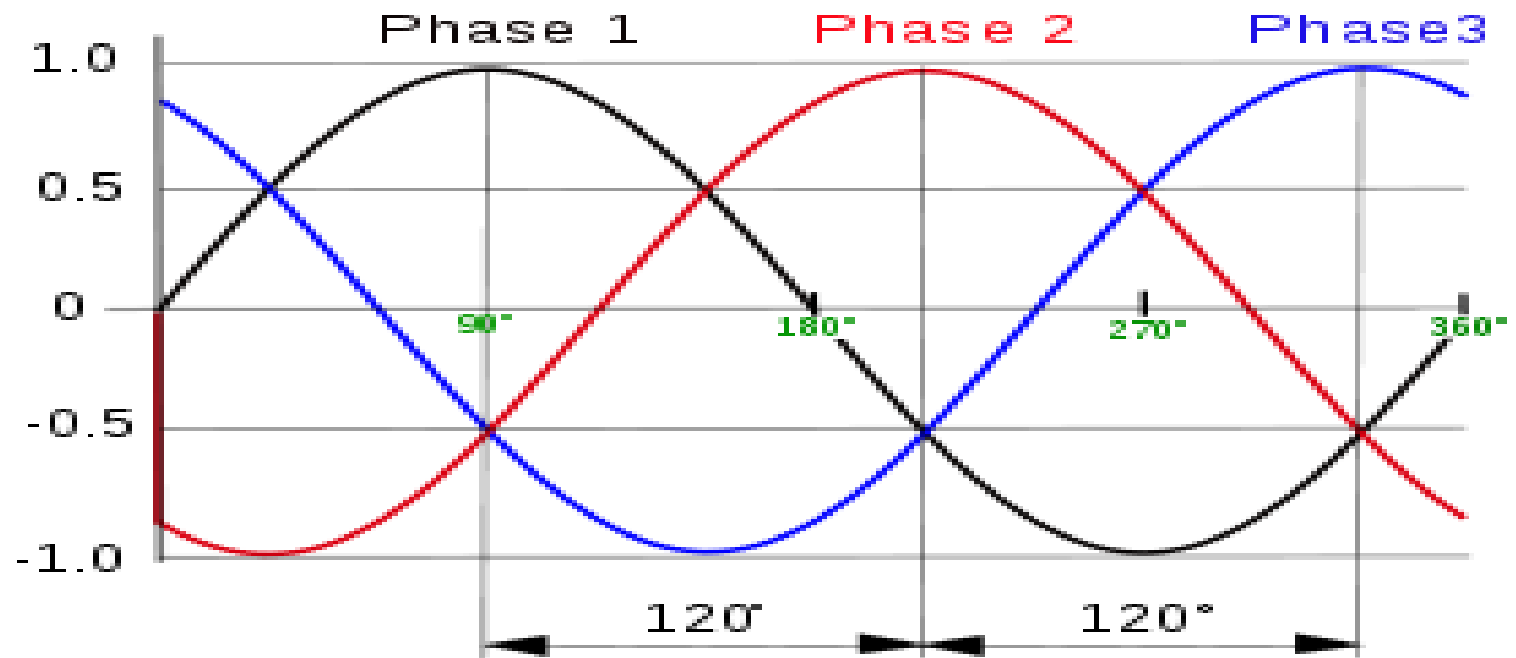

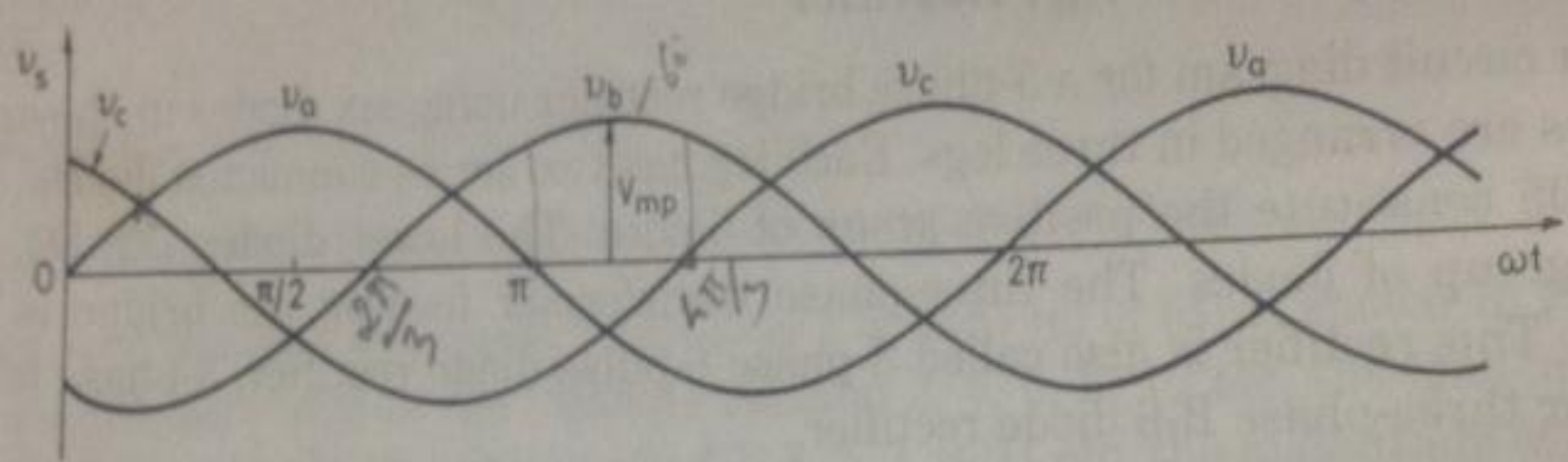

D5	D1	D3	D5	D1 + ve group
D6	D2	D4	D6	D2 - ve group

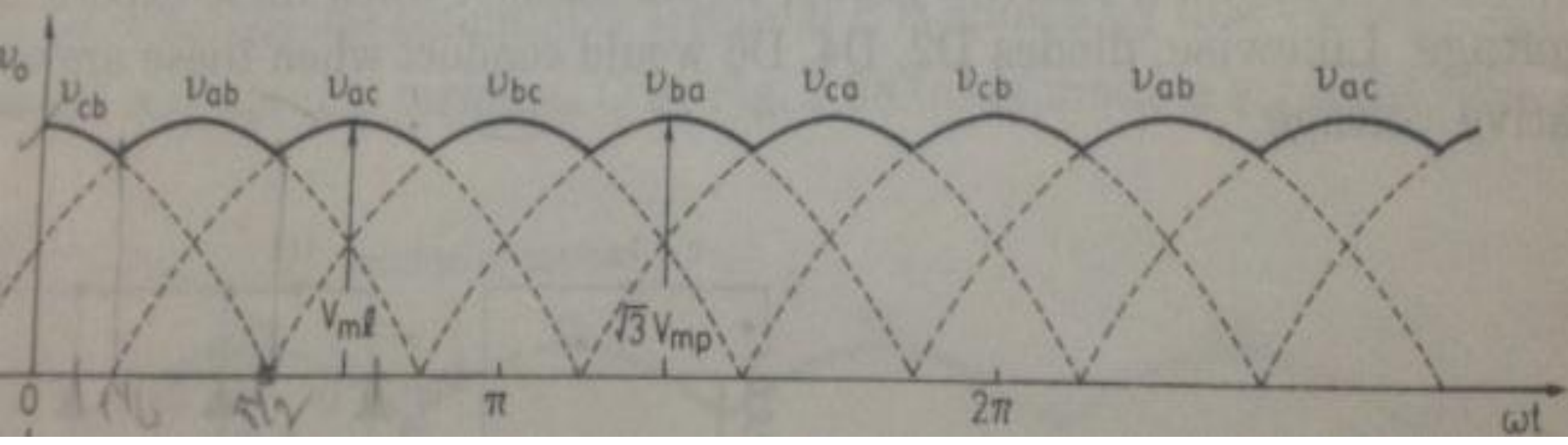

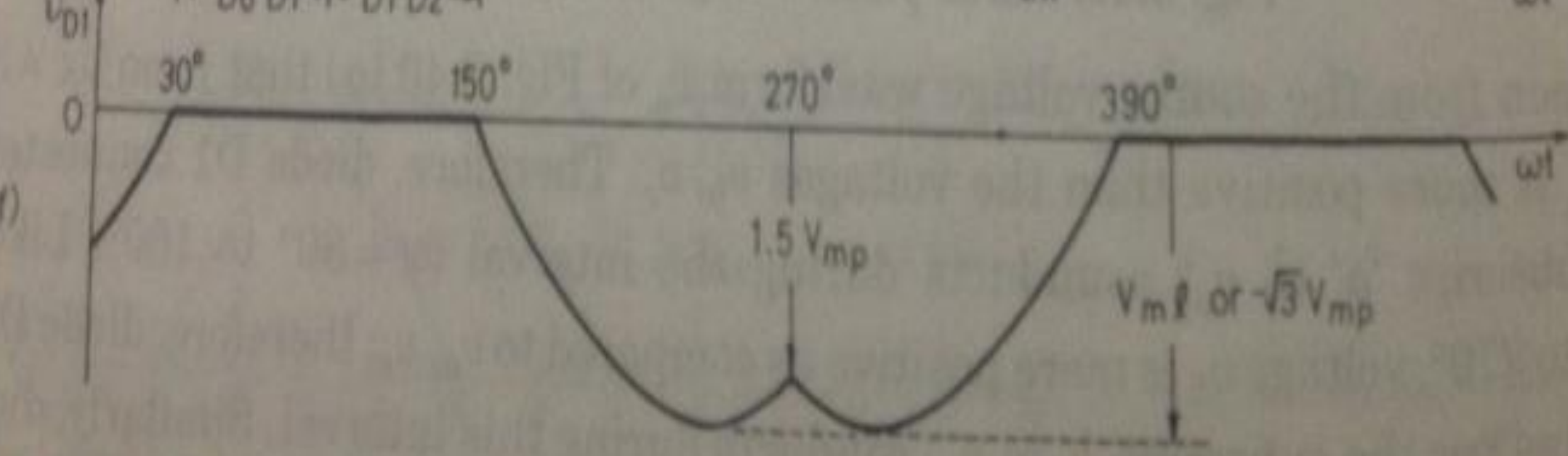
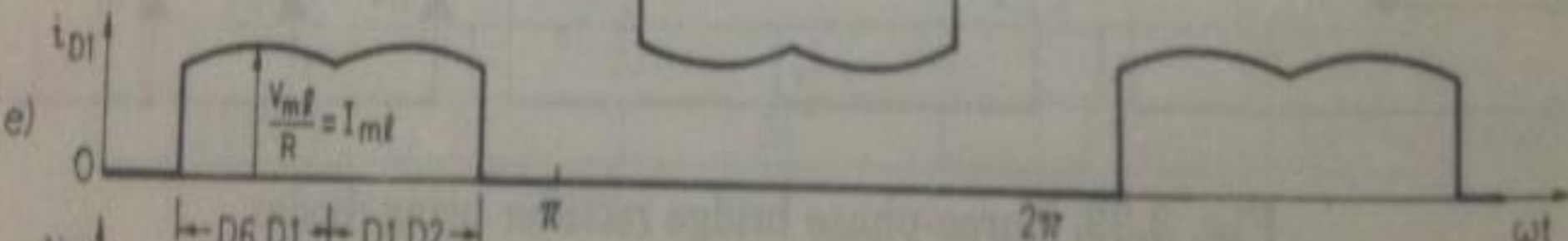
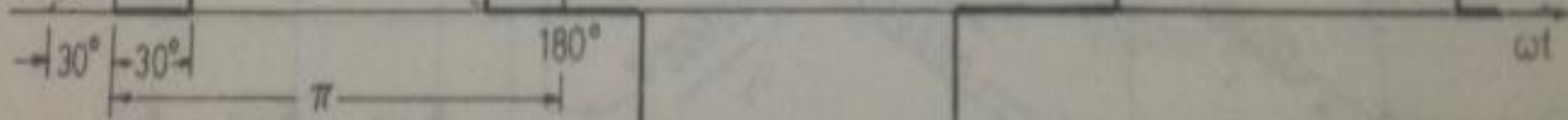
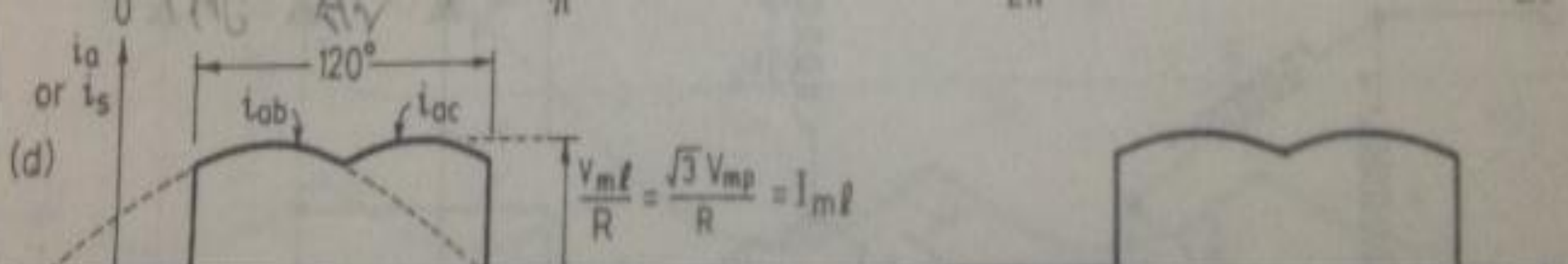


Fig. 9.10 (m)

$$V_o = \frac{1}{\frac{\pi}{3}} \int_{\frac{\pi}{3}}^{\frac{2\pi}{3}} V_{m_{line}} \sin(\omega t) d(\omega t) = \frac{3}{\pi} V_{line} = 0.955 V_{m_{line}}$$

where,

$$V_{m_{phase}} = \sqrt{2} V_{phase}$$

and

$$V_{m_{line}} = \sqrt{3} V_{m_{phase}} = \sqrt{6} V_{phase}$$

The RMS value of the output voltage is given by

$$V_{o_{rms}} = \left[\frac{1}{\frac{\pi}{3}} \int_{\frac{\pi}{3}}^{\frac{2\pi}{3}} (V_{m_{line}} \sin(\omega t))^2 d(\omega t) \right]^{\frac{1}{2}}$$

$$= 0.9588 V_{m_{line}}$$

Ripple voltage,

$$\begin{aligned}V_r &= \sqrt{V_{o_{rms}}^2 - V_o^2} \\&= \sqrt{0.9588^2 - 0.955^2} V_{m_{line}} \\&= 0.0853 V_{m_{line}}\end{aligned}$$

DC output power,

$$\begin{aligned}P_o &= V_o I_o = \frac{3}{\pi} V_{m_{line}} \frac{3}{\pi} I_{m_{line}} \\&= 0.912 V_{m_{line}} I_{m_{line}}\end{aligned}$$


AC input power,

$$\begin{aligned}P_i &= V_{or} I_{or} = (0.9588)^2 V_{m_{line}} I_{m_{line}} \\&= 0.9193 V_{m_{phase}} I_{m_{phase}}\end{aligned}$$

Efficiency,

$$\begin{aligned}\eta &= \frac{P_o}{P_i} = \frac{0.912V_{m_{phase}} I_{m_{phase}}}{0.9193V_{m_{phase}} I_{m_{phase}}} \\ &= 0.992 = 99.2\%\end{aligned}$$

Average Output Voltage, V_{dc}

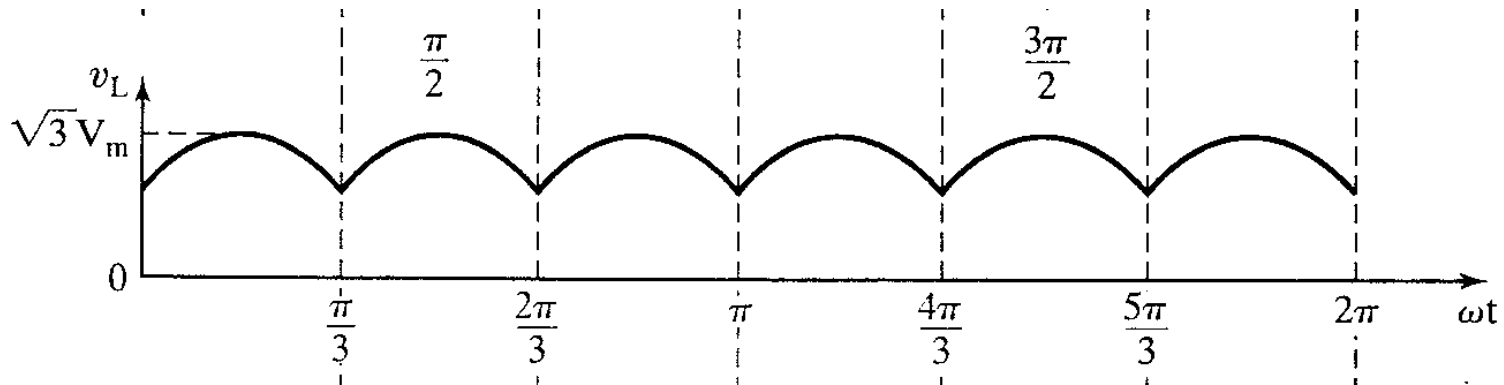

$$V_{dc} = \frac{1}{T} \int_0^T f(t) dt$$

$$V_{dc} = \frac{2}{2\pi} \int_0^{\frac{\pi}{6}} \sqrt{3} V_m \cos \omega t d(\omega t)$$

$$V_{dc} = \frac{3\sqrt{3}}{\pi} V_m = 1.654 V_m$$

rms Output Voltage

$$V_{rms} = \left[\frac{2}{2\pi} \int_0^{\frac{\pi}{6}} 3V_m^2 \cos^2 \omega t d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{rms} = \left(\frac{3}{2} + \frac{9\sqrt{3}}{4\pi} \right)^{\frac{1}{2}} V_m$$


$$V_{rms} = 1.6554V_m$$

Diode Currents


$$I_m = \frac{\sqrt{3}V_m}{R} = \textit{peak}$$

$$I_r = \left[\frac{4}{2\pi} \int_0^{\frac{\pi}{6}} I_m^2 \cos^2 \omega t d(\omega t) \right]^{\frac{1}{2}}$$


$$I_r = 0.5518 I_m$$

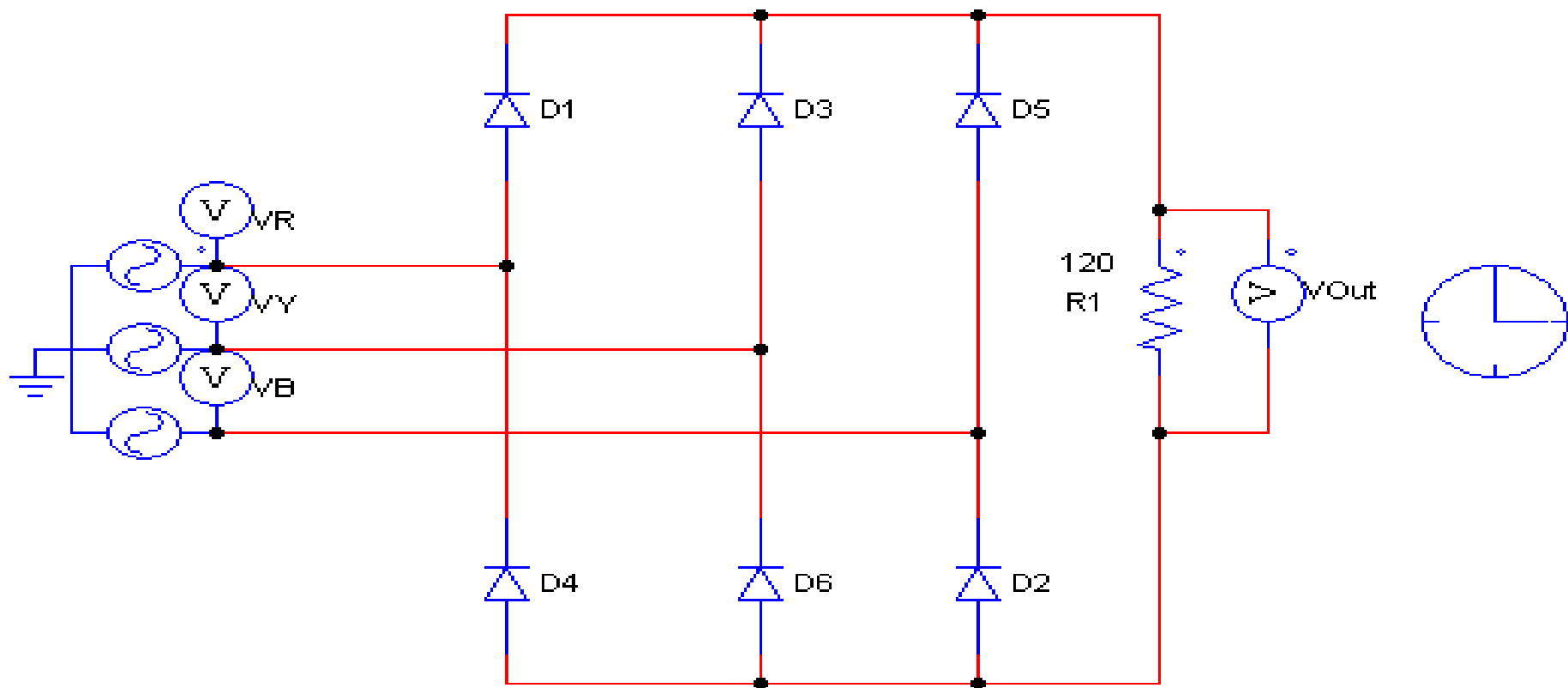


VR VY VB VOut

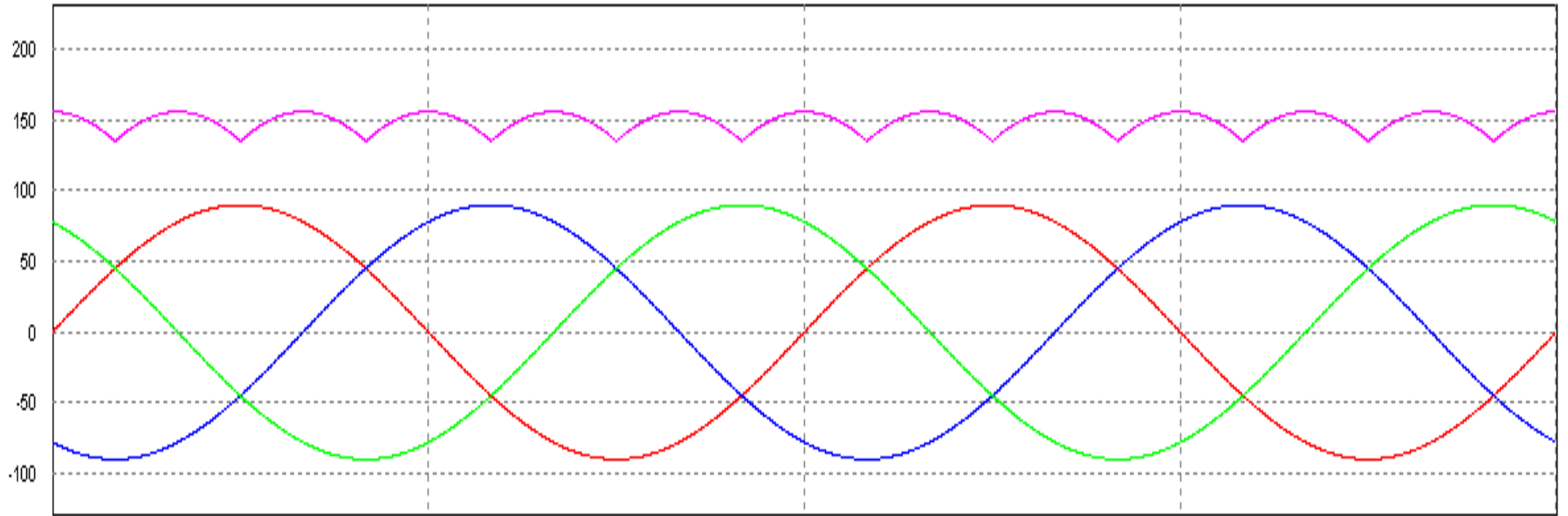


VOut

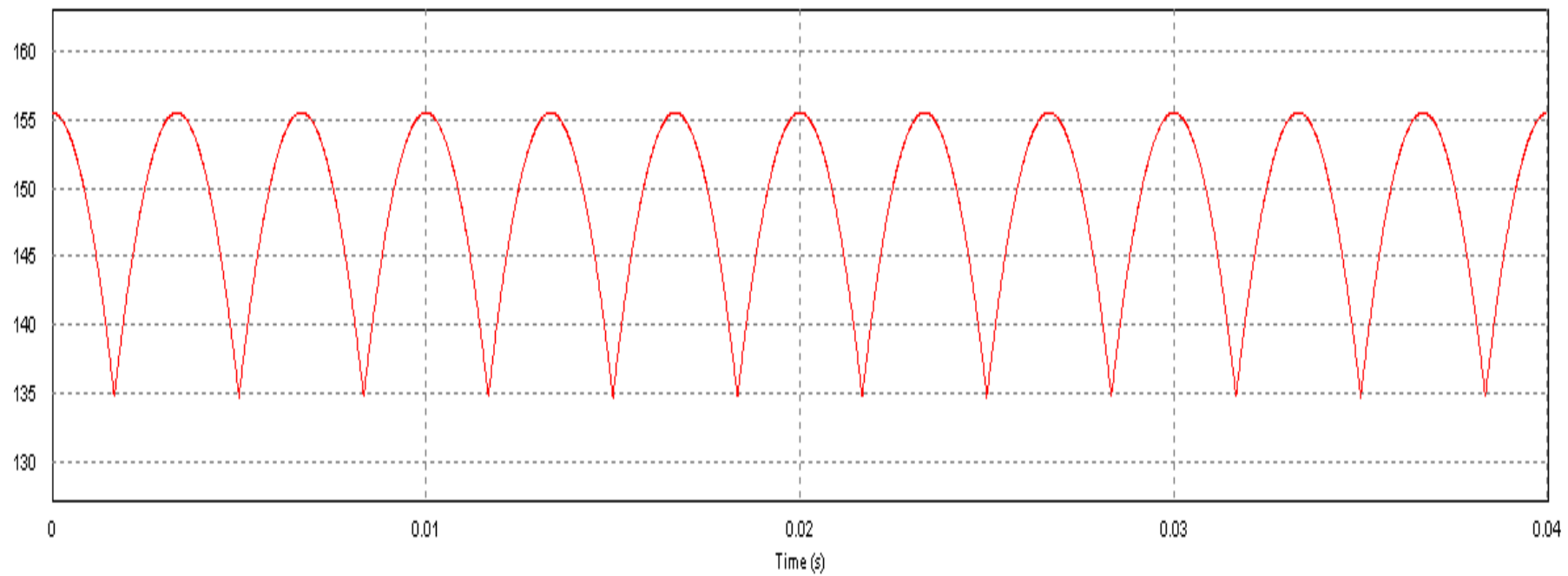


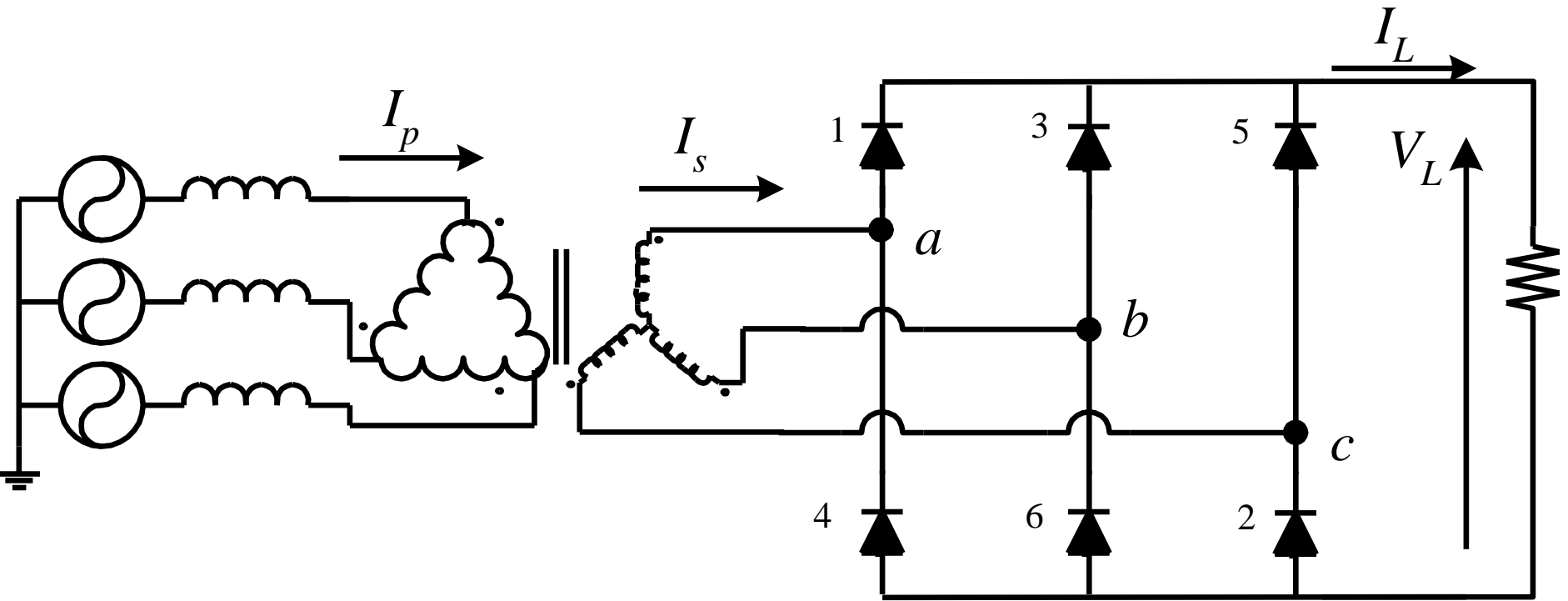Three-Phase Full Wave Rectifier With Resistive Load



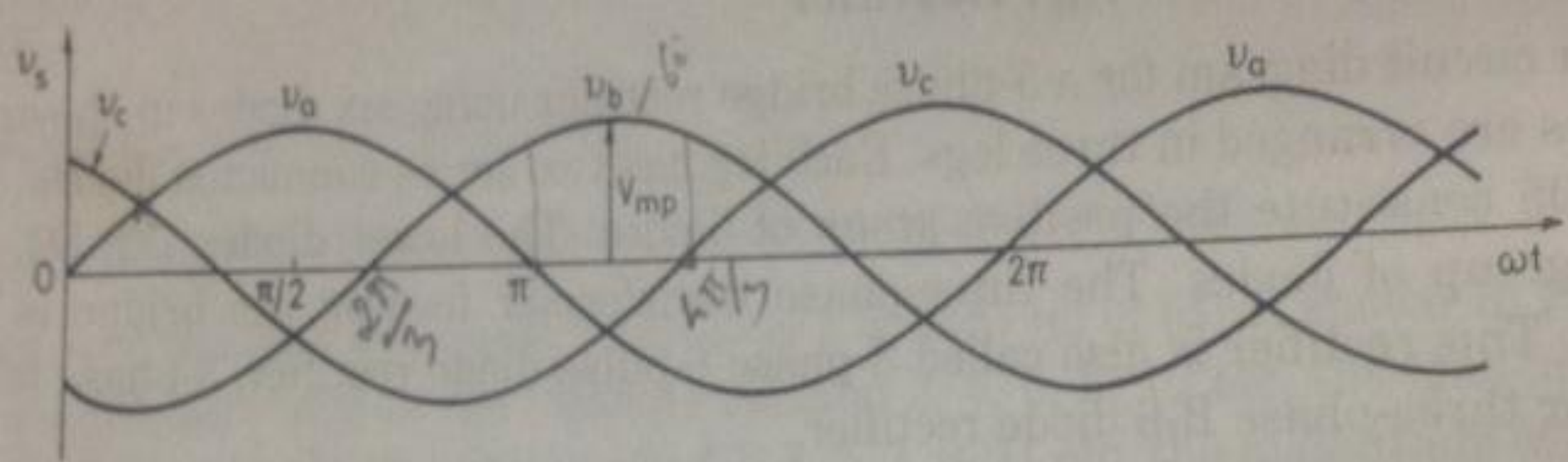

D5	D1	D3	D5	D1 +ve group
D6	D2	D4	D6	D2 -ve group

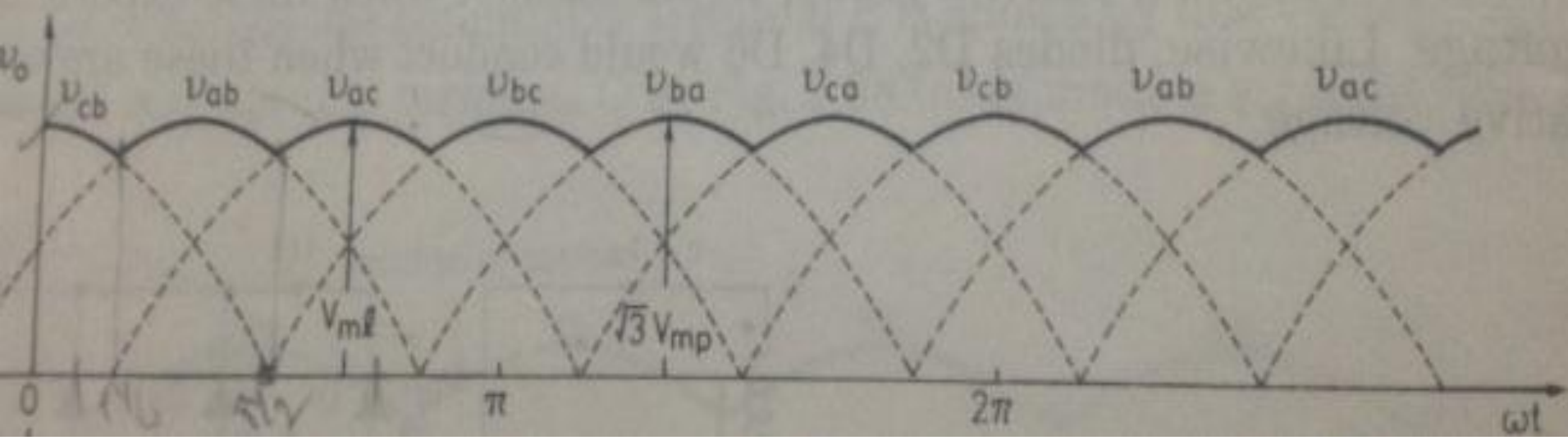



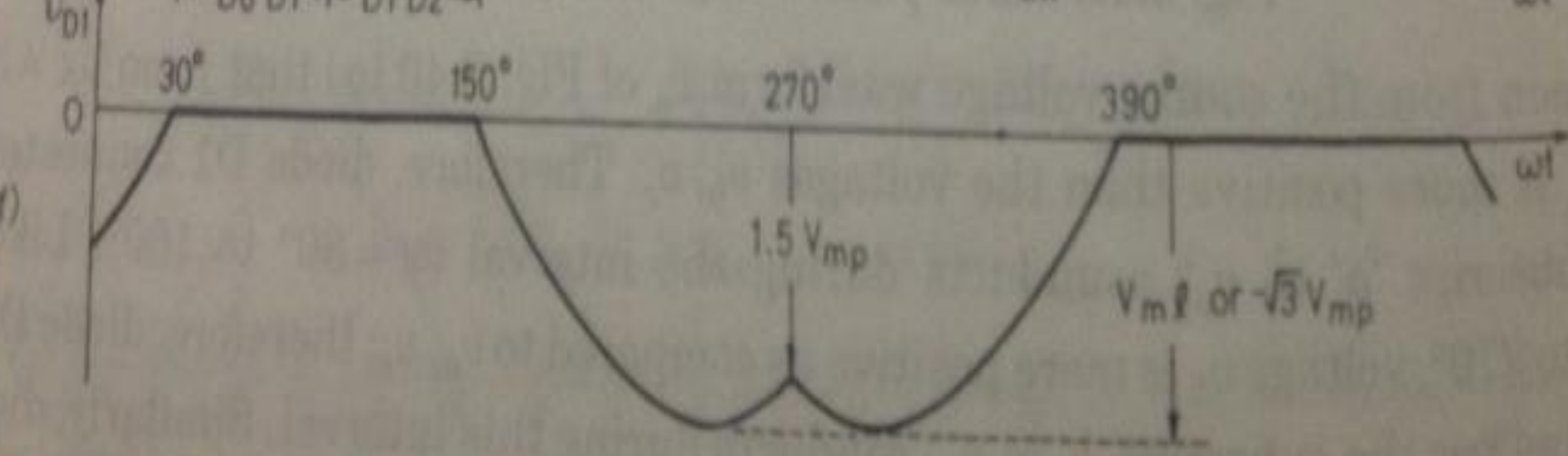
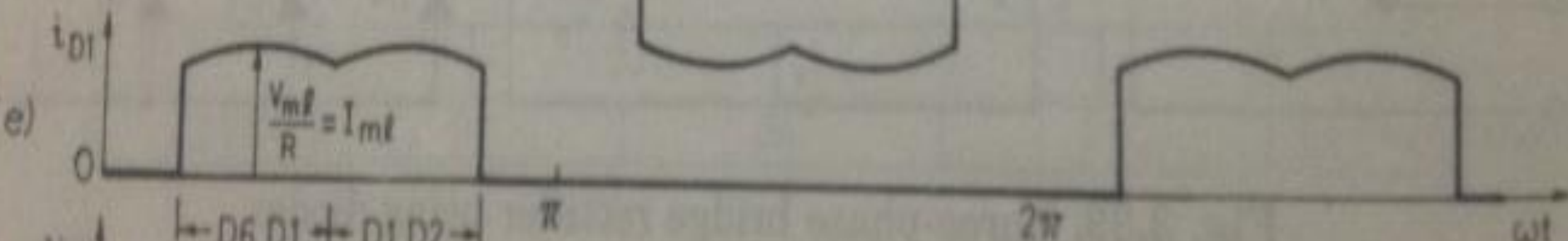
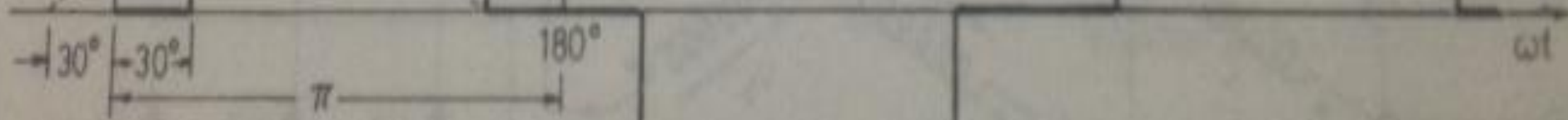
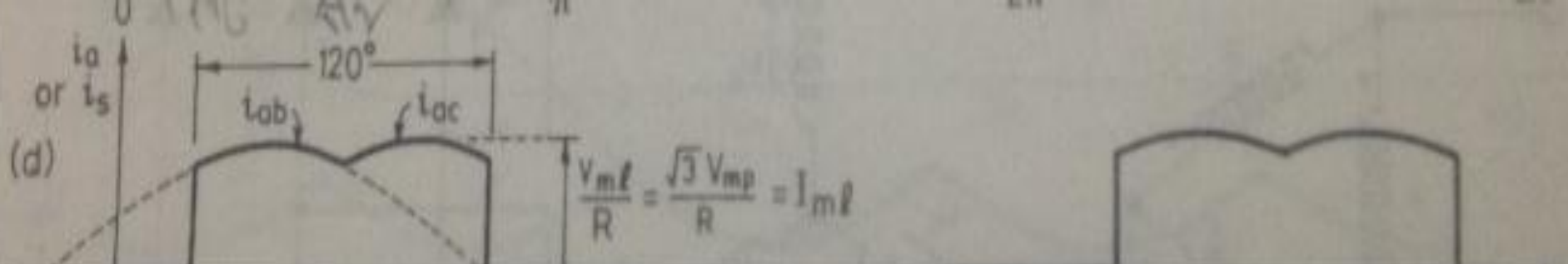


Fig. 9.10 (m)

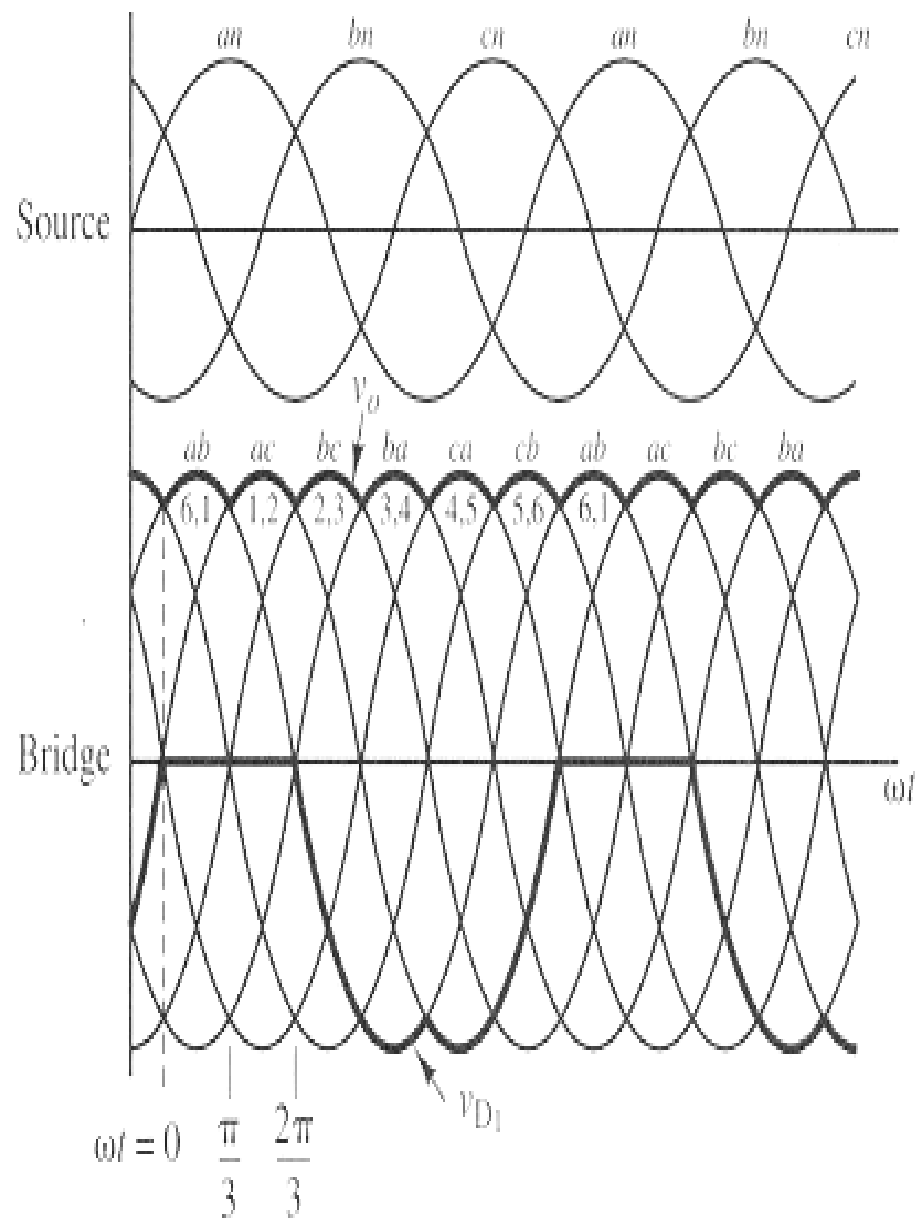

(b)

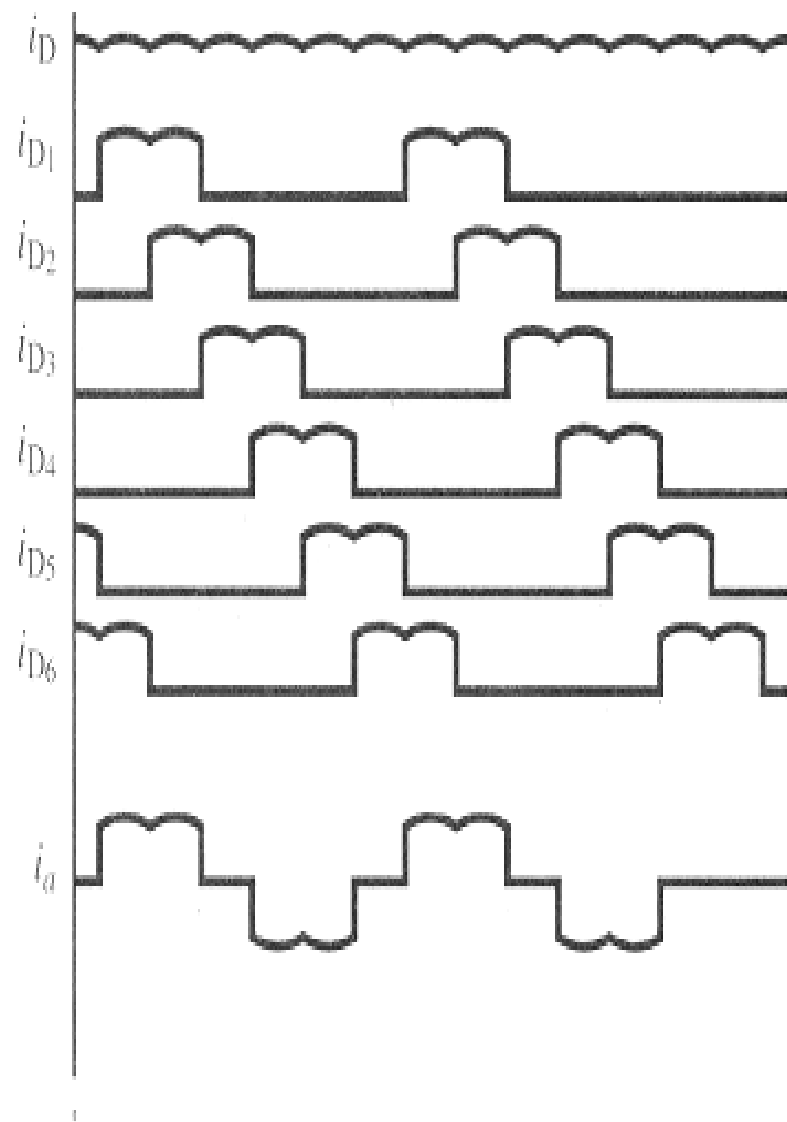

(c)