

VLSI Design (EC0604)
Unit-2
B.Tech (Electronics and Communication)
Semester-6
Ankur Changela


Delay in a Logic Gate

- ❑ Express delays in process-independent unit $d = \frac{d_{abs}}{\tau}$
 - ❑ Delay has two components: $d = f + p$
 - ❑ f : effort delay = gh (a.k.a. stage effort)
 - Again has two components
 - ❑ g : logical effort
 - Measures relative ability of gate to deliver current
 - $g \equiv 1$ for inverter
 - ❑ h : electrical effort = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout
 - ❑ p : parasitic delay
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance
- $\tau = 3RC$
 $\approx 3 \text{ ps in } 65 \text{ nm process}$
 $60 \text{ ps in } 0.6 \mu\text{m process}$

Delay Plots


$$d = f + p$$
$$= gh + p$$

- What about NOR2?

 


Computing Logical Effort

 
- ❑ DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- ❑ Measure from delay vs. fanout plots
- ❑ Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

Catalog of Gates

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	


Catalog of Gates

- Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g = 1$

Electrical Effort: $h = 1$


Parasitic Delay: $p = 1$

Stage Delay: $d = 2$

Frequency: $f_{osc} = 1/(2*N*d) = 1/4N$

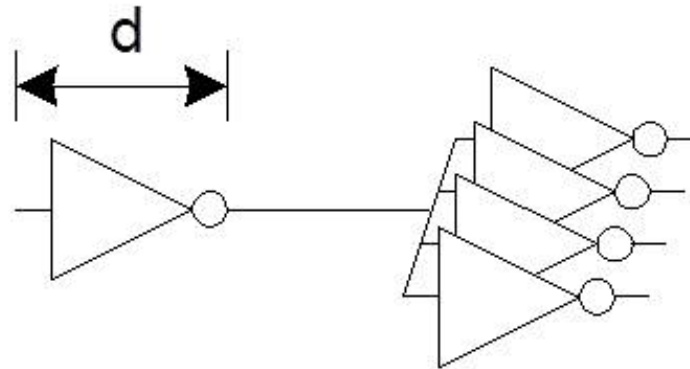Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$

Electrical Effort: $h = 4$

Parasitic Delay: $p = 1$

Stage Delay: $d = 5$

The FO4 delay is about

300 ps in 0.6 μm process

15 ps in a 65 nm process


Multistage Logic Networks

❑ Logical effort generalizes to multistage networks

❑ *Path Logical Effort* $G = \prod g_i$

❑ *Path Electrical Effort* $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 ❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$



Multistage Logic Networks

❑ Logical effort generalizes to multistage networks

❑ *Path Logical Effort* $G = \prod g_i$

❑ *Path Electrical Effort* $H = \frac{C_{out-path}}{C_{in-path}}$

❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$

❑ Can we write $F = GH$?

Paths that Branch

❑ No! Consider paths that branch:

$$G = 1$$


$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

 

Branching Effort

- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$

Multistage Delays

- ❑ Path Effort Delay $D_F = \sum f_i$
- ❑ Path Parasitic Delay $P = \sum p_i$
- ❑ Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

 Example: 3-stage path

- Select gate sizes x and y for least delay from A to B



Example: 3-stage path

 

Logical Effort

$$G = (4/3) * (5/3) * (5/3) = 100/27$$

Electrical Effort

$$H = 45/8$$

Branching Effort

$$B = 3 * 2 = 6$$

Path Effort

$$F = GBH = 125$$

Best Stage Effort

$$\hat{f} = \sqrt[3]{F} = 5$$

Parasitic Delay

$$P = 2 + 3 + 2 = 7$$

Delay


$$D = 3 * 5 + 7 = 22 = 4.4 FO4$$

Example: 3-stage path

- Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$

$$x = (15*2) * (5/3) / 5 = 10$$

 


Best Number of Stages

- ❑ How many stages should a path use?
 - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$


$$= N(64)^{1/N} + N$$

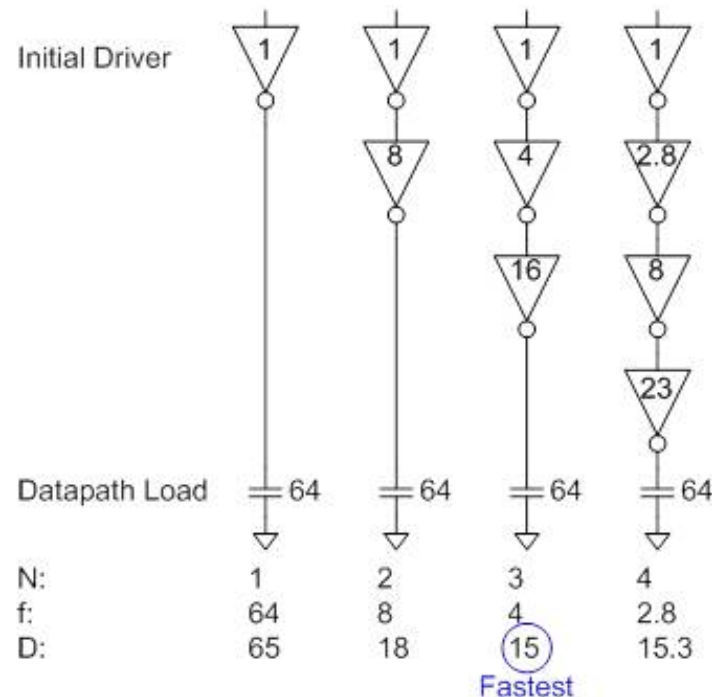

Derivation

- Consider adding inverters to end of path
 - How many give least delay?
 
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$



$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{\frac{1}{N}}$


$$p_{inv} + \rho (1 - \ln \rho) = 0$$

Best Stage Effort

- ❑ $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- ❑ Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- ❑ For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

Sensitivity Analysis

 
- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$

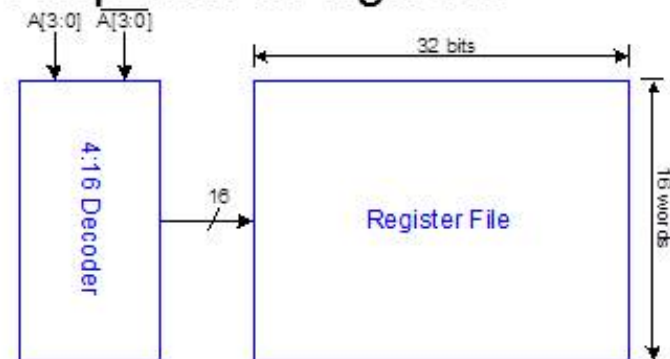Example, Revisited

- ❑ Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.



- ❑ Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs $A[3:0]$
 - Each input may drive 10 unit-sized transistors
- ❑ Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

Number of Stages

- ❑ Decoder effort is mainly electrical and branching

Electrical Effort: $H = (32 \cdot 3) / 10 = 9.6$

Branching Effort: $B = 8$

- ❑ If we neglect logical effort (assume $G = 1$)

Path Effort: $F = GBH = 76.8$

Number of Stages: $N = \log_4 F = 3.1$

- ❑ Try a 4-stage design

Gate Sizes & Delay


Logical Effort: $G = 1 * 6/3 * 1 = 2$

Path Effort: $F = GBH = 154$

Stage Effort: $\hat{f} = F^{1/3} = 5.36$

Path Delay: $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

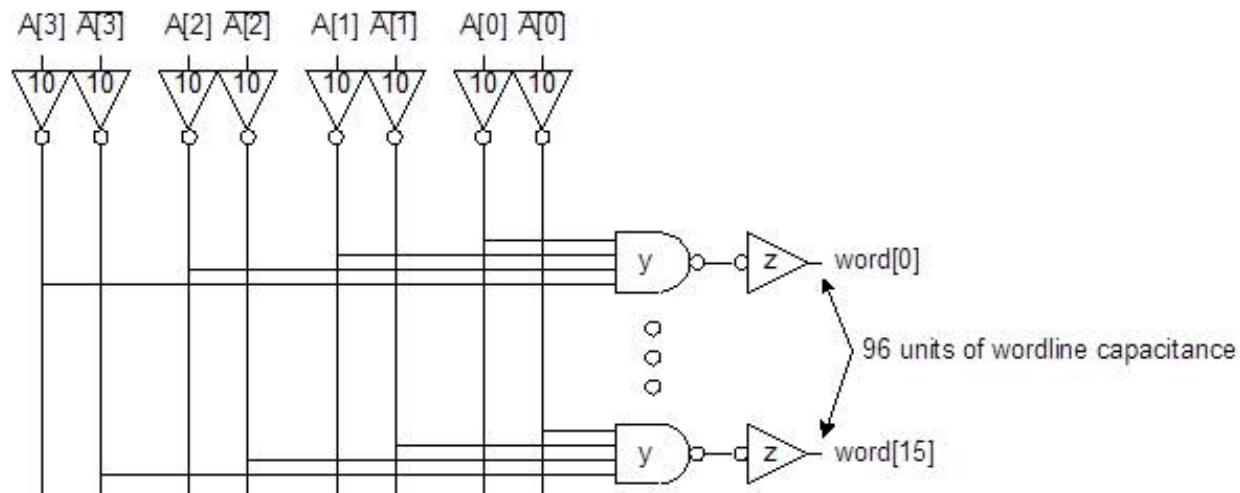Gate sizes: $z = 96 * 1 / 5.36 = 18$ $y = 18 * 2 / 5.36 = 6.7$



Comparison

- ❑ Compare many alternatives with a spreadsheet
- ❑ $D = N(76.8 G)^{1/N} + P$

Design	N	G	P	D
NOR4	1	3	4	234
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Method of Logical Effort

- 1) Compute path effort
- 2) Estimate best number of stages
- 3) Sketch path with N stages
- 4) Estimate least delay
- 5) Determine best stage effort

- 6) Find gate sizes

$$F = GBH$$

$$N = \log_4 F$$

$$D = NF^{\frac{1}{N}} + P$$

$$\hat{f} = F^{\frac{1}{N}}$$

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

Limits of Logical Effort

- ❑ Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- ❑ Simplistic delay model
 - Neglects input rise time effects
- ❑ Interconnect
 - Iteration required in designs with wire
- ❑ Maximum speed only
 - Not minimum area/power for constrained delay

Power and Energy

❑ Power is drawn from a voltage source attached to the V_{DD} pin(s) of a chip.

❑ Instantaneous Power: $P(t) = I(t)V(t)$

❑ Energy:
$$E = \int_0^T P(t) dt$$


❑ Average Power:
$$P_{\text{avg}} = \frac{E}{T} = \frac{1}{T} \int_0^T P(t) dt$$

Power in Circuit Elements


$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$


 
$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$


 
$$\begin{aligned} E_C &= \int_0^{\infty} I(t)V(t)dt = \int_0^{\infty} C \frac{dV}{dt} V(t)dt \\ &= C \int_0^{V_C} V(t)dV = \frac{1}{2} CV_C^2 \end{aligned}$$



Charging a Capacitor


- When the gate output rises
 - Energy stored in capacitor is

$$E_C = \frac{1}{2} C_L V_{DD}^2$$

- But energy drawn from the supply is


$$\begin{aligned} E_{V_{DD}} &= \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt \\ &= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2 \end{aligned}$$

 - Half the energy from V_{DD} is dissipated in the pMOS transistor as heat, other half stored in capacitor
- When the gate output falls
 - Energy in capacitor is dumped to GND
 - Dissipated as heat in the nMOS transistor




Switching Waveforms

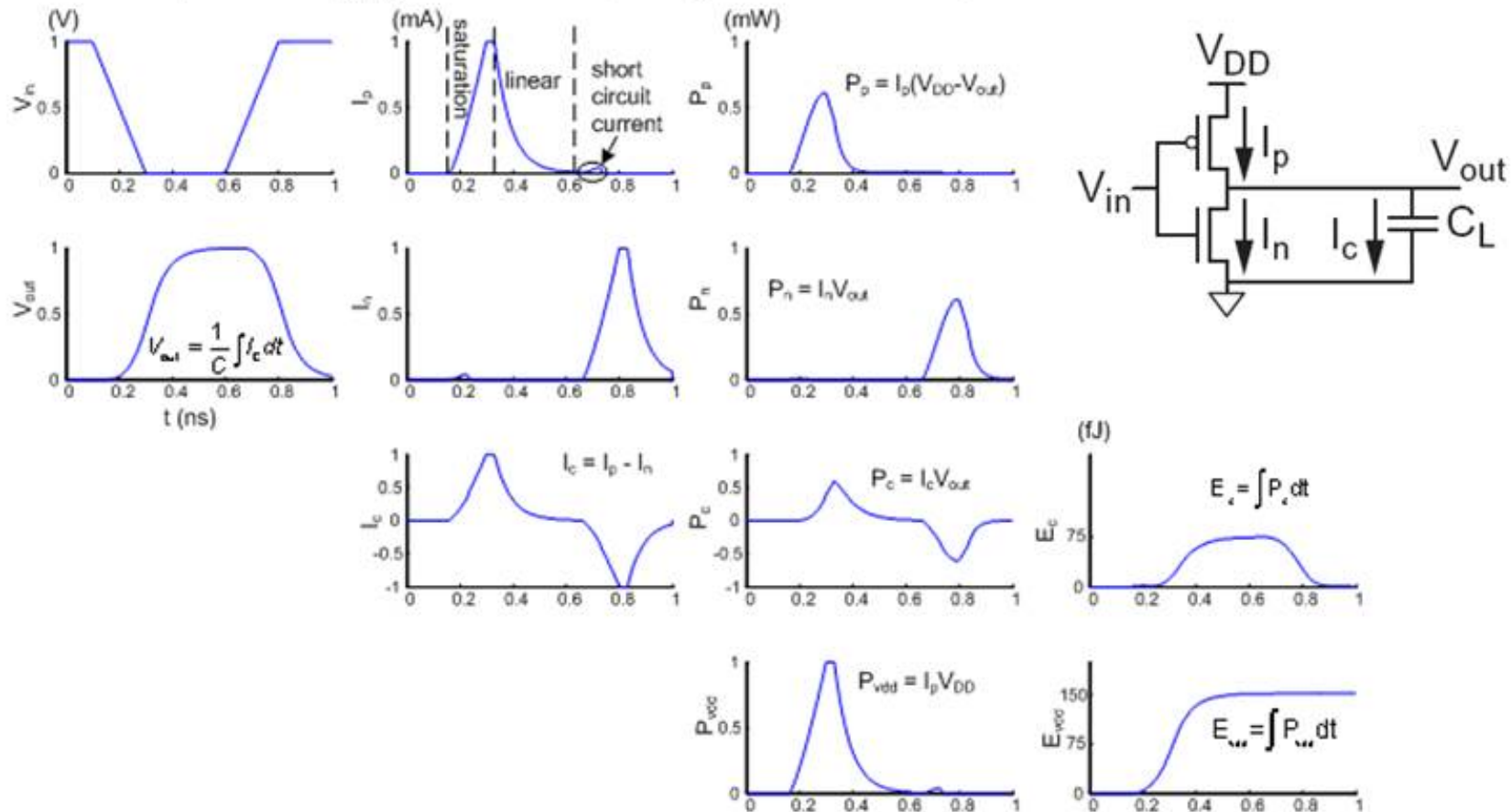Example: $V_{DD} = 1.0 \text{ V}$, $C_L = 150 \text{ fF}$, $f = 1 \text{ GHz}$



Switching Power
 
$$\begin{aligned} P_{\text{switching}} &= \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt \\ &= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt \\ &= \frac{V_{DD}}{T} [T f_{\text{sw}} C V_{DD}] \\ &= C V_{DD}^2 f_{\text{sw}} \end{aligned}$$



Activity Factor

- ❑ Suppose the system clock frequency = f
- ❑ Let $f_{sw} = \alpha f$, where α = activity factor
 - If the signal is a clock, $\alpha = 1$
 - If the signal switches once per cycle, $\alpha = 1/2$

- ❑ Dynamic power:

$$P_{\text{switching}} = \alpha C V_{DD}^2 f$$

Short Circuit Current

- ❑ When transistors switch, both nMOS and pMOS networks may be momentarily ON at once
- ❑ Leads to a blip of “short circuit” current.
- ❑ $< 10\%$ of dynamic power if rise/fall times are comparable for input and output
- ❑ We will generally ignore this component

Power Dissipation Sources

- ❑ $P_{\text{total}} = P_{\text{dynamic}} + P_{\text{static}}$
- ❑ Dynamic power: $P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{shortcircuit}}$
 - Switching load capacitances
 - Short-circuit current
- ❑ Static power: $P_{\text{static}} = (I_{\text{sub}} + I_{\text{gate}} + I_{\text{junct}} + I_{\text{contention}})V_{\text{DD}}$
 - Subthreshold leakage
 - Gate leakage
 - Junction leakage
 - Contention current