

VLSI Design (EC0604)

Unit-4

B.Tech (Electronics and Communication)

Semester-6

Ankur Changela

UNIT4: VLSI Design

Introduction

- **VLSI realization process**
- **Verification and test**
- **Ideal and real tests**
- **Costs of testing**
- **Roles of testing**
- **A modern VLSI device - system-on-a-chip**
- **Testing**
 - **Digital**
 - **Memory**
 - **Analog**
 - **RF**
- **Textbook**
- **Problem to solve**

VLSI Realization Process

Customer's need

Determine requirements

Write specifications


Design synthesis and Verification

Test development

Fabrication

Manufacturing test

Chips to customer

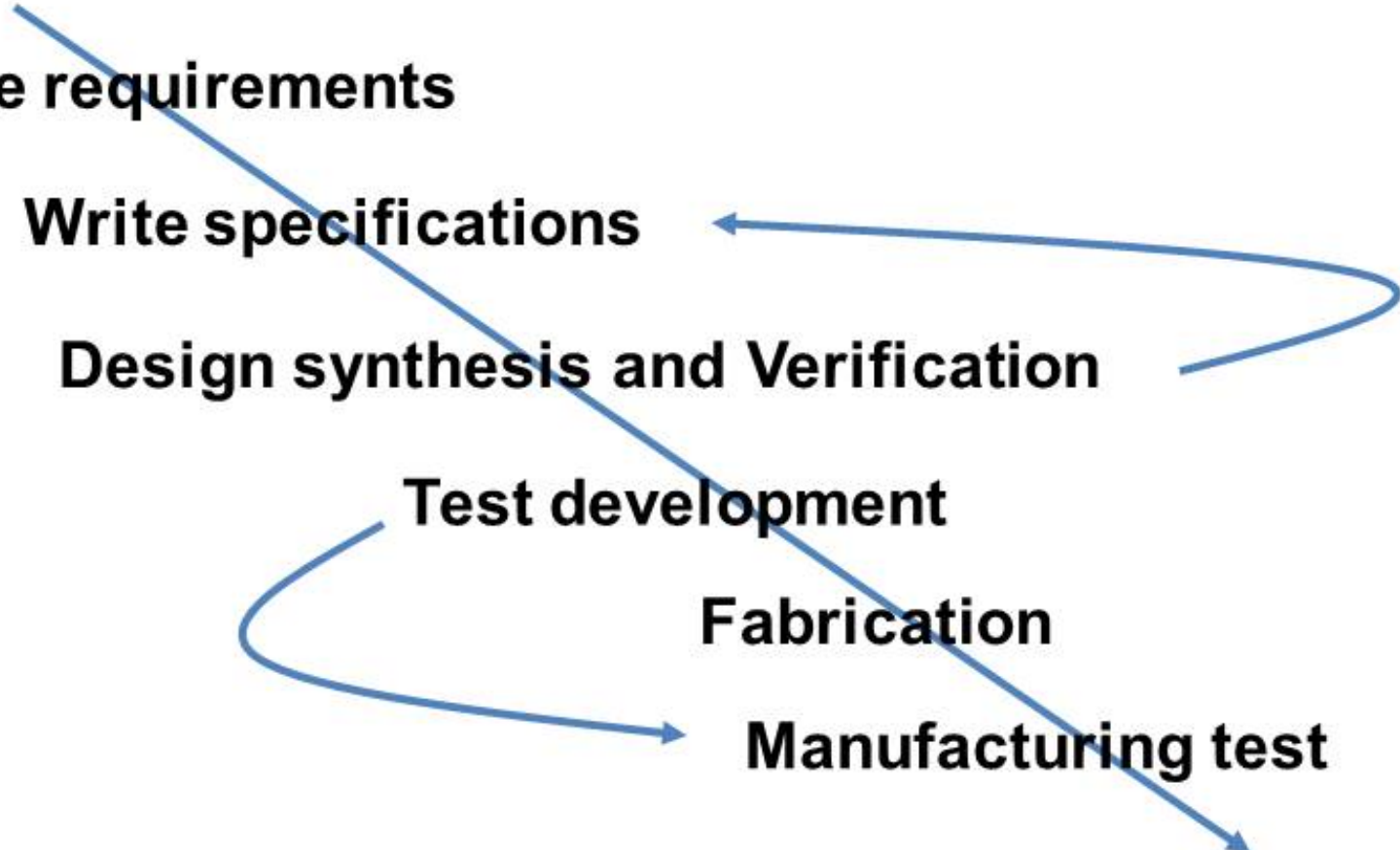

Definitions

- ***Design synthesis:*** Given an I/O function, develop a procedure to manufacture a device using known materials and processes.
- ***Verification:*** Predictive analysis to ensure that the synthesized design, when manufactured, will perform the given I/O function.
- ***Test:*** A manufacturing step that ensures that the physical device, manufactured from the synthesized design, has no manufacturing defect.

Verification vs. Test

Verification

- Verifies correctness of design.
- Performed by simulation, hardware emulation, or formal methods.
- Performed once prior to manufacturing.
- Responsible for quality of design.

Test

- Verifies correctness of manufactured hardware.
- Two-part process:
 - 1. Test generation: software process executed once during design
 - 2. Test application: electrical tests applied to hardware
- Test application performed on every manufactured device.
- Responsible for quality of devices.

Costs of Testing

- ***Design for testability (DFT)***
 - Chip area overhead and yield reduction
 - Performance overhead
- **Software processes of test**
 - Test generation and fault simulation
 - Test programming and debugging
- **Manufacturing test**
 - *Automatic test equipment (ATE)* capital cost
 - Test center operational cost

Present and Future*

	1997 -2001	2003 - 2006
Feature size (micron)	0.25 - 0.15	0.13 - 0.10
Transistors/sq. cm	4 - 10M	18 - 39M
Pin count	100 – 900	160 - 1475
Clock rate (MHz)	200 – 730	530 - 1100
Power (Watts)	1.2 – 61	2 - 96

*** SIA Roadmap, IEEE Spectrum, July 1999**

Fault Modeling

- **Why model faults?**
- **Some real defects in VLSI and PCB**
- **Common fault models**
- **Stuck-at faults**
 - **Single stuck-at faults**
 - **Fault equivalence**
 - **Fault dominance and checkpoint theorem**
 - **Classes of stuck-at faults and multiple faults**
- **Transistor faults**
- **Summary**

Why Model Faults?

- **I/O function tests inadequate for manufacturing (functionality versus component and interconnect testing)**
- **Real defects (often mechanical) too numerous and often not analyzable**
- **A fault model identifies targets for testing**
- **A fault model makes analysis possible**
- **Effectiveness measurable by experiments**

Some Real Defects in Chips

- **Processing defects**
 - **Missing contact windows**
 - **Parasitic transistors**
 - **Oxide breakdown**
 - **...**
- **Material defects**
 - **Bulk defects (cracks, crystal imperfections)**
 - **Surface impurities (ion migration)**
 - **...**
- **Time-dependent failures**
 - **Dielectric breakdown**
 - **Electromigration**
 - **...**
- **Packaging failures**
 - **Contact degradation**
 - **Seal leaks**
 - **...**

Ref.: M. J. Howes and D. V. Morgan, *Reliability and Degradation - Semiconductor Devices and Circuits*, Wiley, 1981.

Observed PCB Defects

Defect classes	Occurrence frequency (%)
Shorts	51
Opens	1
Missing components	6
Wrong components	13
Reversed components	6
Bent leads	8
Analog specifications	5
Digital logic	5
Performance (timing)	5


Ref.: J. Bateson, *In-Circuit Testing*, Van Nostrand Reinhold, 1985.

Common Fault Models

- **Single stuck-at faults**
- **Transistor open and short faults**
- **Memory faults**
- **PLA faults (stuck-at, cross-point, bridging)**
- **Functional faults (processors)**
- **Delay faults (transition, path)**
- **Analog faults**
- **For more details of fault models, see**
M. L. Bushnell and V. D. Agrawal, Essentials of Electronic Testing for Digital, Memory and Mixed-Signal VLSI Circuits, Springer, 2000.

Single Stuck-at Fault

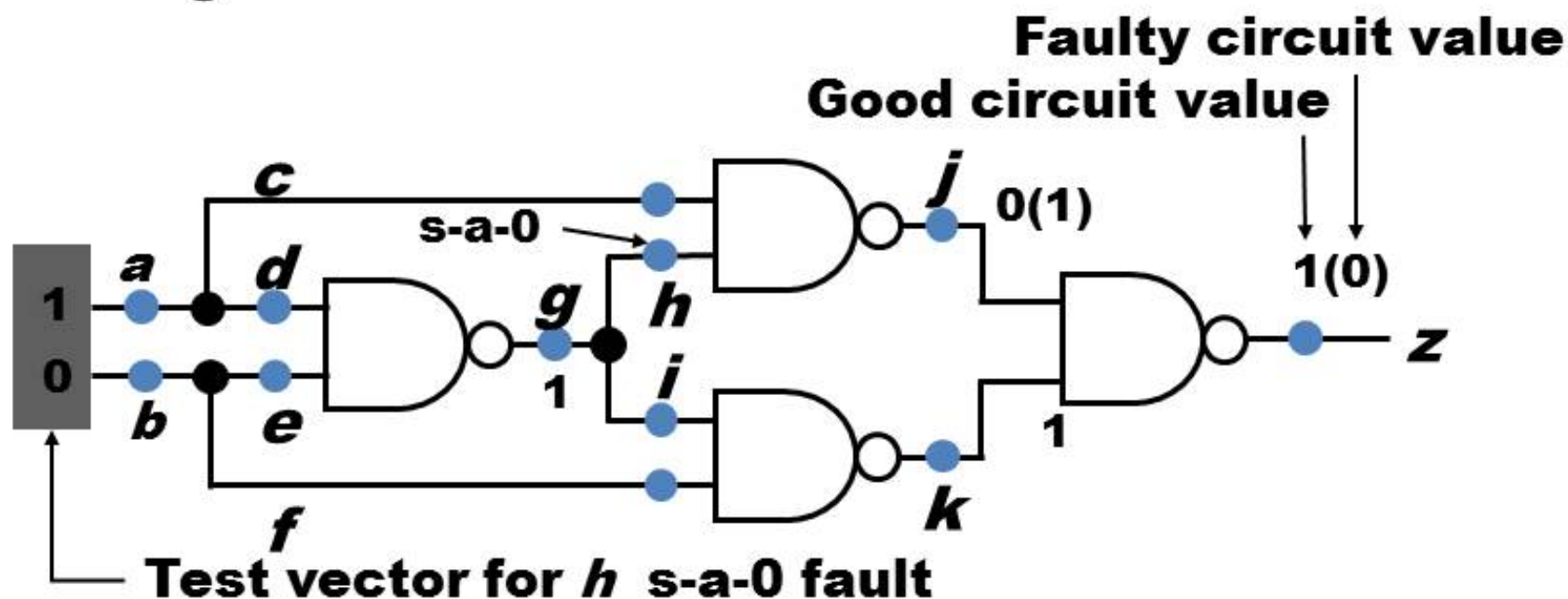
- **Three properties define a single stuck-at fault**
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate
- **Example: XOR circuit has 12 fault sites () and 24 single stuck-at faults**




Fault Equivalence

- **Number of fault sites in a Boolean gate circuit is = #PI + #gates + # (fanout branches)**
- **Fault equivalence: Two faults f1 and f2 are equivalent if all tests that detect f1 also detect f2.**
- **If faults f1 and f2 are equivalent then the corresponding faulty functions are identical.**
- **Fault collapsing: All single faults of a logic circuit can be divided into disjoint equivalence subsets, where all faults in a subset are mutually equivalent. A collapsed fault set contains one fault from each equivalence subset.**

Structural Equivalence

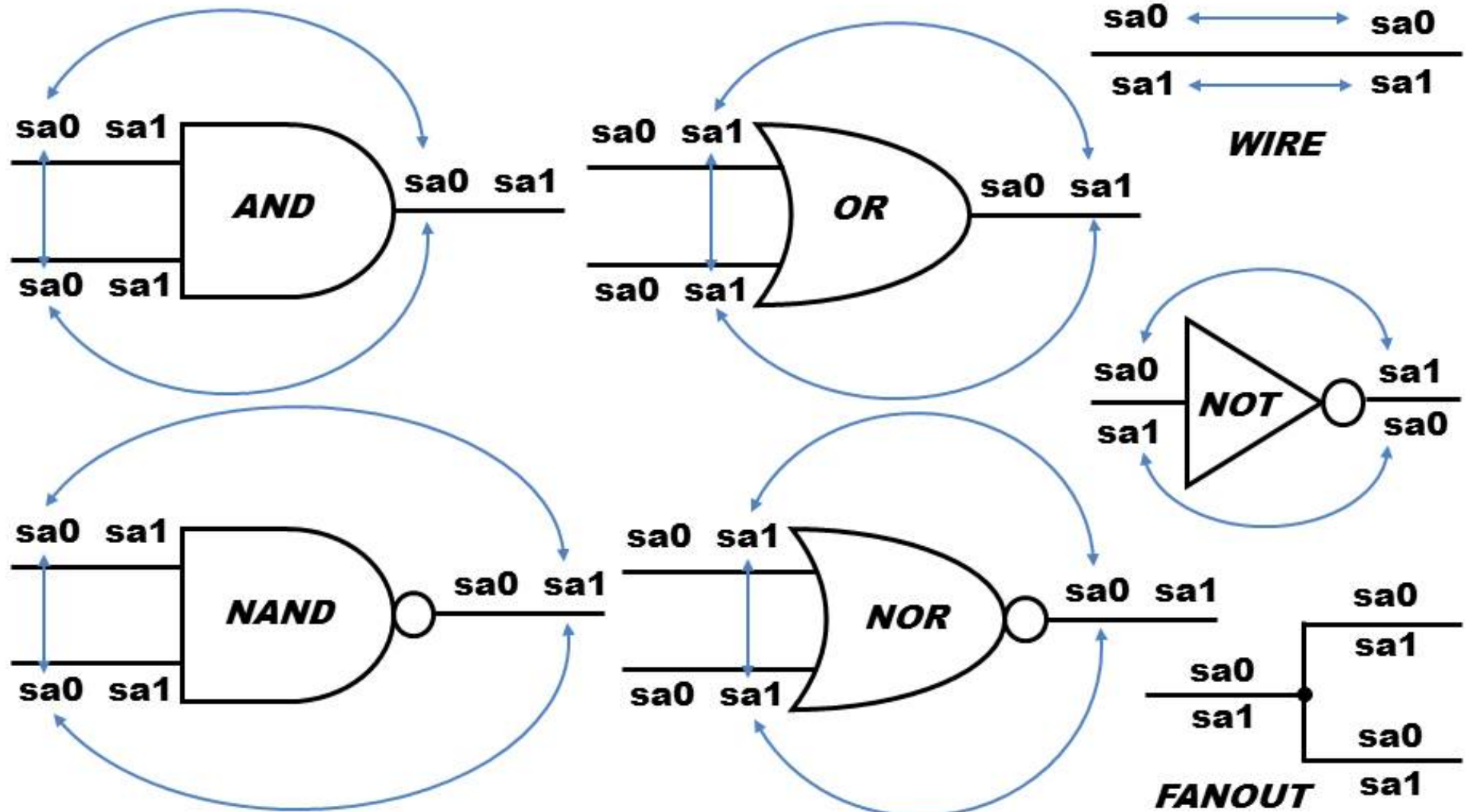


Equivalence Example

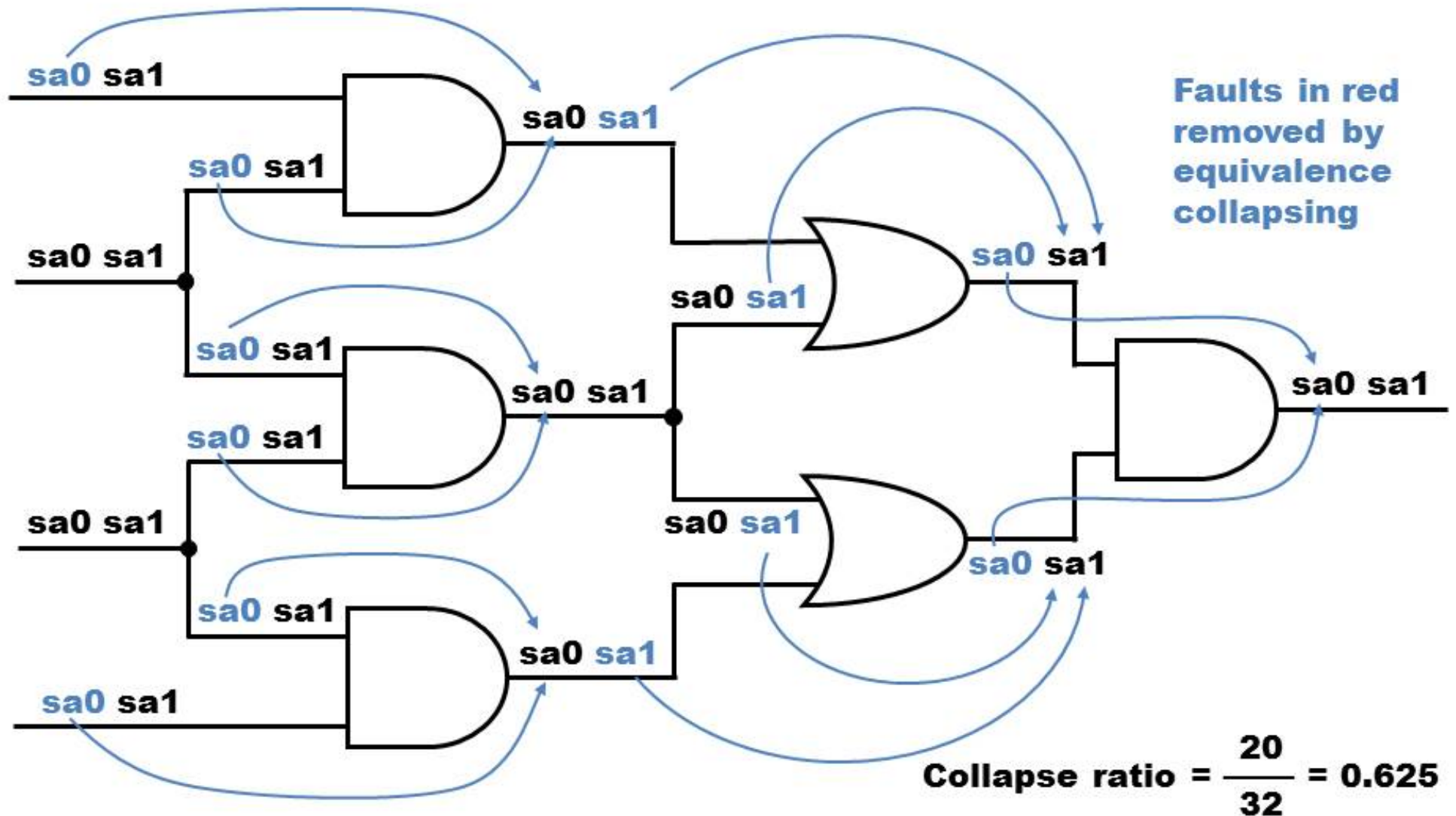


Fault Dominance

- **If all tests of some fault F1 detect another fault F2, then F2 is said to dominate F1.**
- **Dominance fault collapsing: If fault F2 dominates F1, then F2 is removed from the fault list.**
- **When dominance fault collapsing is used, it is sufficient to consider only the input faults of Boolean gates. See the next example.**
- **In a tree circuit (without fanouts) PI faults form a dominance collapsed fault set.**
- **If two faults dominate each other then they are equivalent.**

Dominance Example

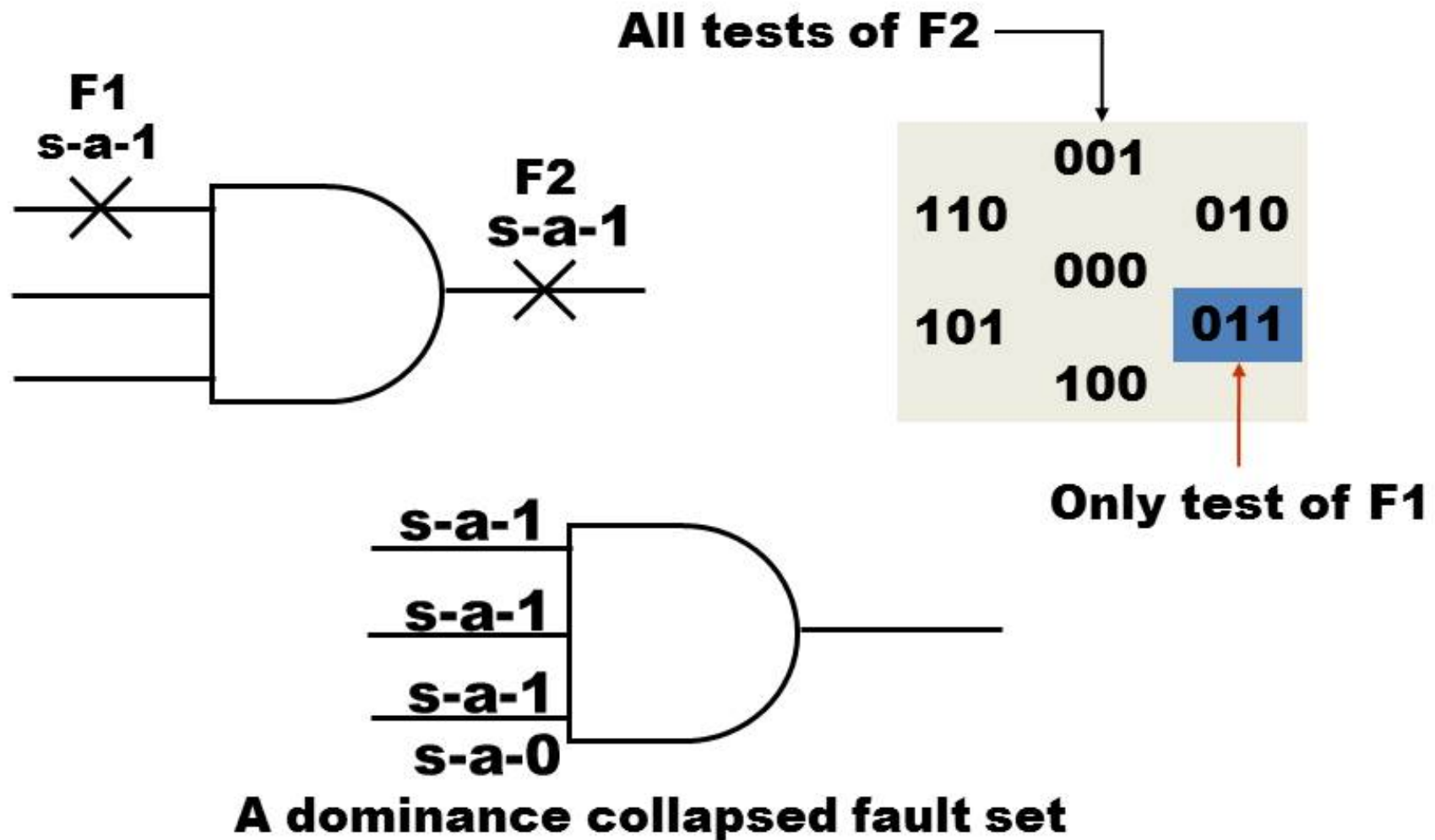

Dominance Example

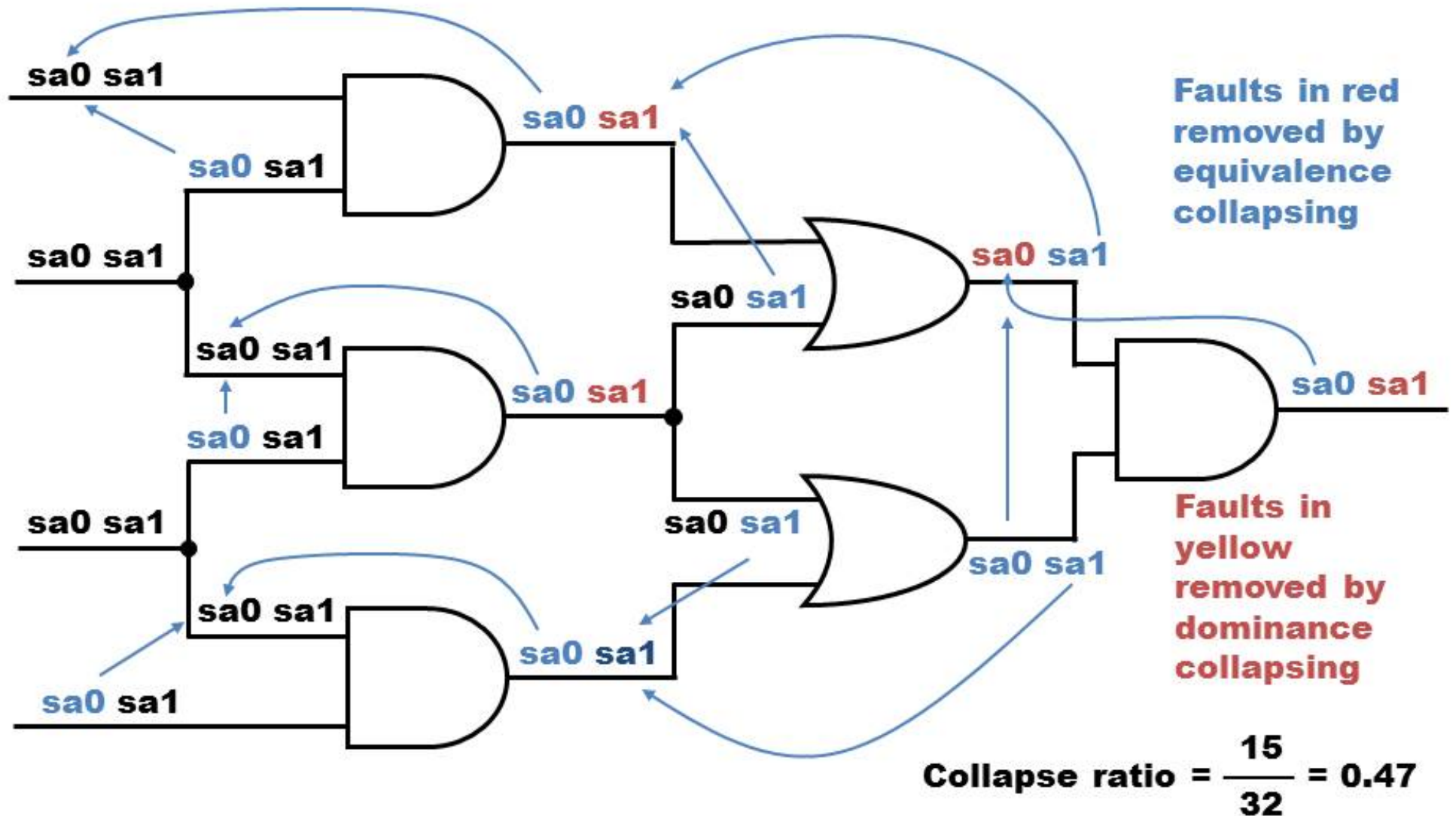

Lecture 4: Testability Analysis

- **Definition**
- **Controllability and observability**
- **SCOAP measures**
 - **Combinational circuits**
 - **Sequential circuits**
- **Summary**

What are Testability Measures?

- **Approximate measures of:**
 - **Difficulty of setting internal circuit lines to 0 or 1 from primary inputs.**
 - **Difficulty of observing internal circuit lines at primary outputs.**
- **Applications:**
 - **Analysis of difficulty of testing internal circuit parts – redesign or add special test hardware.**
 - **Guidance for algorithms computing test patterns – avoid using hard-to-control lines.**





SCOAP Measures

- **SCOAP – Sandia Controllability and Observability Analysis Program**
- **Combinational measures:**
 - **CC0** – Difficulty of setting circuit line to logic 0
 - **CC1** – Difficulty of setting circuit line to logic 1
 - **CO** – Difficulty of observing a circuit line
- **Sequential measures – analogous:**
 - **SC0**
 - **SC1**
 - **SO**
- **Ref.: L. H. Goldstein, “Controllability/Observability Analysis of Digital Circuits,” *IEEE Trans. CAS*, vol. CAS-26, no. 9. pp. 685 – 693, Sep. 1979.**




Range of SCOAP Measures

- **Controllabilities – 1 (easiest) to infinity (hardest)**
- **Observabilities – 0 (easiest) to infinity (hardest)**
- **Combinational measures:**
 - Roughly proportional to number of circuit lines that must be set to control or observe given line.
- **Sequential measures:**
 - Roughly proportional to number of times flip-flops must be clocked to control or observe given line.

Combinational Controllability

  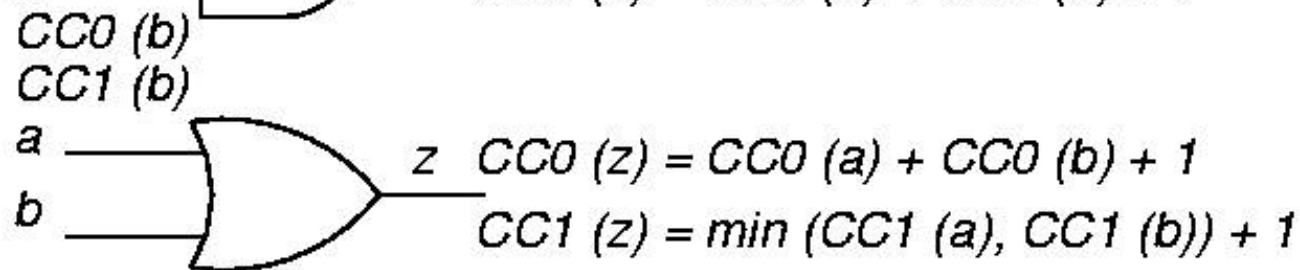 

Controllability Formulas (Continued)

   

Combinational Observability

To observe a gate input: Observe output and make other input values non-controlling.

$$CO(a) = CO(z) + CC1(b) + 1$$

$$CO(b) = CO(z) + CC1(a) + 1$$

$$CO(a) = CO(z) + CC0(b) + 1$$


$$CO(b) = CO(z) + CC0(a) + 1$$

$$CO(a) = CO(z) + \min(CC0(b), CC1(b)) + 1$$

$$CO(b) = CO(z) + \min(CC0(a), CC1(a)) + 1$$

$$CO(a) = CO(z) + CC1(b) + 1$$

$$CO(b) = CO(z) + CC1(a) + 1$$

 

Observability Formulas (Continued)

$$CO(a) = CO(z) + CC0(b) + 1$$





$$CO(b) = CO(z) + CC0(a) + 1$$

$$CO(a) = CO(z) + \min(CC0(b), CC1(b)) + 1$$

$$CO(b) = CO(z) + \min(CC0(a), CC1(a)) + 1$$

$$CO(a) = CO(z) + 1$$

    
$$CO(a) = \min(CO(z1), CO(z2), \dots, CO(zn))$$




Fanout stem: Observe through branch with best observability.

Comb. Controllability

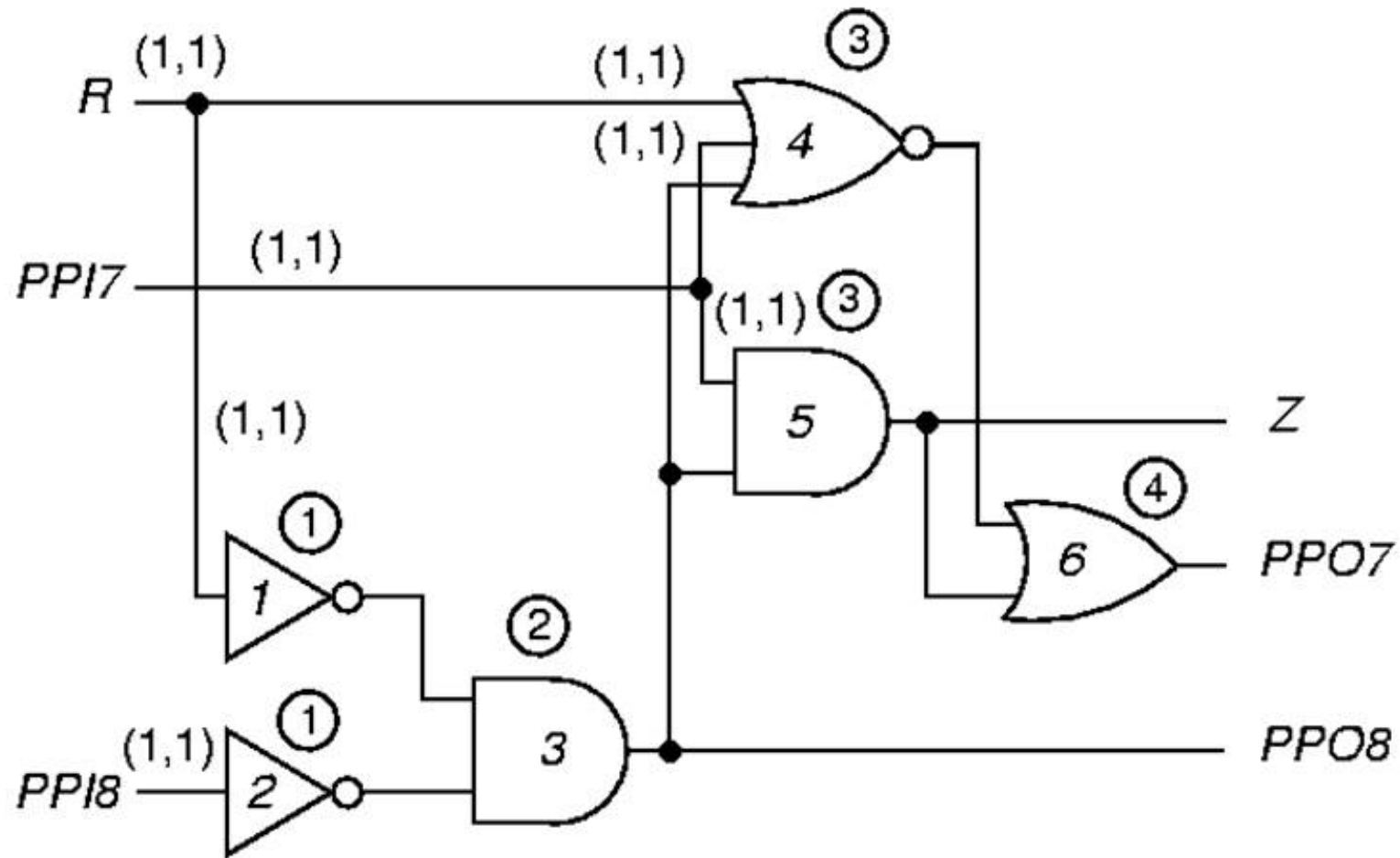
Circled numbers give level number. (CC0, CC1)



Controllability Through Level 2

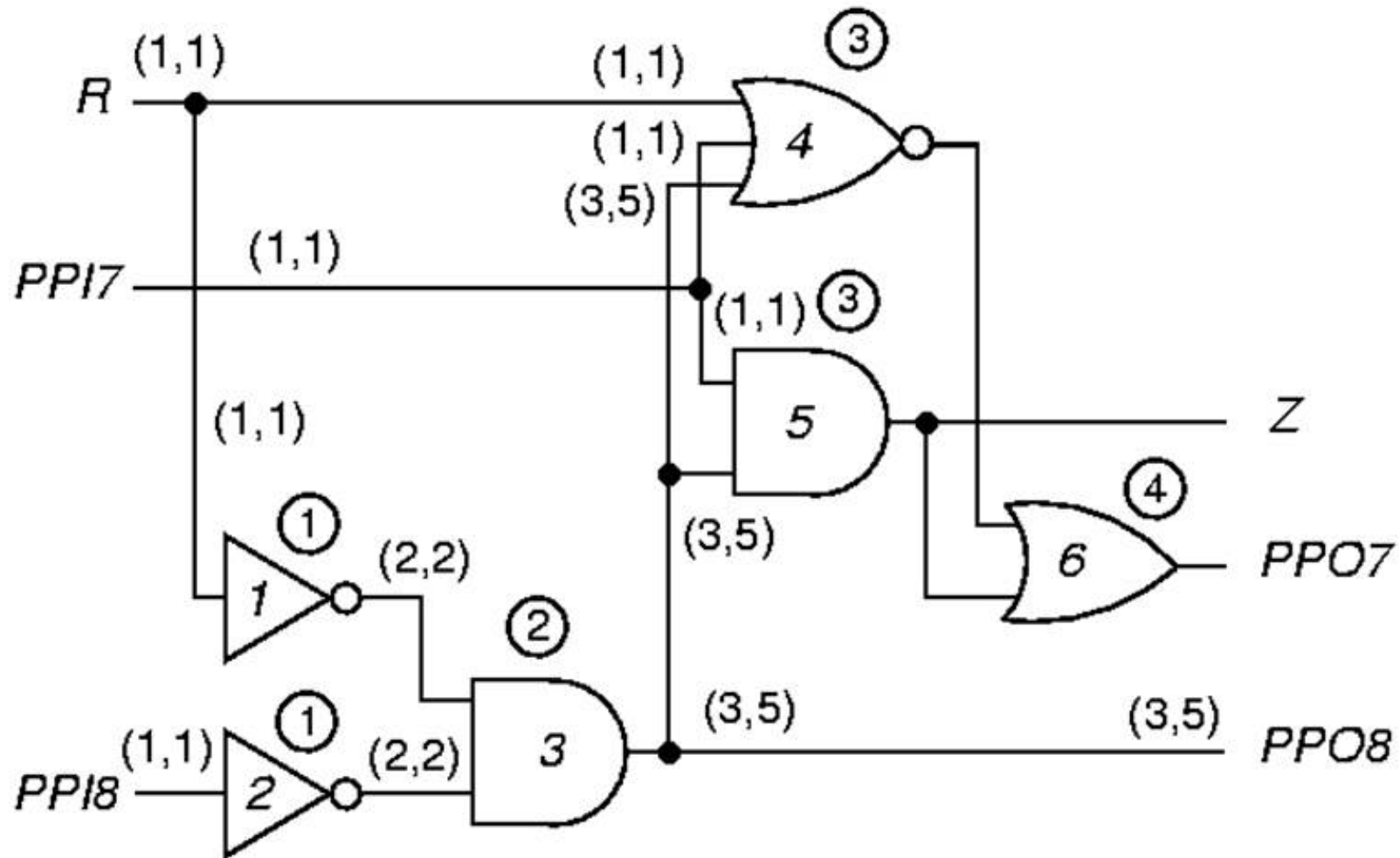


Final Combinational Controllability

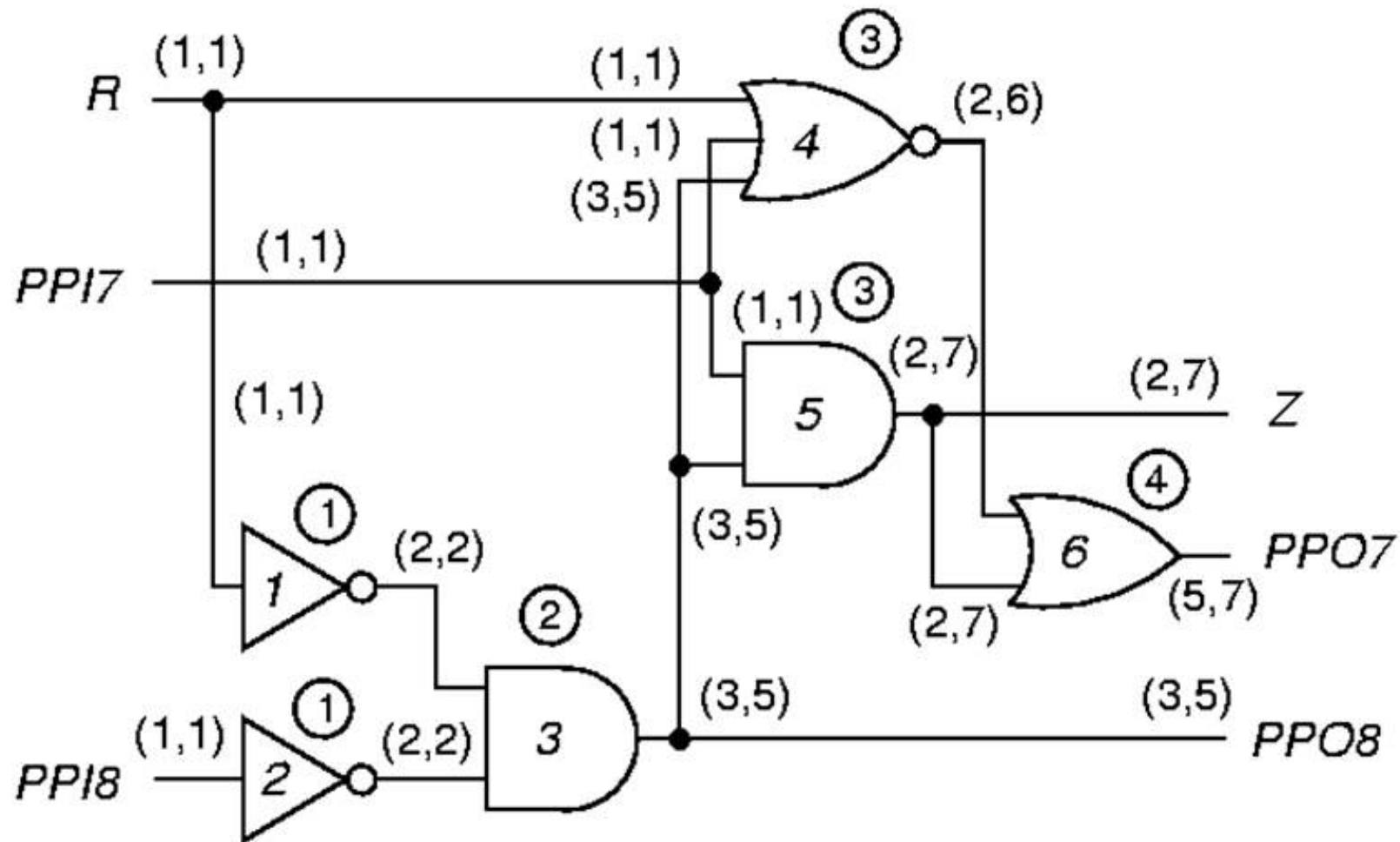


Combinational Observability for Level 1

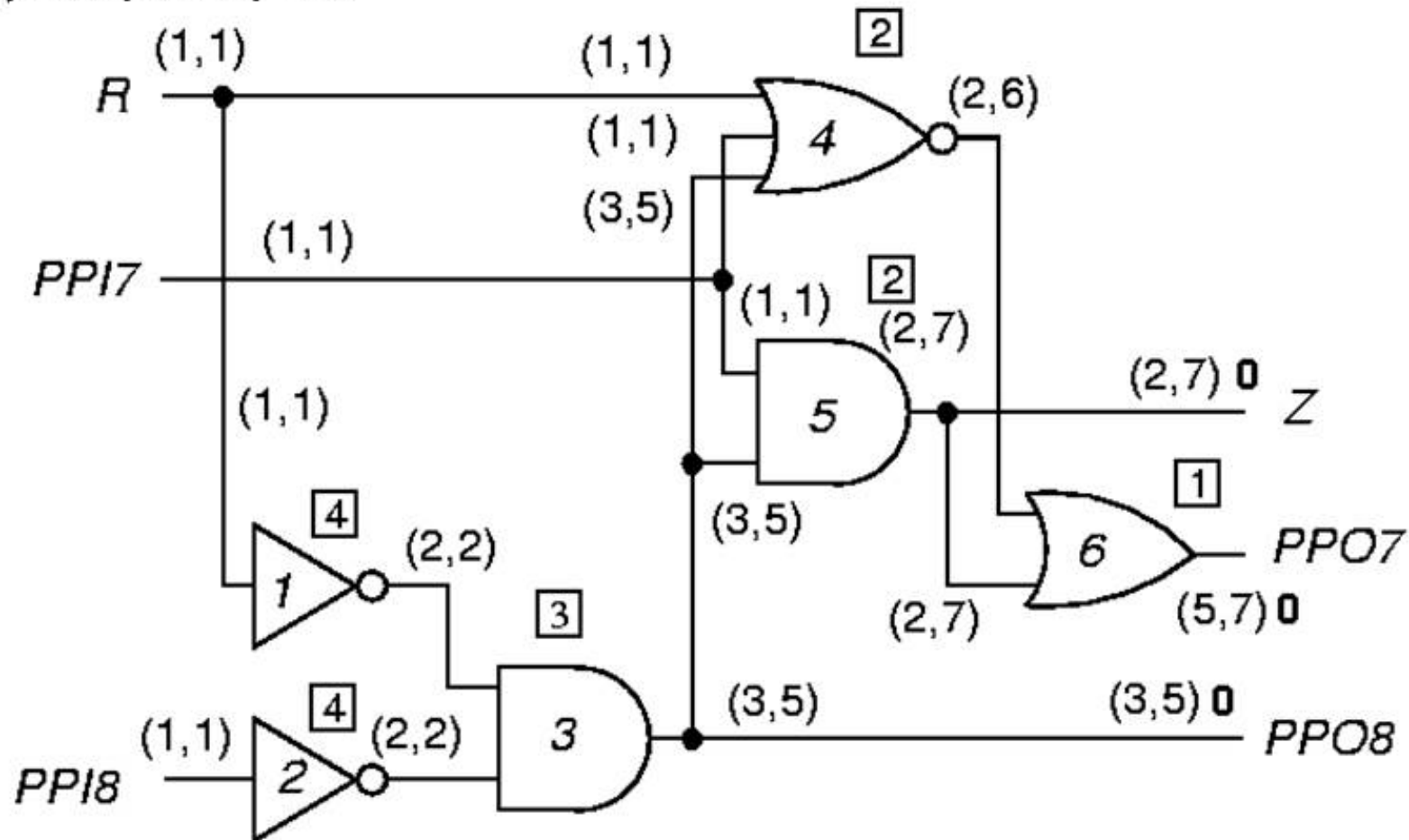Number in square box is level from *primary outputs (POs)*.
(CC0, CC1) CO



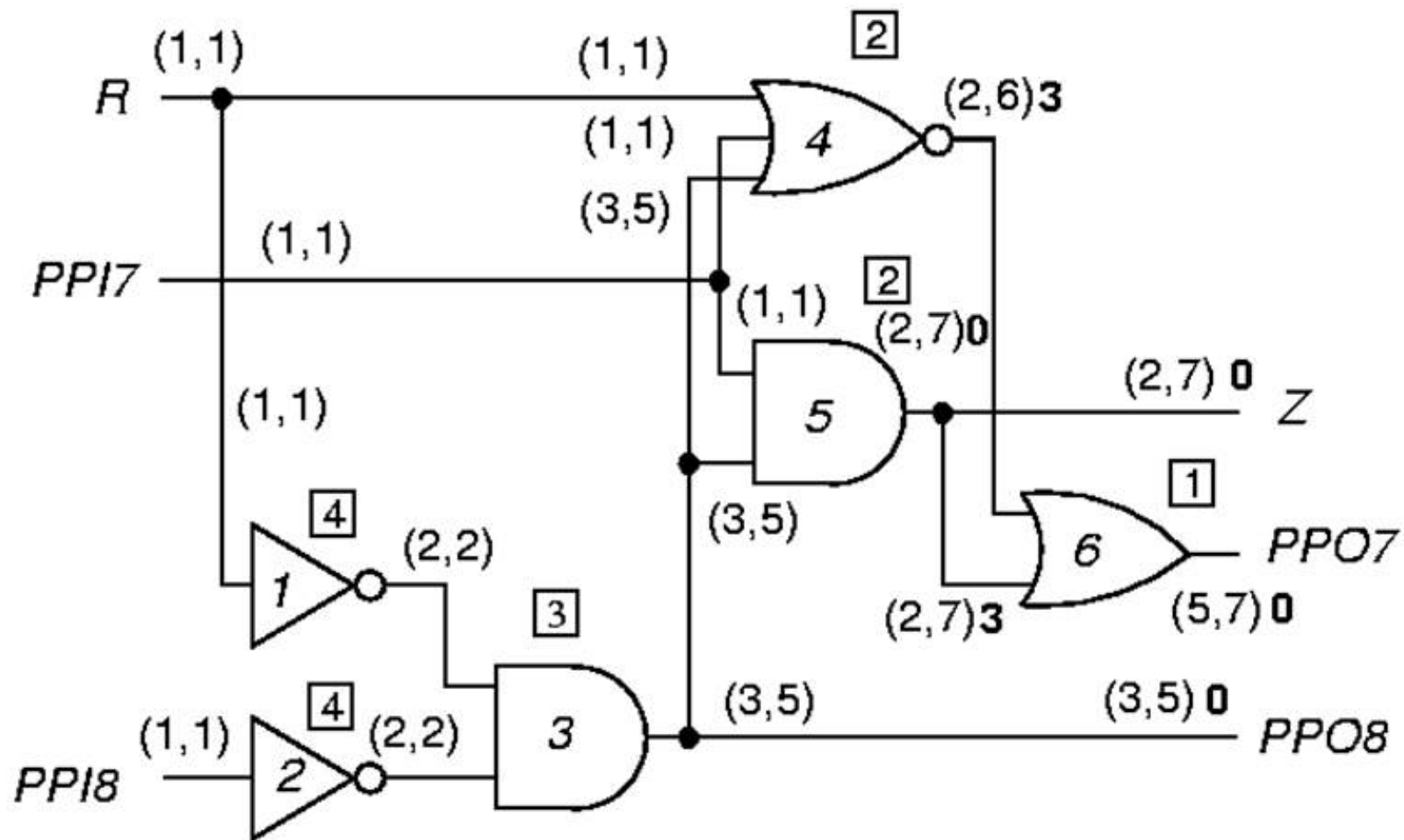Combinational Observabilities for Level 2



Final Combinational Observabilities

