### **Operational Amplifier**

I

## Introduction

- An op-amp is a direct coupled high-gain amplifier usually consisting of one or more differential amplifier and usually followed by a level translator and an O/P stage.
- Used to amplify DC as well as AC I/P signal and was originally designed for performing mathematical operation such as:
  - □ Addition
  - Subtraction
  - Multiplication
  - Integration

□ Also used as active-filter, oscillator, comparator etc.....



# **OPAMP** Block Diagram

- The input stage of an OP-Amp is a differential amplifier (DA) and the output stage is typically a class B push-pull emitter follower.
- The internal stages of an *OP-Amp* are direct-coupled i.e., no coupling capacitors are used. The direct coupling allows the *OP-Amp* to amplify d.c. as well as a.c. signals
- An OP-Amp has *very high input resistance (ideally infinite)*. The effect of high input impedance is that the amplifier will draw a very small current (ideally zero) from the signal source.



The op-amp has the following characteristics:

• It is basically a "three terminal" amplifier with two inputs and an output. It is a differential amplifier with very high gain

$$v_{out} = A(v_+ - v_-)$$

where A is typically  $10^4 - 10^5$ , and the two inputs are known as the *non-inverting*  $(v_+)$  and *inverting*  $(v_-)$  inputs respectively. In the ideal op-amp we assume that the gain A is infinite.

- In an ideal op-amp no current flows into either input, that is they are voltage-controlled and have infinite input resistance. In a practical op-amp the input current is in the order of pico-amps (10<sup>-12</sup>) amp, or less.
- The output acts as a voltage source, that is it can be modeled as a Thevenin source with a very low source resistance.

#### **IDEAL OP-AMP CHARACTERISTICS**

- □ Infinite voltage gain (A)
- □ Infinite input resistance (Ri) . So that almost any signal source can drive it and there is no loading of the preceding stage.
- Zero output resistance (Ro) so that the output can drive an infinite no.of other device.
- □ Zero output voltage when input voltage is zero.
- □ Infinite bandwidth, so that any frequency signal from 0 to ∞Hz can be amplified without attenuation.
- □ Infinite CMRR so that the output Common mode noise voltage is zero.
- Infinite Slew rate so that output voltage changes occurs simultaneously with input voltage changes.



$$\mathbf{V}_{io} = \mathbf{A}\mathbf{V}_{id} = \mathbf{A}\left(\mathbf{V}_1 - \mathbf{V}_2\right)$$



#### **Open** – **Loop Op-Amp Configuration**

- 1. Differential amplifier
- 2. Inverting amplifier
- **3**. Non-Inverting amplifier





### **Differential Input Mode**

- Both input terminals are used
- Input signals are 180° out of phase
- Output is in phase with non-inverting input



## **Inverting Mode**

- Non-Inverting input is grounded (Connected to midsupply)
- Signal is applied to the inverting input
- Output is 180° out of phase with input





- Inverting Input is grounded
- Signal is applied to the non-inverting input
- Output is in phase with the input



### IC 741 OP AMP Pin Diagram

